

**VIETNAM NATIONAL UNIVERSITY - HO CHI MINH CITY**  
**HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY**  
**Faculty of Computer Science and Engineering**



**LAB 4**  
**INTRODUCTION TO SYSTEM ON CHIP**  
**LABORATORY REPORT**  
**Instructor: Pham Kieu Nhat Anh**

**Class: CC01**  
Name: Hoang Thuy Tram  
Student ID: 2353202

Ho Chi Minh city, December 2025

# Contents

<b>1</b>	<b>Github</b>	<b>1</b>
<b>2</b>	<b>RTL implementation</b>	<b>1</b>
2.1	DividerUnsignedPipelined file . . . . .	1
2.2	DatapathMultiCycle file . . . . .	4
<b>3</b>	<b>Testbench</b>	<b>17</b>
3.1	Divider testbench . . . . .	17
3.2	Processor testbench . . . . .	20
<b>4</b>	<b>Testbench results</b>	<b>20</b>
4.1	Divider testbench results . . . . .	20
4.2	Processor testbench results . . . . .	21
<b>5</b>	<b>Simulation waveform</b>	<b>24</b>
5.1	Divider simulation waveform . . . . .	24
5.2	Processor simulation waveform . . . . .	24
<b>6</b>	<b>Timing closure and Resource utilization</b>	<b>26</b>
6.1	Timing closure . . . . .	26
6.2	Resouce utilization . . . . .	26

# 1 Github

The Lab 4 project files (RTL source code, testbenches, simulation scripts) are located in the Lab04 folder. They are available at the following repository: <https://github.com/trxmhoang/SoC.git>

## 2 RTL implementation

### 2.1 DividerUnsignedPipelined file

The DividerUnsignedPipelined module implements a high-throughput divider using an 8-stage pipeline. Instead of calculating the full 32-bit division in a single cycle, which would require a long critical path, the workload is distributed across 8 clock cycles. Each stage processes 4 bits of the quotient using a chain of `divu_liter` sub-modules. Registers (`r_dividend`, `r_divisor`, etc) are placed between each stage to store intermediate results, allowing the divider to accept new inputs every clock cycle while producing a result with a latency of 8 cycles.

```
1  `timescale 1ns / 1ns
2
3  // quotient = dividend / divisor
4
5  module DividerUnsignedPipelined (
6      input          clk, rst, stall,
7      input [31:0]   i_dividend,
8      input [31:0]   i_divisor,
9      output reg [31:0] o_remainder,
10     output reg [31:0] o_quotient
11 );
12
13     // TODO: your code here
14     reg [31:0] r_dividend [0:6];
15     reg [31:0] r_divisor [0:6];
16     reg [31:0] r_quotient [0:6];
17     reg [31:0] r_remainder [0:6];
18
19     // STAGE 0
20     wire [31:0] s0_dividend [0:4];
21     wire [31:0] s0_quotient [0:4];
22     wire [31:0] s0_remainder [0:4];
23
24     assign s0_dividend[0] = i_dividend;
25     assign s0_quotient[0] = 32'b0;
26     assign s0_remainder[0] = 32'b0;
27
28     genvar i, j;
29     generate
30         for (j = 0; j < 4; j = j + 1) begin : stage0_loop
31             divu_liter u_div0 (
32                 .i_dividend (s0_dividend[j]),
33                 .i_divisor (i_divisor),
34                 .i_remainder (s0_remainder[j]),
35                 .i_quotient (s0_quotient[j]),
36                 .o_dividend (s0_dividend[j + 1]),
```

```

37         .o_remainder (s0_remainder[j + 1]),
38         .o_quotient   (s0_quotient[j + 1])
39     );
40     end
41 endgenerate
42
43 always @(posedge clk) begin
44     if (rst) begin
45         r_dividend[0] <= 32'b0;
46         r_divisor[0] <= 32'b0;
47         r_quotient[0] <= 32'b0;
48         r_remainder[0] <= 32'b0;
49     end else if (!stall) begin
50         r_dividend[0] <= s0_dividend[4];
51         r_divisor[0] <= i_divisor;
52         r_quotient[0] <= s0_quotient[4];
53         r_remainder[0] <= s0_remainder[4];
54     end
55 end
56
57 // STAGE 1 - STAGE 6
58 generate
59     for (i = 1; i < 7; i = i + 1) begin : pipe_loop
60         wire [31:0] chain_dividend [0:4];
61         wire [31:0] chain_quotient [0:4];
62         wire [31:0] chain_remainder [0:4];
63         wire [31:0] stage_divisor;
64
65         assign chain_dividend[0] = r_dividend[i - 1];
66         assign chain_quotient[0] = r_quotient[i - 1];
67         assign chain_remainder[0] = r_remainder[i - 1];
68         assign stage_divisor = r_divisor[i - 1];
69
70         for (j = 0; j < 4; j = j + 1) begin : iter_loop
71             divu_liter u_div (
72                 .i_dividend (chain_dividend[j]),
73                 .i_divisor   (stage_divisor),
74                 .i_remainder (chain_remainder[j]),
75                 .i_quotient  (chain_quotient[j]),
76                 .o_dividend  (chain_dividend[j + 1]),
77                 .o_remainder (chain_remainder[j + 1]),
78                 .o_quotient  (chain_quotient[j + 1])
79             );
80         end
81
82         always @(posedge clk) begin
83             if (rst) begin
84                 r_dividend[i] <= 32'b0;
85                 r_divisor[i] <= 32'b0;
86                 r_quotient[i] <= 32'b0;
87                 r_remainder[i] <= 32'b0;
88             end else if (!stall) begin
89                 r_dividend[i] <= chain_dividend[4];

```

```

90         r_divisor[i] <= stage_divisor;
91         r_quotient[i] <= chain_quotient[4];
92         r_remainder[i] <= chain_remainder[4];
93     end
94 end
95 end
96 endgenerate
97
98 // STAGE 7
99 wire [31:0] s7_dividend [0:4];
100 wire [31:0] s7_quotient [0:4];
101 wire [31:0] s7_remainder [0:4];
102
103 assign s7_dividend[0] = r_dividend[6];
104 assign s7_quotient[0] = r_quotient[6];
105 assign s7_remainder[0] = r_remainder[6];
106
107 generate
108     for (j = 0; j < 4; j = j + 1) begin : stage7_loop
109         divu_1iter u_div7 (
110             .i_dividend (s7_dividend[j]),
111             .i_divisor (r_divisor[6]),
112             .i_remainder (s7_remainder[j]),
113             .i_quotient (s7_quotient[j]),
114             .o_dividend (s7_dividend[j + 1]),
115             .o_remainder (s7_remainder[j + 1]),
116             .o_quotient (s7_quotient[j + 1])
117         );
118     end
119 endgenerate
120
121 always @(posedge clk) begin
122     if (rst) begin
123         o_quotient <= 32'b0;
124         o_remainder <= 32'b0;
125     end else if (!stall) begin
126         o_quotient <= s7_quotient[4];
127         o_remainder <= s7_remainder[4];
128     end
129 end
130 endmodule
131
132 module divu_1iter (
133     input [31:0] i_dividend,
134     input [31:0] i_divisor,
135     input [31:0] i_remainder,
136     input [31:0] i_quotient,
137     output reg [31:0] o_dividend,
138     output reg [31:0] o_remainder,
139     output reg [31:0] o_quotient
140 );
141
142 wire [31:0] new_remainder, subtract;

```

```

143 assign new_remainder = {i_remainder[30:0], i_dividend[31]};
144 assign subtract = new_remainder - i_divisor;
145
146 always @(*) begin
147     o_dividend = i_dividend << 1;
148     if (new_remainder >= i_divisor) begin
149         o_remainder = subtract;
150         o_quotient = {i_quotient[30:0], 1'b1};
151     end else begin
152         o_remainder = new_remainder;
153         o_quotient = {i_quotient[30:0], 1'b0};
154     end
155 end
156 endmodule

```

Program 1: RTL implementation of the DividerUnsignedPipelined file.

## 2.2 DatapathMultiCycle file

The DatapathMultiCycle file is an enhanced version of the previous DatapathSingleCycle file. While the core instruction decoding and execution logic remain similar, this module integrates the 8-stage pipelined divider to handle division operations (DIV, DIVU, REM, REMU). This change allows the processor to manage long-latency arithmetic operations without halting the entire system permanently, although in this initial integration, the processor stalls to wait for the result.

Since the new divider takes 8 clock cycles to compute a result, the processor cannot proceed to the next instruction immediately when a division opcode is detected. A stall counter mechanism was added to freeze the Program Counter (PC) and the instruction fetch process.

- Logic: When a division-type instruction (`is_div_op`) is detected, a counter increments from 0 to 8.
- Stall signal (`stall_en`): This signal remains high while `stall_counter < 8`, effectively pausing the PC update and instruction fetch.
- Resume: Once the counter reaches 8, the divider's output is valid. The stall signal goes low, allowing the result to be written to the register file (`rf_we` enables) and the PC to advance to the next instruction.

```

1  /* INSERT NAME AND PENNKEY HERE */
2
3  `timescale 1ns / 1ns
4
5  // registers are 32 bits in RV32
6  `define REG_SIZE 31
7
8  // RV opcodes are 7 bits
9  `define OPCODE_SIZE 6
10
11 // Don't forget your CLA and Divider
12 /* `include "cla.v"
13 `include "DividerUnsignedPipelined.v" */
14

```

```

15 module RegFile (
16     input          [4:0] rd,
17     input          ['REG_SIZE:0] rd_data,
18     input          [4:0] rs1,
19     output reg     ['REG_SIZE:0] rs1_data,
20     input          [4:0] rs2,
21     output reg     ['REG_SIZE:0] rs2_data,
22     input          clk,
23     input          we,
24     input          rst
25 );
26
27 // TODO: copy your homework #3 code here
28 localparam NumRegs = 32;
29 reg ['REG_SIZE:0] regs[0:NumRegs-1];
30 integer i;
31
32 always @(posedge clk or posedge rst) begin
33     if (rst) begin
34         for (i = 0; i < NumRegs; i = i + 1) begin
35             regs[i] <= 0;
36         end
37     end else if (we && (rd != 0)) begin
38         regs[rd] <= rd_data;
39     end
40 end
41
42 always @(*) begin
43     rs1_data = (rs1 == 0) ? 32'd0 : regs[rs1];
44     rs2_data = (rs2 == 0) ? 32'd0 : regs[rs2];
45 end
46 endmodule
47
48 module DatapathMultiCycle (
49     input          clk,
50     input          rst,
51     output reg     halt,
52     output          ['REG_SIZE:0] pc_to_imem,
53     input          ['REG_SIZE:0] inst_from_imem,
54     // addr_to_dmem is a read-write port
55     output reg     ['REG_SIZE:0] addr_to_dmem,
56     input          ['REG_SIZE:0] load_data_from_dmem,
57     output reg     ['REG_SIZE:0] store_data_to_dmem,
58     output reg     [3:0] store_we_to_dmem
59 );
60
61 // TODO: your code here (largely based on homework #3)
62 // components of the instruction
63 wire [6:0] inst_func7;
64 wire [4:0] inst_rs2;
65 wire [4:0] inst_rs1;
66 wire [2:0] inst_func3;
67 wire [4:0] inst_rd;

```

```

68 wire ['OPCODE_SIZE:0] inst_opcode;
69
70 // split R-type instruction - see section 2.2 of RiscV spec
71 assign {inst_funct7, inst_rs2, inst_rs1, inst_funct3, inst_rd,
       inst_opcode} = inst_from_imem;
72
73 // setup for I, S, B & J type instructions
74 // I - short immediates and loads
75 wire [11:0] imm_i;
76 assign imm_i = inst_from_imem[31:20];
77 wire [ 4:0] imm_shamt = inst_from_imem[24:20];
78
79 // S - stores
80 wire [11:0] imm_s;
81 assign imm_s = {inst_funct7, inst_rd};
82
83 // B - conditionals
84 wire [12:0] imm_b;
85 assign {imm_b[12], imm_b[10:1], imm_b[11], imm_b[0]} = {inst_funct7,
       inst_rd, 1'b0};
86
87 // J - unconditional jumps
88 wire [20:0] imm_j;
89 assign {imm_j[20], imm_j[10:1], imm_j[11], imm_j[19:12], imm_j[0]} =
       {inst_from_imem[31:12], 1'b0};
90
91 wire ['REG_SIZE:0] imm_i_sext = {{20{imm_i[11]}}, imm_i[11:0]};
92 wire ['REG_SIZE:0] imm_s_sext = {{20{imm_s[11]}}, imm_s[11:0]};
93 wire ['REG_SIZE:0] imm_b_sext = {{19{imm_b[12]}}, imm_b[12:0]};
94 wire ['REG_SIZE:0] imm_j_sext = {{11{imm_j[20]}}, imm_j[20:0]};
95
96 // opcodes - see section 19 of RiscV spec
97 localparam ['OPCODE_SIZE:0] OpLoad      = 7'b00_000_11;
98 localparam ['OPCODE_SIZE:0] OpStore     = 7'b01_000_11;
99 localparam ['OPCODE_SIZE:0] OpBranch    = 7'b11_000_11;
100 localparam ['OPCODE_SIZE:0] OpJalr     = 7'b11_001_11;
101 localparam ['OPCODE_SIZE:0] OpMiscMem  = 7'b00_011_11;
102 localparam ['OPCODE_SIZE:0] OpJal      = 7'b11_011_11;
103
104 localparam ['OPCODE_SIZE:0] OpRegImm    = 7'b00_100_11;
105 localparam ['OPCODE_SIZE:0] OpRegReg    = 7'b01_100_11;
106 localparam ['OPCODE_SIZE:0] OpEnviron  = 7'b11_100_11;
107
108 localparam ['OPCODE_SIZE:0] OpAuipc     = 7'b00_101_11;
109 localparam ['OPCODE_SIZE:0] OpLui      = 7'b01_101_11;
110
111 wire inst_lui      = (inst_opcode == OpLui      );
112 wire inst_auipc    = (inst_opcode == OpAuipc    );
113 wire inst_jal      = (inst_opcode == OpJal      );
114 wire inst_jalr     = (inst_opcode == OpJalr     );
115
116 wire inst_beq      = (inst_opcode == OpBranch ) & (inst_from_imem
       [14:12] == 3'b000);

```



```

117 wire inst_bne      = (inst_opcode == OpBranch ) & (inst_from_imem
    [14:12] == 3'b001);
118 wire inst_blt      = (inst_opcode == OpBranch ) & (inst_from_imem
    [14:12] == 3'b100);
119 wire inst_bge      = (inst_opcode == OpBranch ) & (inst_from_imem
    [14:12] == 3'b101);
120 wire inst_bltu     = (inst_opcode == OpBranch ) & (inst_from_imem
    [14:12] == 3'b110);
121 wire inst_bgeu     = (inst_opcode == OpBranch ) & (inst_from_imem
    [14:12] == 3'b111);
122
123 wire inst_lb       = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b000);
124 wire inst_lh       = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b001);
125 wire inst_lw       = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b010);
126 wire inst_lbu      = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b100);
127 wire inst_lhu      = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b101);
128
129 wire inst_sb       = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b000);
130 wire inst_sh       = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b001);
131 wire inst_sw       = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b010);
132
133 wire inst_addi      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b000);
134 wire inst_slti      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b010);
135 wire inst_sltiu     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b011);
136 wire inst_xori      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b100);
137 wire inst_ori       = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b110);
138 wire inst_andi      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b111);
139
140 wire inst_slli      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b001) & (inst_from_imem[31:25] == 7'd0      );
141 wire inst_srli      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'd0      );
142 wire inst_srai      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'b0100000);
143
144 wire inst_add       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b000) & (inst_from_imem[31:25] == 7'd0      );
145 wire inst_sub       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b000) & (inst_from_imem[31:25] == 7'b0100000);

```

```

146 wire inst_sll      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b001) & (inst_from_imem[31:25] == 7'd0      );
147 wire inst_slt      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b010) & (inst_from_imem[31:25] == 7'd0      );
148 wire inst_sltu     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b011) & (inst_from_imem[31:25] == 7'd0      );
149 wire inst_xor      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b100) & (inst_from_imem[31:25] == 7'd0      );
150 wire inst_srl      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'd0      );
151 wire inst_sra      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'b0100000);
152 wire inst_or       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b110) & (inst_from_imem[31:25] == 7'd0      );
153 wire inst_and      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b111) & (inst_from_imem[31:25] == 7'd0      );
154
155 wire inst_mul       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b000      );
156 wire inst_mulh     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b001      );
157 wire inst_mulhsu   = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b010      );
158 wire inst_mulhu    = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b011      );
159 wire inst_div      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b100      );
160 wire inst_divu     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b101      );
161 wire inst_rem      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b110      );
162 wire inst_remu     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b111      );
163
164 wire inst_ecall     = (inst_opcode == OpEnviron) & (inst_from_imem
    [31:7]  == 25'd0  );
165 wire inst_fence     = (inst_opcode == OpMiscMem);
166
167 // stall
168 reg [3:0] stall_counter;
169 wire stall_en;
170 wire is_div_op = inst_div | inst_divu | inst_rem | inst_remu;
171
172 always @(posedge clk) begin
173     if (rst) begin
174         stall_counter <= 0;
175     end else begin
176         if (is_div_op) begin
177             if (stall_counter < 8) begin
178                 stall_counter <= stall_counter + 1;
179             end else begin
180                 stall_counter <= 0;
181             end
182         end
183     end

```

```

182         end else begin
183             stall_counter <= 0;
184         end
185     end
186 end
187
188 assign stall_en = is_div_op & (stall_counter < 8);
189
190 // program counter
191 reg ['REG_SIZE:0] pcNext, pcCurrent;
192 always @(posedge clk) begin
193     if (rst) begin
194         pcCurrent <= 32'd0;
195     end else if (!stall_en) begin
196         pcCurrent <= pcNext;
197     end
198 end
199 assign pc_to_imem = pcCurrent;
200
201 // cycle/inst._from_imem counters
202 reg ['REG_SIZE:0] cycles_current, num_inst_current;
203 always @(posedge clk) begin
204     if (rst) begin
205         cycles_current <= 0;
206         num_inst_current <= 0;
207     end else begin
208         cycles_current <= cycles_current + 1;
209         if (!rst && !stall_en) begin
210             num_inst_current <= num_inst_current + 1;
211         end
212     end
213 end
214
215 // NOTE: don't rename your RegFile instance as the tests expect it
216 // to be 'rf'
217 // TODO: you will need to edit the port connections, however.
218 wire ['REG_SIZE:0] rs1_data;
219 wire ['REG_SIZE:0] rs2_data;
220 reg ['REG_SIZE:0] rd_data;
221 reg rf_we;
222
223 RegFile rf (
224     .clk      (clk),
225     .rst      (rst),
226     .we       (rf_we),
227     .rd       (inst_rd),
228     .rd_data  (rd_data),
229     .rs1      (inst_rs1),
230     .rs2      (inst_rs2),
231     .rs1_data (rs1_data),
232     .rs2_data (rs2_data)
233 );

```

```

234 wire [31:0] cla_res, cla_op_b, cla_op_b_raw;
235 wire cla_cin;
236
237 assign cla_op_b_raw = (inst_opcode == OpRegImm) ? imm_i_sext :
    rs2_data;
238 assign cla_op_b = inst_sub ? ~cla_op_b_raw : cla_op_b_raw;
239 assign cla_cin = inst_sub ? 1'b1 : 1'b0;
240
241 cla u_cla (
242     .a      (rs1_data),
243     .b      (cla_op_b),
244     .cin     (cla_cin),
245     .sum     (cla_res)
246 );
247
248 wire [31:0] div_op_a, div_op_b;
249 wire is_signed_div;
250
251 assign is_signed_div = inst_div | inst_rem;
252 assign div_op_a = (is_signed_div & rs1_data[31]) ? (~rs1_data + 1) :
    rs1_data;
253 assign div_op_b = (is_signed_div & rs2_data[31]) ? (~rs2_data + 1) :
    rs2_data;
254
255 wire [31:0] div_quot_raw, div_rem_raw;
256 DividerUnsignedPipelined u_div (
257     .clk (clk),
258     .rst (rst),
259     .stall (1'b0),
260     .i_dividend (div_op_a),
261     .i_divisor   (div_op_b),
262     .o_quotient  (div_quot_raw),
263     .o_remainder (div_rem_raw)
264 );
265
266 reg [31:0] div_res;
267 always @(*) begin
268     if (inst_div || inst_divu) begin
269         if (rs2_data == 0) begin
270             div_res = 32'hFFFFFF_FFFF;
271         end else if (inst_div && (rs1_data == 32'h8000_0000) && (
            rs2_data == 32'hFFFFFF_FFFF)) begin
272             div_res = 32'h8000_0000;
273         end else if (is_signed_div && (rs1_data[31] ^ rs2_data[31]))
            begin
274             div_res = ~div_quot_raw + 32'd1;
275         end else begin
276             div_res = div_quot_raw;
277         end
278     end else begin // rem or remu
279         if (rs2_data == 0) begin
280             div_res = rs1_data;
281         end else if (inst_rem && (rs1_data == 32'h8000_0000) && (

```

```

        rs2_data == 32'hFFFF_FFFF)) begin
282     div_res = 32'd0;
283 end else if (is_signed_div && (rs1_data[31])) begin
284     div_res = ~div_rem_raw + 32'd1;
285 end else begin
286     div_res = div_rem_raw;
287 end
288 end
289 end
290
291 wire [63:0] mul_u, mul_s, mul_su;
292 assign mul_u = {32'b0, rs1_data} * {32'b0, rs2_data};
293 assign mul_s = $signed(rs1_data) * $signed(rs2_data);
294 assign mul_su = $signed(rs1_data) * $signed({1'b0, rs2_data});
295
296 reg take_branch;
297 always @(*) begin
298     case (inst_funct3)
299         3'b000: take_branch = (rs1_data == rs2_data);
300             // beq
301         3'b001: take_branch = (rs1_data != rs2_data);
302             // bne
303         3'b100: take_branch = ($signed(rs1_data) < $signed(rs2_data));
304             // blt
305         3'b101: take_branch = ($signed(rs1_data) >= $signed(rs2_data));
306             // bge
307         3'b110: take_branch = (rs1_data < rs2_data);
308             // bltu
309         3'b111: take_branch = (rs1_data >= rs2_data);
310             // bgeu
311         default: take_branch = 1'b0;
312     endcase
313 end
314
315 reg [31:0] load_data;
316 always @(*) begin
317     case (addr_to_dmem[1:0])
318         2'b00: load_data = load_data_from_dmem;
319         2'b01: load_data = load_data_from_dmem >> 8;
320         2'b10: load_data = load_data_from_dmem >> 16;
321         2'b11: load_data = load_data_from_dmem >> 24;
322     endcase
323 end
324
325 reg illegal_inst;
326
327 always @(*) begin
    illegal_inst = 1'b0;
    pcNext = pcCurrent + 4;
    rf_we = 0;
    rd_data = 0;
    halt = 0;
    addr_to_dmem = 0;

```

```

328     store_data_to_dmem = 0;
329     store_we_to_dmem = 0;
330
331     case (inst_opcode)
332     OpLui: begin
333         // TODO: start here by implementing lui
334         rf_we = 1;
335         rd_data = {inst_from_imem[31:12], 12'b0};
336     end
337
338     OpAuipc: begin
339         rf_we = 1;
340         rd_data = pcCurrent + {inst_from_imem[31:12], 12'b0};
341     end
342
343     OpJal: begin
344         rf_we = 1;
345         rd_data = pcCurrent + 4;
346         pcNext = pcCurrent + imm_j_sext;
347     end
348
349     OpJalr: begin
350         rf_we = 1;
351         rd_data = pcCurrent + 4;
352         pcNext = (rs1_data + imm_i_sext) & ~32'd1;
353     end
354
355     OpBranch: begin
356         if (take_branch) begin
357             pcNext = pcCurrent + imm_b_sext;
358         end
359     end
360
361     OpLoad: begin
362         rf_we = 1;
363         addr_to_dmem = rs1_data + imm_i_sext;
364
365         case (inst_func3)
366             3'b000: rd_data = {{24{load_data[7]}}}, load_data[7:0]]; //
367                     lb
368             3'b001: rd_data = {{16{load_data[15]}}}, load_data[15:0]]; //
369                     lh
370             3'b010: rd_data = load_data; //
371                     lw
372             3'b100: rd_data = {24'b0, load_data[7:0]]; //
373                     lbu
374             3'b101: rd_data = {16'b0, load_data[15:0]]; //
375                     lhu
376         endcase
377     end
378
379     OpStore: begin
380         addr_to_dmem = rs1_data + imm_s_sext;

```

```

376     store_data_to_dmem = rs2_data << (addr_to_dmem[1:0] * 8);
377
378     case (inst_funct3)
379         3'b000: store_we_to_dmem = 4'b0001 << addr_to_dmem[1:0]; //
                 sb
380         3'b001: store_we_to_dmem = 4'b0011 << addr_to_dmem[1:0]; //
                 sh
381         3'b010: store_we_to_dmem = 4'b1111; //
                 sw
382     endcase
383 end
384
385 OpRegImm: begin
386     rf_we = 1;
387     case (inst_funct3)
388         3'b000: rd_data = cla_res; // addi
389         3'b010: rd_data = ($signed(rs1_data) < $signed(imm_i_sext))
                 ? 32'd1 : 32'd0; // slti
390         3'b011: rd_data = (rs1_data < imm_i_sext) ? 32'd1 : 32'd0;
                 // sltiu
391         3'b100: rd_data = rs1_data ^ imm_i_sext;
                 // xori
392         3'b110: rd_data = rs1_data | imm_i_sext;
                 // ori
393         3'b111: rd_data = rs1_data & imm_i_sext;
                 // andi
394         3'b001: rd_data = rs1_data << imm_shamt;
                 // slli
395         3'b101: begin
396             if (inst_funct7 == 7'd0) begin
397                 rd_data = rs1_data >> imm_shamt;
398                 // srli
399             end else begin
400                 rd_data = $signed(rs1_data) >>> imm_shamt;
401                 // srai
402             end
403         end
404     endcase
405 end
406
407 OpRegReg: begin
408     if (is_div_op) begin
409         rf_we = !stall_en;
410     end else begin
411         rf_we = 1;
412     end
413
414     if (inst_funct7 == 7'd1) begin
415         case (inst_funct3)
416             3'b000: rd_data = rs1_data * rs2_data; // mul
417             3'b001: rd_data = mul_s[63:32]; // mulh
418             3'b010: rd_data = mul_su[63:32]; //

```

```

417         mulhsu
418         3'b011: rd_data = mul_u[63:32]; //
        mulhu
419         3'b100, 3'b101, 3'b110, 3'b111: rd_data = div_res; // div,
        divu, rem, remu
420     endcase
421     end else begin
422         case (inst_funct3)
423             3'b000: rd_data = cla_res;
// add,
        sub
424             3'b001: rd_data = rs1_data << rs2_data[4:0];
// sll
425             3'b010: rd_data = ($signed(rs1_data) < $signed(rs2_data))
        ? 32'd1 : 32'd0; // slt
426             3'b011: rd_data = (rs1_data < rs2_data) ? 32'd1 : 32'd0;
// sltu
427             3'b100: rd_data = rs1_data ^ rs2_data;
// xor
428             3'b101: begin
        if (inst_funct7[5]) rd_data = $signed(rs1_data) >>>
            rs2_data[4:0]; // sra
429             else rd_data = rs1_data >> rs2_data[4:0];
// srl
430         end
431             3'b110: rd_data = rs1_data | rs2_data;
// or
432             3'b111: rd_data = rs1_data & rs2_data;
// and
433         endcase
434     end
435 end
436
437 OpEnviron: begin
438     if (inst_from_imem[31:7] == 25'd0) halt = 1'b1; // ecall
439 end
440
441 default: begin
442     illegal_inst = 1'b1;
443 end
444 endcase
445 end
446 endmodule
447
448 module MemorySingleCycle #(
449     parameter NUM_WORDS = 512
450 ) (
451     input rst, // rst for both imem
        and dmem
452     input clock_mem, // clock for both imem
        and dmem
453     input ['REG_SIZE:0] pc_to_imem, // must always be
        aligned to a 4B boundary

```



```

454 output reg ['REG_SIZE:0] inst_from_imem, // the value at memory
      location pc_to_imem
455 input ['REG_SIZE:0] addr_to_dmem, // must always be
      aligned to a 4B boundary
456 output reg ['REG_SIZE:0] load_data_from_dmem, // the value at memory
      location addr_to_dmem
457 input ['REG_SIZE:0] store_data_to_dmem, // the value to be
      written to addr_to_dmem, controlled by store_we_to_dmem
458 // Each bit determines whether to write the corresponding byte of
      store_data_to_dmem to memory location addr_to_dmem.
459 // E.g., 4'b1111 will write 4 bytes. 4'b0001 will write only the
      least-significant byte.
460 input [ 3:0] store_we_to_dmem
461 );
462
463 // memory is arranged as an array of 4B words
464 reg ['REG_SIZE:0] mem_array[0:NUM_WORDS-1];
465
466 // preload instructions to mem_array
467 always @(posedge rst) begin
468     $readmemh("mem_initial_contents.hex", mem_array);
469 end
470
471 localparam AddrMsb = $clog2(NUM_WORDS) + 1;
472 localparam AddrLsb = 2;
473
474 always @(posedge clock_mem) begin
475     inst_from_imem <= mem_array[{pc_to_imem[AddrMsb:AddrLsb]}];
476 end
477
478 always @(negedge clock_mem) begin
479     if (store_we_to_dmem[0]) begin
480         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][7:0] <=
            store_data_to_dmem[7:0];
481     end
482     if (store_we_to_dmem[1]) begin
483         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][15:8] <=
            store_data_to_dmem[15:8];
484     end
485     if (store_we_to_dmem[2]) begin
486         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][23:16] <=
            store_data_to_dmem[23:16];
487     end
488     if (store_we_to_dmem[3]) begin
489         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][31:24] <=
            store_data_to_dmem[31:24];
490     end
491     // dmem is "read-first": read returns value before the write
492     load_data_from_dmem <= mem_array[{addr_to_dmem[AddrMsb:AddrLsb]}];
493 end
494 endmodule
495
496 /*

```

```

497 This shows the relationship between clock_proc and clock_mem. The
    clock_mem is
498 phase-shifted 90    from clock_proc. You could think of one proc cycle
    being
499 broken down into 3 parts. During part 1 (which starts @posedge
    clock_proc)
500 the current PC is sent to the imem. In part 2 (starting @posedge
    clock_mem) we
501 read from imem. In part 3 (starting @negedge clock_mem) we read/write
    memory and
502 prepare register/PC updates, which occur at @posedge clock_proc.
503
504
505 proc: | ---- | -----
506
507 mem:  _ _ _ | ---- | _ _ _
508 */
509 module Processor (
510     input  clock_proc,
511     input  clock_mem,
512     input  rst,
513     output halt
514 );
515
516 wire ['REG_SIZE:0] pc_to_imem, inst_from_imem, mem_data_addr,
    mem_data_loaded_value, mem_data_to_write;
517 wire [          3:0] mem_data_we;
518
519 // This wire is set by cocotb to the name of the currently-running
    test, to make it easier
520 // to see what is going on in the waveforms.
521 wire [(8*32)-1:0] test_case;
522
523 MemorySingleCycle #(
524     .NUM_WORDS(8192)
525 ) memory (
526     .rst                (rst),
527     .clock_mem          (clock_mem),
528     // imem is read-only
529     .pc_to_imem         (pc_to_imem),
530     .inst_from_imem     (inst_from_imem),
531     // dmem is read-write
532     .addr_to_dmem       (mem_data_addr),
533     .load_data_from_dmem (mem_data_loaded_value),
534     .store_data_to_dmem  (mem_data_to_write),
535     .store_we_to_dmem    (mem_data_we)
536 );
537
538 DatapathMultiCycle datapath (
539     .clk                (clock_proc),
540     .rst                (rst),
541     .pc_to_imem         (pc_to_imem),
542     .inst_from_imem     (inst_from_imem),

```

```

543     .addr_to_dmem      (mem_data_addr),
544     .store_data_to_dmem (mem_data_to_write),
545     .store_we_to_dmem   (mem_data_we),
546     .load_data_from_dmem (mem_data_loaded_value),
547     .halt               (halt)
548 );
549 endmodule

```

Program 2: RTL implementation of the DatapathMultiCycle file.

## 3 Testbench

### 3.1 Divider testbench

This testbench is used to verify the functional correctness and the latency of the 8-stage Pipelined Unsigned Divider. Unlike standard combinational logic tests, this testbench must account for the 8-cycle latency between input stimulus and valid output.

The testbench uses two separate `initial` blocks running in parallel to handle the pipelined nature of the device:

- Stimulus generator: Feeds input data into the divider on every clock cycle.
- Output checker: Waits for the pipeline latency (roughly 10 cycles for reset and pipeline stages) before beginning to check the output against the expected values.

The testbench generates 15 random and directed test cases:

- Test 0: The first iteration test has exact division.
- Test 1: The second iteration test has remainder.
- Test 2: The third iteration test has dividend smaller than divisor.
- Test 3-14: The remaining cases use `$random` to generate arbitrary 32-bit values to ensure robust coverage.

```

1  `timescale 1ns / 1ps
2  module tb_div;
3  reg clk, rst, stall;
4  reg [31:0] i_dividend, i_divisor;
5  wire [31:0] o_remainder, o_quotient;
6
7  integer i, j;
8  integer pass, fail;
9  parameter TEST_CNT = 15;
10
11 reg [31:0] i_divd [0:TEST_CNT-1];
12 reg [31:0] i_divs [0:TEST_CNT-1];
13 reg [31:0] exp_quot [0:TEST_CNT-1];
14 reg [31:0] exp_rem [0:TEST_CNT-1];
15
16 DividerUnsignedPipelined dut (
17     .clk(clk),

```

```

18     .rst(rst),
19     .stall(stall),
20     .i_dividend(i_dividend),
21     .i_divisor(i_divisor),
22     .o_remainder(o_remainder),
23     .o_quotient(o_quotient)
24 );
25
26 task divi;
27     $display ("%0s", {80{"-"}});
28 endtask
29
30 task br;
31     $display ("%0s", {100{"="}});
32 endtask
33
34 task msg (input [700:0] txt);
35     begin
36         br();
37         $display ("%0s", txt);
38         br();
39     end
40 endtask
41
42 initial begin
43     clk = 0;
44     forever #5 clk = ~clk;
45 end
46
47 initial begin
48     $dumpfile("wave_div.vcd");
49     $dumpvars(0, tb_div);
50     msg ("TEST BEGIN");
51
52     rst = 1;
53     stall = 0;
54     i_dividend = 0;
55     i_divisor = 1;
56     pass = 0;
57     fail = 0;
58     #20;
59
60     @(negedge clk);
61     rst = 0;
62     repeat (2) @(posedge clk);
63
64     for (i = 0; i < TEST_CNT; i = i + 1) begin
65         @(negedge clk);
66         if (i == 0) begin
67             i_divd[i] = 100;
68             i_divs[i] = 10; // chia het
69         end else if (i == 1) begin
70             i_divd[i] = 100;

```

```

71         i_divs[i] = 30; // co du
72     end else if (i == 2) begin
73         i_divd[i] = 5;
74         i_divs[i] = 10; // bi chia < chia
75     end else begin
76         i_divd[i] = $random;
77         i_divs[i] = ($random % 100) + 1;
78     end
79
80     i_dividend = i_divd[i];
81     i_divisor = i_divs[i];
82
83     exp_quot[i] = i_divd[i] / i_divs[i];
84     exp_rem[i] = i_divd[i] % i_divs[i];
85 end
86
87 @(negedge clk);
88 i_dividend = 0;
89 i_divisor = 1;
90 end
91
92 initial begin
93     wait (rst == 0);
94     repeat (10) @(posedge clk); // 2 delay + 8 latency = 10
95
96     for (j = 0; j < TEST_CNT; j = j + 1) begin
97         @(negedge clk);
98         if ((o_quotient === exp_quot[j]) && (o_remainder === exp_rem[j]
99             ])) begin
100             $display("[PASS] Time = %0t | Test #%2d: %d / %d | Output
101                 Q = %d, R = %d", $time, j, i_divd[j], i_divs[j],
102                 o_quotient, o_remainder);
103             pass = pass + 1;
104         end else begin
105             $display("[FAIL] Time = %0t | Test #%2d: %d / %d | Expect
106                 Q = %d, R = %d | Output Q = %d, R = %d", $time, j,
107                 i_divd[j], i_divs[j], exp_quot[j], exp_rem[j],
108                 o_quotient, o_remainder);
109             fail = fail + 1;
110         end
111     end
112
113     msg ("SUMMARY");
114     $display ("TOTAL TESTS : %0d", pass + fail);
115     $display ("TOTAL PASSED: %0d", pass);
116     $display ("TOTAL FAILED: %0d", fail);
117
118     if (fail == 0)
119         $display ("=====> ALL TESTS PASSED");
120     else if (pass == 0)
121         $display ("=====> ALL TESTS FAILED");
122     else
123         $display ("=====> SOME TESTS FAILED");

```

```

118
119     msg ("TEST END");
120
121     #100;
122     $finish;
123 end
124 endmodule

```

Program 3: Testbench implementation of the DividerUnsignedPipelined module.

## 3.2 Processor testbench

To verify the `DatapathMultiCycle` file, we reused the testbench originally designed for the `DatapathSingleCycle` file (`tb_single.v`), can be viewed again in Section 4.2 in Lab 3 report. This approach is valid because the Instruction Set Architecture (ISA) interface remains identical between the two designs. Both processors:

- Read 32-bit instruction from memory.
- Execute standard RV32I instructions (ADD, SUB, BEQ, etc).
- Perform division operations (DIV, DIVU, REM, REMU), although with different internal latencies.
- Ultimately update the register file and memory with the same correct values.

Since the testbench verifies correctness based on the final state rather than internal details, it serves as an effective regression test to ensure that the new multi-cycle features did not break existing functionality.

While the test logic remains the same, the execution time for division-heavy programs increase significantly due to the 8-cycle latency per division operation.

## 4 Testbench results

All test cases executed successfully for all tested modules, with each marked as **PASSED**. This outcome confirms that the test modules behave as intended and that the implemented RTL designs meet the expected functionality.

### 4.1 Divider testbench results

```

1 # =====
2 # TEST BEGIN
3 # =====
4 # [PASS] Time = 120000 | Test # 0:          100 /          10 | Output Q
   =          10, R =          0
5 # [PASS] Time = 130000 | Test # 1:          100 /          30 | Output Q
   =          3, R =          10
6 # [PASS] Time = 140000 | Test # 2:           5 /          10 | Output Q
   =          0, R =           5
7 # [PASS] Time = 150000 | Test # 3: 303379748 / 4294967198 | Output Q
   =          0, R = 303379748

```

```

8 # [PASS] Time = 160000 | Test # 4: 2223298057 / 4294967288 | Output Q
  = 0, R = 2223298057
9 # [PASS] Time = 170000 | Test # 5: 112818957 / 58 | Output Q
  = 1945154, R = 25
10 # [PASS] Time = 180000 | Test # 6: 2999092325 / 4294967283 | Output Q
   = 0, R = 2999092325
11 # [PASS] Time = 190000 | Test # 7: 15983361 / 30 | Output Q
   = 532778, R = 21
12 # [PASS] Time = 200000 | Test # 8: 992211318 / 98 | Output Q
   = 10124605, R = 28
13 # [PASS] Time = 210000 | Test # 9: 1993627629 / 13 | Output Q
   = 153355971, R = 6
14 # [PASS] Time = 220000 | Test #10: 2097015289 / 4294967227 | Output Q
   = 0, R = 2097015289
15 # [PASS] Time = 230000 | Test #11: 3807872197 / 4294967223 | Output Q
   = 0, R = 3807872197
16 # [PASS] Time = 240000 | Test #12: 1924134885 / 4294967256 | Output Q
   = 0, R = 1924134885
17 # [PASS] Time = 250000 | Test #13: 2301810194 / 40 | Output Q
   = 57545254, R = 34
18 # [PASS] Time = 260000 | Test #14: 2033215986 / 4294967251 | Output Q
   = 0, R = 2033215986
19 # =====
20 # SUMMARY
21 # =====
22 # TOTAL TESTS : 15
23 # TOTAL PASSED: 15
24 # TOTAL FAILED: 0
25 # =====> ALL TESTS PASSED
26 # =====
27 # TEST END
28 # =====
29 # ** Note: $finish : ../../tb/tb_div.v(122)
30 # Time: 360 ns Iteration: 0 Instance: /tb_div

```

Simulation 1: Testbench results of the DividerUnsignedPipelined module.

## 4.2 Processor testbench results

```

1 # =====
2 # TEST BEGIN
3 # =====
4 # =====
5 # TEST 1
6 # =====
7 # [PASS] Time = 691 | ADDI x1, x0, 10 | Output x1 = 0
  x0000000a
8 # [PASS] Time = 691 | ADDI x2, x0, -5 | Output x2 = 0
  xfffffffb
9 # [PASS] Time = 691 | ADD x3, x1, x2 | Output x3 = 0
  x00000005
10 # [PASS] Time = 691 | SUB x4, x1, x2 | Output x4 = 0
   x0000000f

```

11	# [PASS] Time = 691	AND x5, x1, x2   Output x5 = 0
	x0000000a	
12	# [PASS] Time = 691	OR x6, x1, x2   Output x6 = 0
	xffffffffb	
13	# [PASS] Time = 691	XOR x7, x1, x2   Output x7 = 0
	xffffffff1	
14	# [PASS] Time = 691	SLLI x8, x1, 2   Output x8 = 0
	x00000028	
15	# [PASS] Time = 691	SRAI x9, x2, 1   Output x9 = 0
	xffffffffd	
16	# [PASS] Time = 691	SRLI x10, x2, 1   Output x10 = 0
	x7ffffffd	
17	# [PASS] Time = 691	SLT x11, x2, x1   Output x11 = 0
	x00000001	
18	# [PASS] Time = 691	SLTU x12, x2, x1   Output x12 = 0
	x00000000	
19	# [PASS] Time = 691	MUL x13, x1, x1   Output x13 = 0
	x00000064	
20	# [PASS] Time = 691	DIV x14, x1, x2   Output x14 = 0
	xffffffffe	
21	# [PASS] Time = 691	REM x15, x1, x2   Output x15 = 0
	x00000000	
22	# [PASS] Time = 691	DIVU x16, x2, x1   Output x16 = 0
	x19999999	
23	# [PASS] Time = 691	LW x18, 100(x0)   Output x18 = 0
	x00000005	
24	# [PASS] Time = 691	ADDI x19, x0, 1   Output x19 = 0
	x00000001	
25	# [PASS] Time = 691	JAL x20, 8   Output x20 = 0
	x00000058	
26	# [PASS] Time = 691	ADDI x21, x0, 2   Output x21 = 0
	x00000002	
27	# [PASS] Time = 691	LUI x22, 0x12345   Output x22 = 0
	x12345000	
28	# [PASS] Time = 691	XORI x23, x1, 5   Output x23 = 0
	x0000000f	
29	# [PASS] Time = 691	ANDI x24, x1, 0xF   Output x24 = 0
	x0000000a	
30	# [PASS] Time = 691	ORI x25, x13, 0xFF00   Output x25 = 0
	xffffffff64	
31	# [PASS] Time = 691	SLTI x26, x7, 0x28   Output x26 = 0
	x00000001	
32	# [PASS] Time = 691	LTIU x27, x8, 0xFFFF_FFF1   Output x27 = 0
	x00000001	
33	# [PASS] Time = 691	SLL x28, x1, x19   Output x28 = 0
	x00000014	
34	# [PASS] Time = 691	SRL x29, x6, x19   Output x29 = 0
	x7ffffffd	
35	# [PASS] Time = 691	SRA x30, x6, x19   Output x30 = 0
	xffffffffd	
36	# [PASS] Time = 691	REMU x31, x6, x3   Output x31 = 0
	x00000001	
37	# [PASS] HALT asserted.	



```

38 # =====
39 # TEST 2 (REUSED REGISTERS)
40 # =====
41 # [PASS] Time = 971 |      ADDI x1, x0, 0xFFFF_FFFB | Output x1 = 0
      xfffffffbb
42 # [PASS] Time = 971 |      ADDI x2, x0, 3 | Output x2 = 0
      x00000003
43 # [PASS] Time = 971 |      MULH x3, x1, x2 | Output x3 = 0
      xfffffff
44 # [PASS] Time = 971 |      MULHSU x4, x1, x2 | Output x4 = 0
      xfffffff
45 # [PASS] Time = 971 |      MULHU x5, x1, x2 | Output x5 = 0
      x00000002
46 # [PASS] Time = 971 |      ADDI x6, x0, 0xABCD_FE98 | Output x6 = 0
      xfffffe98
47 # [PASS] Time = 971 |      LB x7, 100(x0) | Output x7 = 0
      xffffff98
48 # [PASS] Time = 971 |      LH x8, 104(x0) | Output x8 = 0
      xfffffe98
49 # [PASS] Time = 971 |      LBU x9, 105(x0) | Output x9 = 0
      x000000fe
50 # [PASS] Time = 971 |      LHU x10, 104(x0) | Output x10 = 0
      x0000fe98
51 # [PASS] Time = 971 |      ADD x11, x9, x10 | Output x11 = 0
      x0000ff96
52 # [PASS] Time = 971 |      OR x12, x9, x10 | Output x12 = 0
      x0000fefe
53 # [PASS] Time = 971 |      LW x13, 120(x0) | Output x13 = 0
      x000000fe
54 # [PASS] Time = 971 |      JALR x14, 130(x0) | Output x14 = 0
      x00000054
55 # [PASS] HALT asserted.
56 # =====
57 # SUMMARY
58 # =====
59 # TOTAL TESTS : 46
60 # TOTAL PASSED: 46
61 # TOTAL FAILED: 0
62 # =====> ALL TESTS PASSED
63 # =====
64 # TEST END
65 # =====
66 # ** Note: $finish      : ../../tb/tb_single.v(230)
67 #      Time: 1071 ns   Iteration: 0   Instance: /tb_single

```

Simulation 2: Testbench results of the Processor module.

## 5 Simulation waveform

### 5.1 Divider simulation waveform

 


Figure 1

In Figure 1, the testbench updates the dividend and divisor values on each negative clock edge to initiate new division operations. At 40,000 ps, the first test case loads dividend = 100 (0x64) and divisor = 10 (0x0a). The `DividerUnsignedPipelined` module has an 8-stage pipeline latency, meaning the result appears after 8 positive clock edges. Consequently, at 120,000 ps (8 cycles later), the outputs are updated: quotient = 10 (0x0a) and remainder = 0.

The second test case loads dividend = 100 (0x64) and divisor = 30 (0x1e) at 50,000 ps (one clock cycle after the first). Due to the pipelined architecture, this operation also requires 8 clock cycles to complete. At 130,000 ps, the second result emerges: quotient = 3 and remainder = 10 (0x0a). This pattern continues for subsequent test cases, with each new operation initiated on consecutive negative edges.

 


Figure 2

As shown in Figure 2, once the pipeline is filled (after the initial 8-cycle latency), the divider produces one result per clock cycle in steady-state operation. The testbench loads 15 test cases sequentially, feeding new operands every cycle. After all valid test cases complete, the testbench sets dividend = 0 and divisor = 1 as safe default values to avoid division-by-zero scenarios, which are not handled in this design. Once the pipeline is full, we get one result per cycle, although each operation needs 8 cycles.

### 5.2 Processor simulation waveform

 


Figure 3

Both processor implementations were tested using the same testbench file `tb_single.v` to ensure they produce identical functional results. As shown in Figure 3, the multi-cycle processor executes most instructions with the same behavior as the single-cycle implementation. The register file values, ALU results and memory interface signals match between both designs, confirming that both processors correctly implement the RISC-V instruction set. For instructions like ADD, SUB, LW, SW, and branches, both processors complete execution in one clock cycle and advance the program counter by 4 bytes to fetch the next instruction.

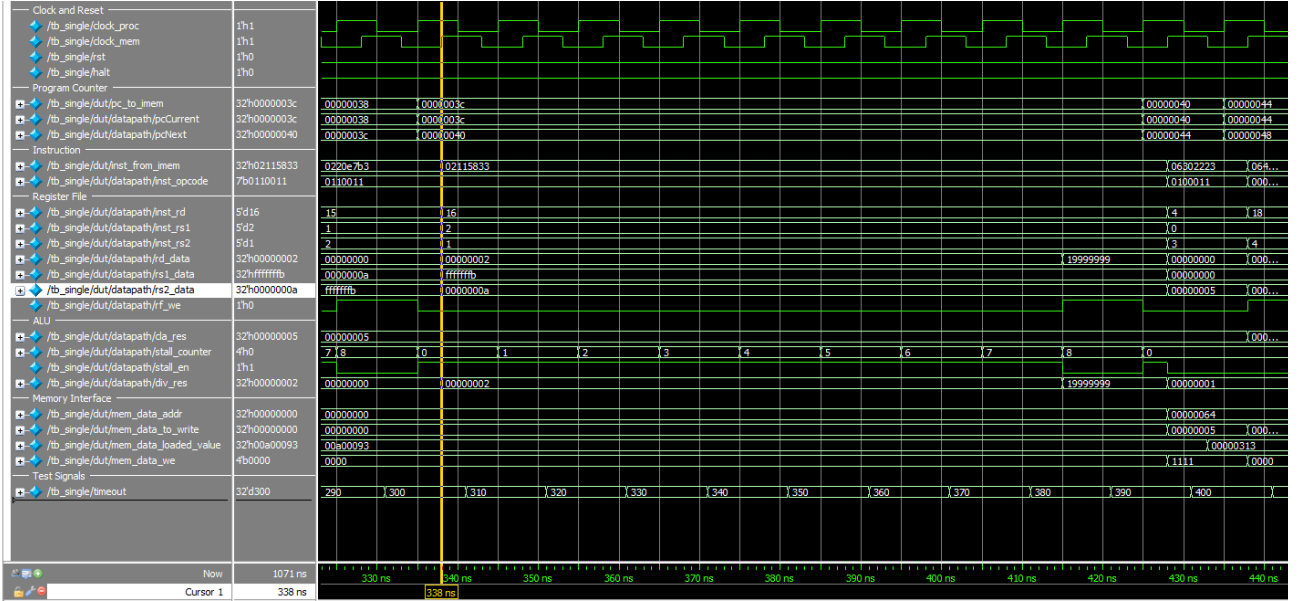


Figure 4

However, a significant difference appears when executing division instructions. The single-cycle processor uses a combinational divider that completes the entire division operation within a single clock cycle. In contrast, the multi-cycle processor employs a pipelined divider which has an 8-stage pipeline architecture. As shown in Figure 4 at approximately 338 ns, when the DIVU instruction is executed, the processor detects that this is a division operation and activates the stall mechanism. The `stall_counter` begins counting from 0 to 8 over eight consecutive clock cycles, during which the `stall_en` signal remains high. While `stall_en` is active, the program counter freezes at its current value (0x3C in this case) and does not advance to the next instruction. The register file write enable signal `rf_we` is also disabled during the stall period, preventing any premature register updates. After finishing the 8-stages pipelines in 8 clock cycles, on the next positive edge `clock_proc`, the program counter finally advanced to the next instruction. Therefore, each division instruction takes 9 clock cycles total: 8 for computation and 1 for safe control handoff, which is standard practice in pipelined processor design where the write-back stage occurs one cycle after the execution stage completes.

Although each individual division takes 9 cycles to complete in the multi-cycle design compared to just 1 cycle in the single-cycle design, the multi-cycle processor can run at a higher clock frequency. For programs that do not heavily rely on division operations, the multi-cycle processor achieves better overall performance through its higher clock frequency despite having a variable CPI (Cycles Per Instruction) of 1 for most instructions and 9 for divisions.

## 6 Timing closure and Resource utilization

### 6.1 Timing closure

Design Timing Summary			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): -9,451 ns	Worst Hold Slack (WHS): -0,239 ns	Worst Pulse Width Slack (WPWS): 3,020 ns	
Total Negative Slack (TNS): -8431,276 ns	Total Hold Slack (THS): -189,649 ns	Total Pulse Width Negative Slack (TPWS): 0,000 ns	
Number of Failing Endpoints: 1290	Number of Failing Endpoints: 1587	Number of Failing Endpoints: 0	
Total Number of Endpoints: 4276	Total Number of Endpoints: 4276	Total Number of Endpoints: 1664	
Timing constraints are not met.			

Figure 5: Timing summary.

After synthesizing and implementing the multi-cycle datapath design on the Arty Z7-20 FPGA, we obtained the following timing results:

- Constraint clock (clock\_proc) frequency: 125 MHz (Period: 8.000 ns)
- Worst Negative Slack (WNS): -9.451 ns
- Conclusion: The design has not achieved Timing closure (Timing constraints are not met).

Based on the WNS, the maximum operating frequency ( $F_{max}$ ) is calculated as follows:

$$T_{min} = T_{constraint} - WNS = 8.000 - (-9.451) = 17.451ns$$

$$F_{max} = \frac{1}{T_{min}} \approx 57.30MHz$$

The previous results we get from the single-cycle datapath design in Lab 3 (can be viewed in Section 7.1) had a significantly lower  $F_{max}$  ( 8.75 MHz). Meanwhile, the introduction of the 8-stage pipelined divider has successfully broken the critical path. The new  $F_{max}$  of 57.30 MHz represents a massive improvement, approximately 6.5 times faster, compared to the single-cycle version. Although the design still does not meet the aggressive 125 MHz constraint, the pipelining strategy has proven effective in reducing the critical path delay, validating the design goal of the multi-cycle architecture.

### 6.2 Resouce utilization

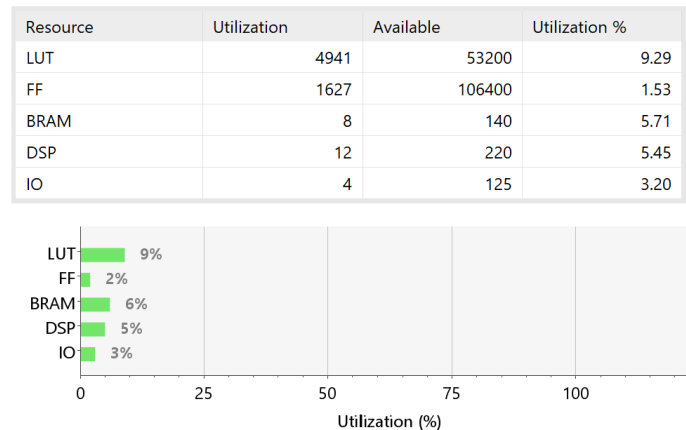


Figure 6: Utilization summary.

Both single-cycle datapath and multi-cycle datapath resulted in 9% LUT usage, indicating that the combinational logic complexity is similar. However, there is a noticeable increase in Flip-Flop utilization, 1.53% vs 0.96% in single-cycle). This increase is directly attributed to the pipeline registers added between the 8 stages of the divider and the new state registers (stall counter) in the datapath. In conclusion, the design fits easily within the Arty Z7-20 FPGA.