

VIETNAM NATIONAL UNIVERSITY - HO CHI MINH CITY
HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY
Faculty of Computer Science and Engineering



LAB 1
INTRODUCTION TO SYSTEM ON CHIP
LABORATORY REPORT
Instructor: Pham Kieu Nhat Anh

Class: CC01
Name: Hoang Thuy Tram
Student ID: 2353202

Ho Chi Minh city, December 2025

Contents

1	Github	1
2	Exercise 1	1
2.1	RTL implementation	1
2.2	Testbench	8
2.3	Testbench results	15
2.4	Simulation waveform	18
2.5	FPGA results	25
3	Exercise 2	27
3.1	RTL implementation	27
3.2	Testbench	29
3.3	Testbench results	33
3.4	Simulation waveform	36
3.5	FPGA results	38
4	Exercise 3	41
4.1	RTL implementation	41
4.2	Testbench	42
4.3	Testbench results	47
4.4	Simulation waveform	49
4.5	FPGA results	51
5	Divider	54
5.1	RTL implementation	54
5.2	Testbench	55
5.3	Testbench results	60

1 Github

The Lab 1 project files (RTL source code, testbenches, simulation scripts) are located in the Lab01 folder. They are available at the following repository: <https://github.com/trxmhoang/SoC.git>

2 Exercise 1

2.1 RTL implementation

The debounce module is designed to filter out mechanical noise, also known as bouncing, that occurs when a physical button is pressed. It ensures that the FPGA only registers a single, clean signal instead of multiple rapid spikes. It outputs two signals, a stable level through signal `btn_stable` and a single-cycle pulse through signal `btn_pulse`, triggered when the button is pressed.

```
1 module debounce (
2     input wire clk,
3     input wire rst_n,
4     input wire btn_in,
5     output reg btn_stable,
6     output reg btn_pulse
7 );
8
9 'ifdef SIMULATION
10    //for sim, debounce is 10 cycles
11    parameter STABLE_CNT = 21'd10;
12 'else
13    //for fpga, use the real delay
14    parameter STABLE_CNT = 21'd1_250_000;
15 'endif
16
17 reg [20:0] cnt;
18 reg btn1;
19 reg btn2;
20 reg btn_stable_pre;
21
22 always @(posedge clk or negedge rst_n) begin
23     if (!rst_n) begin
24         btn1 <= 1;
25         btn2 <= 1;
26         btn_stable <= 1;
27         btn_stable_pre <= 1;
28         btn_pulse <= 0;
29         cnt <= 0;
30     end else begin
31         btn_stable_pre <= btn_stable;
32         btn1 <= btn_in;
33         btn2 <= btn1;
34
35         if (btn2 != btn_stable)
36             if (cnt < STABLE_CNT) cnt <= cnt + 1;
37         else
```

```

38         cnt <= 0;
39
40     if (cnt == STABLE_CNT)
41         btn_stable <= btn2;
42
43     if (btn_stable == 0 && btn_stable_pre == 1)
44         btn_pulse <= 1;
45     else
46         btn_pulse <= 0;
47 end
48
49 endmodule

```

Program 1: RTL implementation for the debounce module of Exercise 1.

The `ex1` module implements the traffic light control system that can be configured. It uses a Finite State Machine to cycle through the standard traffic light sequence: Red, green and yellow for two directions - horizontal and vertical.

The system operates in three modes, selectable via Button 0 through signal `button[0]`:

- Mode 1 (normal operation): The traffic lights cycle automatically. The duration for green and yellow lights is determined by `green_time` and `yellow_time` registers. A 1-second pulse (`pulse_1s`), generated by a clock divider, decrements the timer trigger state transitions.
- Mode 2 (config green lights): The user can adjust the green lights duration (`green_time`) using Button 1 (`button[1]`) to increase and Button 2 (`button [2]`) to decrease, Button 3 (`button[3]`) saves the new value when pressed.
- Mode 3 (config yellow lights): Similar to mode 2, but allows adjustment and saving for the yellow lights duration (`yellow_time`).

The first two 7-segment LEDs on the left-hand side display the current mode, while the two 7-segment LEDs on the right-hand side display the timer while green and yellow LEDs running. Two additional LEDs indicate the current state of the vertical and horizontal traffic lights. During the configuration (Mode 2 and Mode 3), these two LEDs have the same color, all green in Mode 2 and all yellow in Mode 3, indicating to the users that they are configuring which LED timer. When the reset switch is activated, the 7-segment LEDs default to Mode 1 and the timer LEDs are turned off, meanwhile the horizontal and vertical traffic lights both become red to indicate the reset is on. The configured values for the green and yellow timers are preserved during reset, retaining the user's settings.

```

1 module ex1 (
2     input wire clk,
3     input wire rst_n,
4     input wire [3:0] button,
5     output reg [2:0] hor_led,
6     output reg [2:0] ver_led,
7     output reg [3:0] bcd0,
8     output reg [3:0] bcd1,
9     output reg [3:0] bcd2,
10    output reg [3:0] bcd3
11 );

```

```

12
13 parameter RED = 3'b100;
14 parameter YELLOW = 3'b110;
15 parameter GREEN = 3'b010;
16
17 parameter INIT = 3'd0; //initial state
18 parameter HR_VG = 3'd1; //horizontal red - vertical green
19 parameter HR_VY = 3'd2; //horizontal red - vertical yellow
20 parameter HG_VR = 3'd3; //horizontal green - vertical red
21 parameter HY_VR = 3'd4; //horizontal yellow - vertical red
22
23 parameter MODE1 = 2'd1;
24 parameter MODE2 = 2'd2;
25 parameter MODE3 = 2'd3;
26
27 'ifdef SIMULATION
28     //for sim, a sec is 100 cycles
29     parameter PULSE_COUNT = 27'd100;
30 'else
31     //for fpga, a sec is 125m cycles
32     parameter PULSE_COUNT = 27'd125_000_000;
33 'endif
34
35 //clock divider
36 reg [26:0] clk_cnt;
37 wire pulse_1s;
38
39 always @ (posedge clk or negedge rst_n) begin
40     if (!rst_n)
41         clk_cnt <= 27'd0;
42     else if (clk_cnt == PULSE_COUNT - 1)
43         clk_cnt <= 27'd0;
44     else
45         clk_cnt <= clk_cnt + 1;
46 end
47
48 assign pulse_1s = (clk_cnt == PULSE_COUNT - 1);
49
50 //debounce handling
51 wire [3:0] btn_stable;
52 wire [3:0] btn_pulse;
53 wire [3:0] btn_press;
54
55 debounce u_db0 (
56     .clk          (clk),
57     .rst_n        (rst_n),
58     .btn_in       (button[0]),
59     .btn_stable  (btn_stable[0]),
60     .btn_pulse   (btn_pulse[0])
61 );
62
63 debounce u_db1 (
64     .clk          (clk),

```

```

65     .rst_n      (rst_n),
66     .btn_in     (button[1]),
67     .btn_stable (btn_stable[1]),
68     .btn_pulse  (btn_pulse[1])
69 );
70
71 debounce u_db2 (
72     .clk        (clk),
73     .rst_n      (rst_n),
74     .btn_in     (button[2]),
75     .btn_stable (btn_stable[2]),
76     .btn_pulse  (btn_pulse[2])
77 );
78
79 debounce u_db3 (
80     .clk        (clk),
81     .rst_n      (rst_n),
82     .btn_in     (button[3]),
83     .btn_stable (btn_stable[3]),
84     .btn_pulse  (btn_pulse[3])
85 );
86
87 assign btn_press = btn_pulse;
88
89 //button handling
90 reg [2:0] state;
91 reg [6:0] timer;
92 reg [1:0] mode;
93 reg [6:0] green_time = 7'd3, yellow_time = 7'd2;
94 reg [6:0] temp_green_time, temp_yellow_time;
95
96 always @(posedge clk or negedge rst_n) begin
97     if (!rst_n) begin
98         mode <= MODE1;
99         temp_green_time <= green_time;
100        temp_yellow_time <= yellow_time;
101    end else begin
102        case(btn_press)
103            4'b0001: begin
104                case(mode)
105                    MODE1: mode <= MODE2;
106                    MODE2: begin
107                        mode <= MODE3;
108                        temp_green_time <= green_time;
109                    end
110                    MODE3: begin
111                        mode <= MODE1;
112                        temp_yellow_time <= yellow_time;
113                    end
114                    default: begin
115                        mode <= MODE1;
116                        state <= HR_VG;
117                        timer <= green_time;

```

```

118         end
119     endcase
120 end
121
122 4'b0010: begin
123     case(mode)
124         MODE2:
125             if(temp_green_time < 99) temp_green_time <=
126                 temp_green_time + 1;
127         MODE3:
128             if(temp_yellow_time < 20) temp_yellow_time <=
129                 temp_yellow_time + 1;
130         endcase
131     end
132
133 4'b0100: begin
134     case(mode)
135         MODE2:
136             if(temp_green_time > 2) temp_green_time <=
137                 temp_green_time - 1;
138         MODE3:
139             if(temp_yellow_time > 1) temp_yellow_time <=
140                 temp_yellow_time - 1;
141         endcase
142     end
143
144 4'b1000: begin
145     case(mode)
146         MODE2:
147             green_time <= temp_green_time;
148         MODE3:
149             yellow_time <= temp_yellow_time;
150         endcase
151     end
152
153 //led handling
154 always @(posedge clk or negedge rst_n) begin
155     if(!rst_n) begin
156         state <= INIT;
157         timer <= 0;
158     end else if (mode != MODE1) begin
159         state <= INIT;
160         timer <= 0;
161     end else if (pulse_1s) begin
162         case(state)
163             INIT: begin
164                 state <= HR_VG;
165                 timer <= green_time;
166             end

```

```

167     HR_VG: begin
168         if(timer <= 1) begin
169             state <= HR_VY;
170             timer <= yellow_time;
171         end else begin
172             timer <= timer - 1;
173         end
174     end
175
176     HR_VY: begin
177         if(timer <= 1) begin
178             state <= HG_VR;
179             timer <= green_time;
180         end else begin
181             timer <= timer - 1;
182         end
183     end
184
185     HG_VR: begin
186         if(timer <= 1) begin
187             state <= HY_VR;
188             timer <= yellow_time;
189         end else begin
190             timer <= timer - 1;
191         end
192     end
193
194     HY_VR: begin
195         if(timer <= 1) begin
196             state <= HR_VG;
197             timer <= green_time;
198         end else begin
199             timer <= timer - 1;
200         end
201     end
202
203         default: state <= INIT;
204     endcase
205 end else begin
206     state <= state;
207     timer <= timer;
208 end
209 end
210
211 //led display
212 always @(*) begin
213     case (mode)
214         MODE1: begin
215             case (state)
216                 INIT: begin
217                     hor_led = RED;
218                     ver_led = RED;
219                 end

```

```

220
221     HR_VG: begin
222         hor_led = RED;
223         ver_led = GREEN;
224     end
225
226     HR_VY: begin
227         hor_led = RED;
228         ver_led = YELLOW;
229     end
230
231     HG_VR: begin
232         hor_led = GREEN;
233         ver_led = RED;
234     end
235
236     HY_VR: begin
237         hor_led = YELLOW;
238         ver_led = RED;
239     end
240
241     default: begin
242         hor_led = RED;
243         ver_led = RED;
244     end
245     endcase
246 end
247
248 MODE2: begin
249     hor_led = GREEN;
250     ver_led = GREEN;
251 end
252
253 MODE3: begin
254     hor_led = YELLOW;
255     ver_led = YELLOW;
256 end
257
258 default: begin
259     hor_led = RED;
260     ver_led = RED;
261 end
262 endcase
263
264 // segment handling
265 reg [7:0] display_val;
266 reg [3:0] ten_digit;
267 reg [3:0] one_digit;
268
269 always @(*) begin
270     case(mode)
271         MODE1: display_val = timer;

```

```

273     MODE2: display_val = temp_green_time;
274     MODE3: display_val = temp_yellow_time;
275     default: display_val = timer;
276   endcase
277
278   ten_digit = display_val / 10;
279   one_digit = display_val % 10;
280
281   bcd0 = one_digit;
282   bcd1 = ten_digit;
283   bcd2 = 4'hF;
284   bcd3 = mode;
285 end
286 endmodule

```

Program 2: RTL implementation of Exercise 1.

2.2 Testbench

The provided testbench is designed to verify the functional correctness of the FSM controls a traffic light system, as implemented in section 2.1. The testbench runs multiple scenarios to ensure the operation of the FSM in various modes and input conditions:

- Test 1 (Auto mode test): Verifies automatic cycling of light states and timers, confirming correct encoding and transitions of the 7-segment display, horizontal (`hor_led`) and vertical (`ver_led`) traffic signals based on predefined time intervals.
- Test 2 (FSM button test): Assesses manual interaction with the system through simulated button presses. This test set checks the increase and decrease of green and yellow light timings and saving/no saving scenarios, ensuring the controller updates the timer values and LED signals as expected.
- Test 3 (Reset test): Checks the system's response to a reset event. This test ensures the FSM correctly returns to its initial state and reinitializes the timer and LED outputs - both during and after the reset release.
- Test 4 (Min, Max boundary test): Verifies correct boundary handling of timer values. The system is subjected to scenarios where green and yellow timers are increased or decreased to their maximum and minimum allowable limits, ensuring no overflow or underflow occurs.

```

1 module tb;
2 reg clk;
3 reg rst_n;
4 reg [3:0] button;
5 wire [2:0] hor_led;
6 wire [2:0] ver_led;
7 wire [3:0] bcd0;
8 wire [3:0] bcd1;
9 wire [3:0] bcd2;
10 wire [3:0] bcd3;
11
12 parameter RED = 3'b100;

```

```

13 parameter YELLOW = 3'b110;
14 parameter GREEN = 3'b010;
15 parameter CLK_PERIOD = 8; // 8ns => 125MHz
16
17 integer pass, fail;
18
19 `ifdef SIMULATION
20     //for sim, debounce is 100 cycles + margin
21     parameter DB = (100 * CLK_PERIOD) + 70; // 870ns
22     //for sim, a sec is 100 clock cycles + margin
23     parameter WAIT_1S = (100 * CLK_PERIOD) * 1 + 20;
24     parameter WAIT_2S = (100 * CLK_PERIOD) * 2 + 20;
25     parameter WAIT_3S = (100 * CLK_PERIOD) * 3 + 20;
26     parameter WAIT_4S = (100 * CLK_PERIOD) * 4 + 20;
27     parameter WAIT_5S = (100 * CLK_PERIOD) * 5 + 20;
28     parameter WAIT_6S = (100 * CLK_PERIOD) * 6 + 20;
29 `else
30     parameter DB = 10_000_000; // 10ms
31     parameter WAIT_1S = 1_100_000_000;
32     parameter WAIT_2S = 2_000_000_000;
33     parameter WAIT_3S = 64'd3_000_000_000;
34     parameter WAIT_4S = 64'd4_000_000_000;
35     parameter WAIT_5S = 64'd5_000_000_000;
36     parameter WAIT_6S = 64'd6_000_000_000;
37 `endif
38
39 ex1 dut (
40     .clk (clk),
41     .rst_n (rst_n),
42     .button (button),
43     .hor_led (hor_led),
44     .ver_led (ver_led),
45     .bcd0 (bcd0),
46     .bcd1 (bcd1),
47     .bcd2 (bcd2),
48     .bcd3 (bcd3)
49 );
50
51 task divi;
52     $display ("-----");
53     -----");
54 endtask
55
56 task msg (input [700:0] txt);
57     begin
58         divi();
59         $display ("%0s", txt);
60         divi();
61     end
62 endtask
63
64 task check (input [3:0] exp_bcd3, input [3:0] exp_bcd2, input [3:0]

```

```

exp_bcd1, input [3:0] exp_bcd0, input [2:0] exp_hor_led, input
[2:0] exp_ver_led);
begin
    #10;
    $display ("[EXPECT] Time = %0t | 7SEGs = %0h%0h-%0h%0h,
        HOR_LED = %b, VER_LED = %b", $time, exp_bcd3, exp_bcd2,
        exp_bcd1, exp_bcd0, exp_hor_led, exp_ver_led);

$display ("[OUTPUT] Time = %0t | 7SEGs = %0h%0h-%0h%0h,
        HOR_LED = %b, VER_LED = %b", $time, bcd3, bcd2, bcd1, bcd0,
        hor_led, ver_led);

if ((bcd0 == exp_bcd0) && (bcd1 == exp_bcd1) && (bcd2 ==
    exp_bcd2) && (bcd3 == exp_bcd3) && (hor_led == exp_hor_led)
    && (ver_led == exp_ver_led)) begin
    $display ("=====> PASSED");
    pass = pass + 1;
end else begin
    $display ("=====> FAILED");
    fail = fail + 1;
end
end
endtask

task incr;
begin
    button = 4'b0010;
    #(DB);
    button = 4'b0000;
    #(DB);
end
endtask

task decr;
begin
    button = 4'b0100;
    #(DB);
    button = 4'b0000;
    #(DB);
end
endtask

task save;
begin
    button = 4'b1000;
    #(DB);
    button = 4'b0000;
    #(DB);
end
endtask

task mode;
begin

```

```

110         button = 4'b0001;
111         #(DB);
112         button = 4'b0000;
113         #(DB);
114     end
115 endtask
116
117 initial begin
118     clk = 0;
119     forever #4 clk = ~clk;
120 end
121 //F = 125MHz clock -> T = 8ns period
122
123 initial begin
124     $dumpfile ("tb.vcd");
125     $dumpvars (0, tb);
126
127     rst_n = 1'b0;
128     button = 4'b0000;
129     pass = 0;
130     fail = 0;
131     #100;
132     rst_n = 1'b1;
133     #100;
134
135     msg ("TEST 1: FSM AUTO MODE TEST");
136     #(WAIT_1S);
137     check (4'd1, 4'd15, 4'd0, 4'd3, RED, GREEN);
138
139     #(WAIT_3S);
140     check (4'd1, 4'd15, 4'd0, 4'd2, RED, YELLOW);
141
142     #(WAIT_2S);
143     check (4'd1, 4'd15, 4'd0, 4'd3, GREEN, RED);
144
145     #(WAIT_3S);
146     check (4'd1, 4'd15, 4'd0, 4'd2, YELLOW, RED);
147
148     #(WAIT_2S);
149     check (4'd1, 4'd15, 4'd0, 4'd3, RED, GREEN);
150
151     msg ("TEST 2: FSM BUTTON TEST");
152     msg ("\t1. Increase green 3 times, increase yellow 3 times, then
153           save");
154     //green
155     mode();
156     repeat (3) incr();
157     check (4'd2, 4'd15, 4'd0, 3'd6, GREEN, GREEN);
158     save();
159     //yellow
160     mode();
161     repeat (3) incr();
162     check (4'd3, 4'd15, 4'd0, 4'd5, YELLOW, YELLOW);

```

```

162     save();
163     mode();
164
165     #(WAIT_2S);
166     check (4'd1, 4'd15, 4'd0, 4'd4, RED, GREEN);
167     #(WAIT_6S);
168     check (4'd1, 4'd15, 4'd0, 4'd3, RED, YELLOW);
169
170     msg ("\t2. Decrease green 2 times, decrease yellow 1 time, then
171           save");
172     //green
173     mode();
174     repeat (2) decr();
175     check (4'd2, 4'd15, 4'd0, 3'd4, GREEN, GREEN);
176     save();
177     //yellow
178     mode();
179     decr();
180     check (4'd3, 4'd15, 4'd0, 4'd4, YELLOW, YELLOW);
181     save();
182     mode();
183
184     #(WAIT_1S);
185     check (4'd1, 4'd15, 4'd0, 4'd3, RED, GREEN);
186     #(WAIT_3S);
187     check (4'd1, 4'd15, 4'd0, 4'd4, RED, YELLOW);
188
189     msg ("\t3. Increase green 1 time, decrease yellow 1 time, then no
190           save");
191     //green
192     mode();
193     incr();
194     check (4'd2, 4'd15, 4'd0, 3'd5, GREEN, GREEN);
195     //yellow
196     mode();
197     decr();
198     check (4'd3, 4'd15, 4'd0, 4'd3, YELLOW, YELLOW);
199     mode();
200
201     #(WAIT_2S);
202     check (4'd1, 4'd15, 4'd0, 4'd2, RED, GREEN);
203     #(WAIT_4S);
204     check (4'd1, 4'd15, 4'd0, 4'd2, RED, YELLOW);
205
206     msg ("\t4. Increase green 1 time, decrease yellow 1 time, then
207           save");
208     //green
209     mode();
210     incr();
211     check (4'd2, 4'd15, 4'd0, 3'd5, GREEN, GREEN);

```

```

212     decr();
213     check (4'd3, 4'd15, 4'd0, 4'd3, YELLOW, YELLOW);
214     save();
215     mode();
216
217     #(WAIT_2S);
218     check (4'd1, 4'd15, 4'd0, 4'd3, RED, GREEN);
219     #(WAIT_4S);
220     check (4'd1, 4'd15, 4'd0, 4'd2, RED, YELLOW);
221
222     msg ("TEST 3: RESET TEST");
223     mode();
224     check (4'd2, 4'd15, 4'd0, 4'd5, GREEN, GREEN);
225     $display ("Resetting...");
226     rst_n = 1'b0;
227     #(WAIT_2S);
228     check (4'd1, 4'd15, 4'd0, 4'd0, RED, RED);
229
230     mode();
231     check (4'd1, 4'd15, 4'd0, 4'd0, RED, RED);
232
233     mode();
234     check (4'd1, 4'd15, 4'd0, 4'd0, RED, RED);
235
236     $display ("Releasing reset...");
237     rst_n = 1'b1;
238     #800;
239     #(WAIT_1S);
240     check (4'd1, 4'd15, 4'd0, 4'd4, RED, GREEN);
241     #(WAIT_5S);
242     check (4'd1, 4'd15, 4'd0, 4'd2, RED, YELLOW);
243
244     msg ("TEST 4: MIN, MAX BOUNDARY TEST");
245     msg ("\t1. Increase green 94 times, increase yellow 17 times to
246           reach max");
247     //green
248     mode();
249     repeat (94) incr();
250     check (4'd2, 4'd15, 4'd9, 4'd9, GREEN, GREEN);
251     save();
252     //yellow
253     mode();
254     repeat (17) incr();
255     check (4'd3, 4'd15, 4'd2, 4'd0, YELLOW, YELLOW);
256     save();
257     mode();
258
259     msg ("\t 2. Increase green 3 times, increase yellow 5 times");
260     //green
261     mode();
262     repeat (3) incr();
263     check (4'd2, 4'd15, 4'd9, 4'd9, GREEN, GREEN);
264     save();

```

```

264 //yellow
265 mode();
266 repeat (5) incr();
267 check (4'd3, 4'd15, 4'd2, 4'd0, YELLOW, YELLOW);
268 save();
269 mode();
270
271 msg ("\t 3. Decrease green 97 times, decrease yellow 19 times to
      reach min");
272 //green
273 mode();
274 repeat (97) decr();
275 check (4'd2, 4'd15, 4'd0, 4'd2, GREEN, GREEN);
276 save();
277 //yellow
278 mode();
279 repeat (19) decr();
280 check (4'd3, 4'd15, 4'd0, 4'd1, YELLOW, YELLOW);
281 save();
282 mode();
283
284 msg ("\t 4. Decrease green 8 times, decrease yellow 3 times");
285 //green
286 mode();
287 repeat (8) decr();
288 check (4'd2, 4'd15, 4'd0, 4'd2, GREEN, GREEN);
289 save();
290 //yellow
291 mode();
292 repeat (3) decr();
293 check (4'd3, 4'd15, 4'd0, 4'd1, YELLOW, YELLOW);
294 save();
295 mode();
296
297 #100;
298 msg ("SUMMARY");
299 $display ("TOTAL TESTS : %0d", pass + fail);
300 $display ("TOTAL PASSED: %0d", pass);
301 $display ("TOTAL FAILED: %0d", fail);
302 if (fail == 0)
303     $display ("===== > ALL TESTS PASSED");
304 else if (pass == 0)
305     $display ("===== > ALL TESTS FAILED");
306 else
307     $display ("===== > SOME TESTS FAILED");
308 #100;
309 $finish;
310 end
311 endmodule

```

Program 3: Testbench implementation of Exercise 1.

2.3 Testbench results

All test cases executed successfully, with each marked as PASSED. This outcome confirms that the test module behaves as intended and that the implemented RTL design meets the expected functionality.

```
1 # -----
2 # TEST 1: FSM AUTO MODE TEST
3 #
4 # [EXPECT] Time = 1030 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
5 # [OUTPUT] Time = 1030 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
6 # =====> PASSED
7 # [EXPECT] Time = 3460 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
8 # [OUTPUT] Time = 3460 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
9 # =====> PASSED
10 # [EXPECT] Time = 5090 | 7SEGs = 1f-03, HOR_LED = 010, VER_LED = 100
11 # [OUTPUT] Time = 5090 | 7SEGs = 1f-03, HOR_LED = 010, VER_LED = 100
12 # =====> PASSED
13 # [EXPECT] Time = 7520 | 7SEGs = 1f-02, HOR_LED = 110, VER_LED = 100
14 # [OUTPUT] Time = 7520 | 7SEGs = 1f-02, HOR_LED = 110, VER_LED = 100
15 # =====> PASSED
16 # [EXPECT] Time = 9150 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
17 # [OUTPUT] Time = 9150 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
18 # =====> PASSED
19 #
20 # -----
21 # TEST 2: FSM BUTTON TEST
22 #
23 #
24 # 1. Increase green 3 times, increase yellow 3 times, then save
25 #
26 # [EXPECT] Time = 16120 | 7SEGs = 2f-06, HOR_LED = 010, VER_LED = 010
27 # [OUTPUT] Time = 16120 | 7SEGs = 2f-06, HOR_LED = 010, VER_LED = 010
28 # =====> PASSED
29 # [EXPECT] Time = 24830 | 7SEGs = 3f-05, HOR_LED = 110, VER_LED = 110
30 # [OUTPUT] Time = 24830 | 7SEGs = 3f-05, HOR_LED = 110, VER_LED = 110
31 # =====> PASSED
32 # [EXPECT] Time = 29940 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 010
33 # [OUTPUT] Time = 29940 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 010
34 # =====> PASSED
35 # [EXPECT] Time = 34770 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 110
36 # [OUTPUT] Time = 34770 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 110
37 # =====> PASSED
38 #
39 # 2. Decrease green 2 times, decrease yellow 1 time, then save
40 #
41 # [EXPECT] Time = 40000 | 7SEGs = 2f-04, HOR_LED = 010, VER_LED = 010
42 # [OUTPUT] Time = 40000 | 7SEGs = 2f-04, HOR_LED = 010, VER_LED = 010
43 # =====> PASSED
44 # [EXPECT] Time = 45230 | 7SEGs = 3f-04, HOR_LED = 110, VER_LED = 110
45 # [OUTPUT] Time = 45230 | 7SEGs = 3f-04, HOR_LED = 110, VER_LED = 110
46 # =====> PASSED
47 # [EXPECT] Time = 49540 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
48 # [OUTPUT] Time = 49540 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
# =====> PASSED
```

```

49 # [EXPECT] Time = 51970 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 110
50 # [OUTPUT] Time = 51970 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 110
51 # =====> PASSED
52 #
53 # -----
54 #   3. Increase green 1 time, decrease yellow 1 time, then no save
55 # -----
56 # [EXPECT] Time = 55460 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
57 # [OUTPUT] Time = 55460 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
58 # =====> PASSED
59 # [EXPECT] Time = 58950 | 7SEGs = 3f-03, HOR_LED = 110, VER_LED = 110
60 # [OUTPUT] Time = 58950 | 7SEGs = 3f-03, HOR_LED = 110, VER_LED = 110
61 # =====> PASSED
62 # [EXPECT] Time = 62320 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 010
63 # [OUTPUT] Time = 62320 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 010
64 # =====> PASSED
65 # [EXPECT] Time = 65550 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
66 # [OUTPUT] Time = 65550 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
67 # =====> PASSED
68 #
69 # -----
70 #   4. Increase green 1 time, decrease yellow 1 time, then save
71 # -----
72 # [EXPECT] Time = 69040 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
73 # [OUTPUT] Time = 69040 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
74 # =====> PASSED
75 # [EXPECT] Time = 74270 | 7SEGs = 3f-03, HOR_LED = 110, VER_LED = 110
76 # [OUTPUT] Time = 74270 | 7SEGs = 3f-03, HOR_LED = 110, VER_LED = 110
77 # =====> PASSED
78 # [EXPECT] Time = 79380 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
79 # [OUTPUT] Time = 79380 | 7SEGs = 1f-03, HOR_LED = 100, VER_LED = 010
80 # =====> PASSED
81 # [EXPECT] Time = 82610 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
82 # [OUTPUT] Time = 82610 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
83 # =====> PASSED
84 #
85 # TEST 3: RESET TEST
86 #
87 # -----
88 # [EXPECT] Time = 84360 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
89 # [OUTPUT] Time = 84360 | 7SEGs = 2f-05, HOR_LED = 010, VER_LED = 010
90 # =====> PASSED
91 # Resetting...
92 # [EXPECT] Time = 85990 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
93 # [OUTPUT] Time = 85990 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
94 # =====> PASSED
95 # [EXPECT] Time = 87740 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
96 # [OUTPUT] Time = 87740 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
97 # =====> PASSED
98 # [EXPECT] Time = 89490 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
99 # [OUTPUT] Time = 89490 | 7SEGs = 1f-00, HOR_LED = 100, VER_LED = 100
100 # =====> PASSED
101 # Releasing reset...
102 # [EXPECT] Time = 91120 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 010
103 # [OUTPUT] Time = 91120 | 7SEGs = 1f-04, HOR_LED = 100, VER_LED = 010
104 # =====> PASSED

```

```

102 # [EXPECT] Time = 95150 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
103 # [OUTPUT] Time = 95150 | 7SEGs = 1f-02, HOR_LED = 100, VER_LED = 110
104 # =====> PASSED
105 #
106 # -----
107 # TEST 4: MIN, MAX BOUNDARY TEST
108 #
109 #
110 # 1. Increase green 94 times, increase yellow 17 times to reach max
111 #
112 # -----
113 # [EXPECT] Time = 260460 | 7SEGs = 2f-99, HOR_LED = 010, VER_LED = 010
114 # [OUTPUT] Time = 260460 | 7SEGs = 2f-99, HOR_LED = 010, VER_LED = 010
115 # =====> PASSED
116 # [EXPECT] Time = 293530 | 7SEGs = 3f-20, HOR_LED = 110, VER_LED = 110
117 # [OUTPUT] Time = 293530 | 7SEGs = 3f-20, HOR_LED = 110, VER_LED = 110
118 # =====> PASSED
119 #
120 # 2. Increase green 3 times, increase yellow 5 times
121 #
122 # -----
123 # [EXPECT] Time = 303980 | 7SEGs = 2f-99, HOR_LED = 010, VER_LED = 010
124 # [OUTPUT] Time = 303980 | 7SEGs = 2f-99, HOR_LED = 010, VER_LED = 010
125 # =====> PASSED
126 # -----
127 # 3. Decrease green 97 times, decrease yellow 19 times to reach min
128 #
129 # -----
130 # [EXPECT] Time = 490180 | 7SEGs = 2f-02, HOR_LED = 010, VER_LED = 010
131 # [OUTPUT] Time = 490180 | 7SEGs = 2f-02, HOR_LED = 010, VER_LED = 010
132 # =====> PASSED
133 # [EXPECT] Time = 526730 | 7SEGs = 3f-01, HOR_LED = 110, VER_LED = 110
134 # [OUTPUT] Time = 526730 | 7SEGs = 3f-01, HOR_LED = 110, VER_LED = 110
135 # =====> PASSED
136 # -----
137 # 4. Decrease green 8 times, decrease yellow 3 times
138 #
139 # -----
140 # [EXPECT] Time = 545880 | 7SEGs = 2f-02, HOR_LED = 010, VER_LED = 010
141 # [OUTPUT] Time = 545880 | 7SEGs = 2f-02, HOR_LED = 010, VER_LED = 010
142 # =====> PASSED
143 # [EXPECT] Time = 554590 | 7SEGs = 3f-01, HOR_LED = 110, VER_LED = 110
144 # [OUTPUT] Time = 554590 | 7SEGs = 3f-01, HOR_LED = 110, VER_LED = 110
145 # =====> PASSED
146 #
147 # -----
148 # SUMMARY
149 #
150 # -----
151 # TOTAL TESTS : 35
152 # TOTAL PASSED: 35
153 # TOTAL FAILED: 0
154 # =====> ALL TESTS PASSED
155 # ** Note: $finish : ../tb/tb.v(308)
156 #     Time: 558270 ns Iteration: 0 Instance: /tb

```

Simulation 1: Testbench results of Exercise 1.

2.4 Simulation waveform

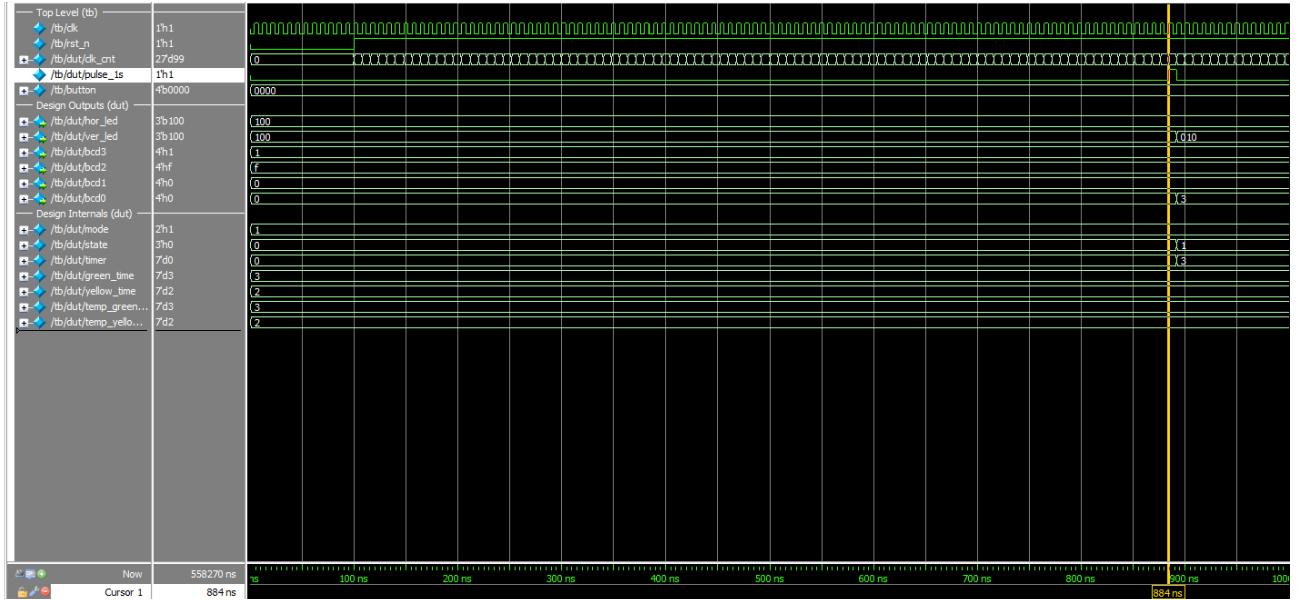


Figure 1.1

In the simulation, one second corresponds to 100 clock cycles, and the debounce interval is set to 10 cycles for easier observation compared to the actual FPGA values.

Figure 1.1 illustrates the behavior when the reset signal is asserted and then deasserted, so both the horizontal and vertical LEDs are initialized to their default state, showing red.

After 100 clock cycles, tracked by the `clk_cnt` signal, a pulse is generated to represent the one-second duration. At 884 ns, the `pulse_1s` signal is asserted for a single clock cycle and then deasserted in the following cycle.

On the next cycle after `pulse_1s` is asserted, the traffic light controller begins operation. The initial state sets the horizontal LED to red and the vertical LED to green, marking the start of the traffic light sequence.

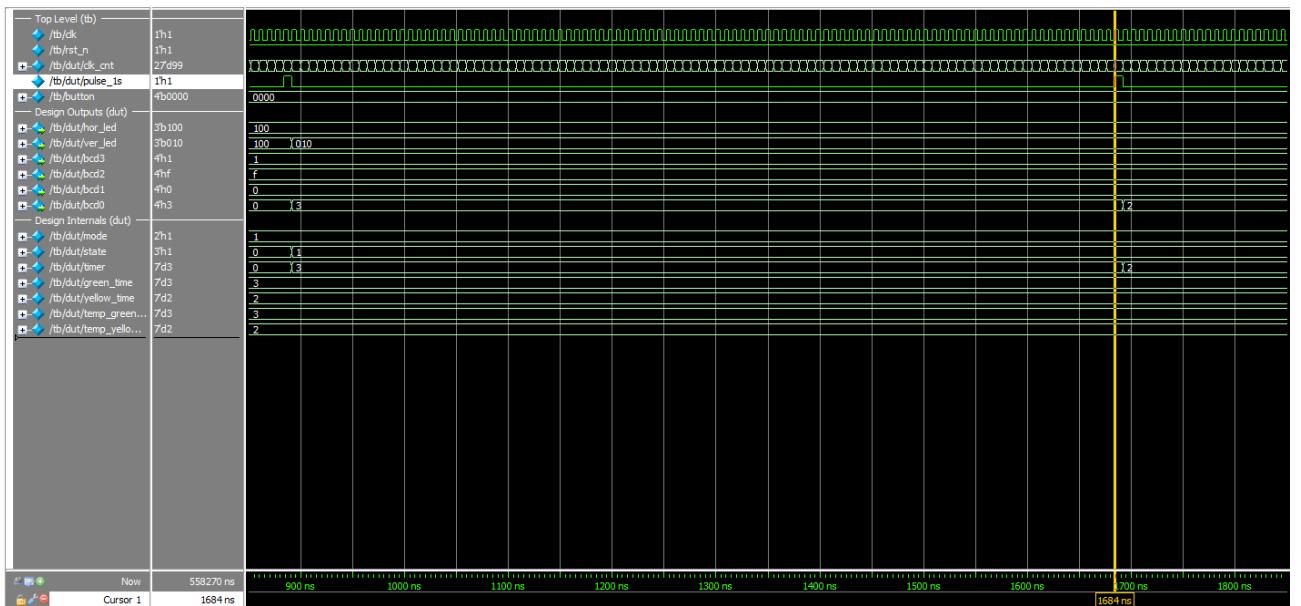


Figure 1.2

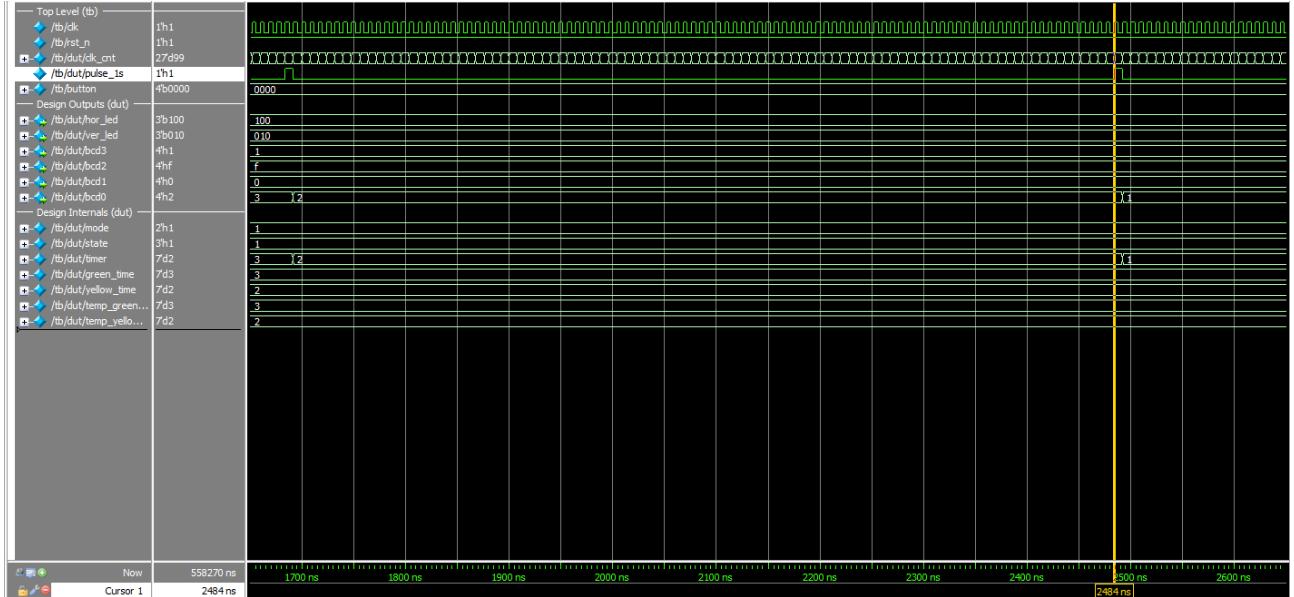


Figure 1.3

The `pulse_1s` signal indicates that one second has elapsed. The duration of the red LED is defined as the sum of the green and yellow LED intervals. For easier timing analysis, this module tracks only the durations of the green and yellow LEDs.

Every 100 clock cycles, the `pulse_1s` signal is asserted, and on the following cycle, the traffic lights are updated.

As shown in Figure 1.2, at 1684 ns, the horizontal traffic light remains red, while the vertical traffic light updates its green LED countdown from 3 seconds to 2 seconds.

In Figure 1.3, at 2484 ns, another `pulse_1s` event occurs, marking the passage of one second. This triggers the vertical traffic light to update again, reducing the green LED countdown from 2 seconds to 1 second.

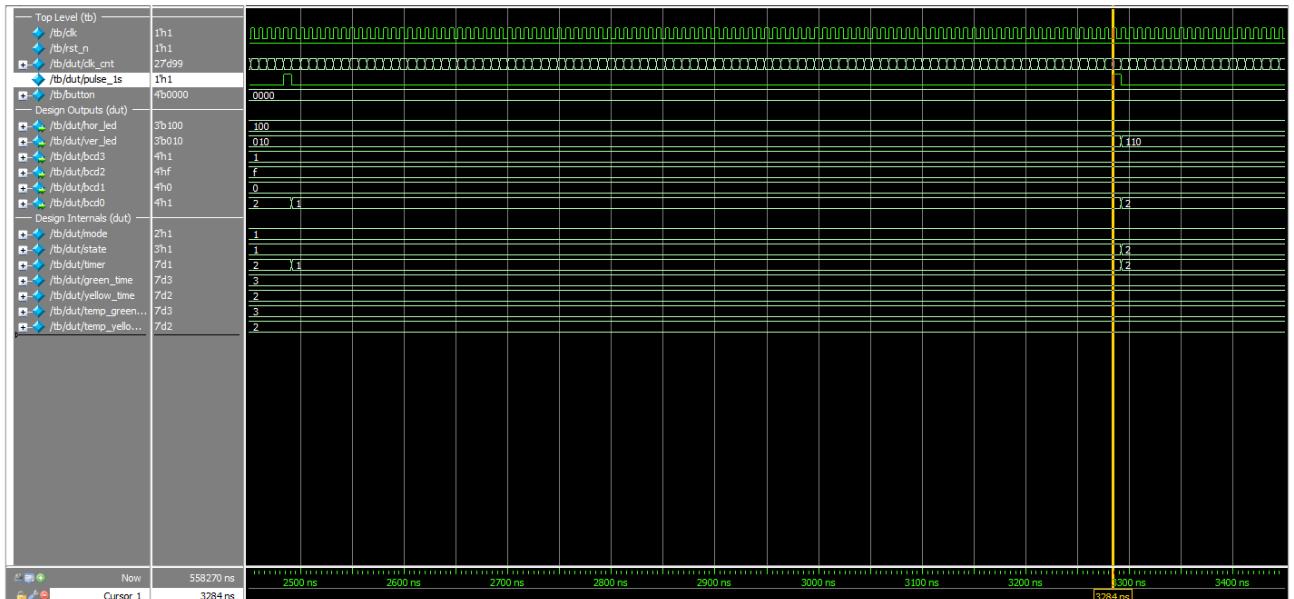


Figure 1.4

In Figure 1.4, another second has elapsed, completing the 3-second countdown for the vertical traffic light's green LED. Consequently, at the next clock cycle after `pulse_1s` is asserted at 3284 ns, the vertical traffic light transitions to the yellow LED, which has a 2-second duration. This demonstrates how both traffic lights automatically update their states. The behavior can

be observed more clearly in Test 1 of the test bench, where the system waits for one LED countdown to finish and then verifies that both traffic lights update accordingly.

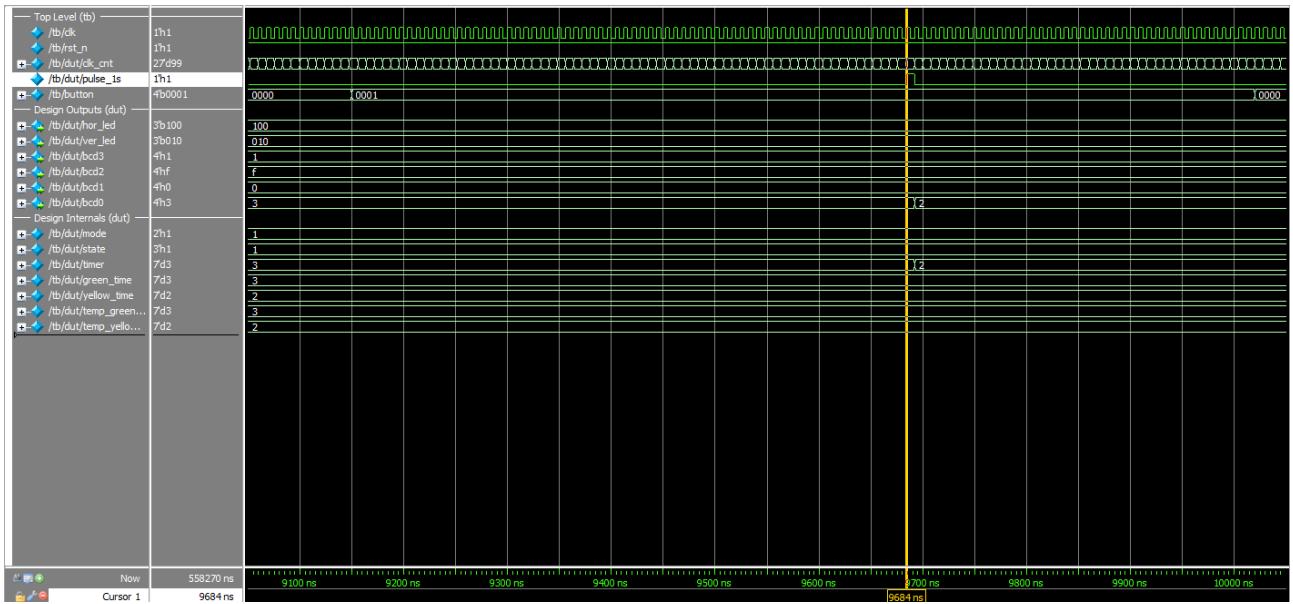


Figure 1.5

Figure 1.5 illustrates the conclusion of the auto mode test, during which no buttons are pressed. When Button 0 is activated (represented by the `button` signal), the system transitions out of auto mode.

Once the `button[0]` signal is asserted (Figure 1.5), then deasserted (Figure 1.6), the `bcd3` signal updates to a value of 2, indicating a switch to Mode 2. In this mode, the duration of the green LEDs for the traffic lights can be modified and both the horizontal and vertical LEDs turn green, confirming that Mode 2 is active.

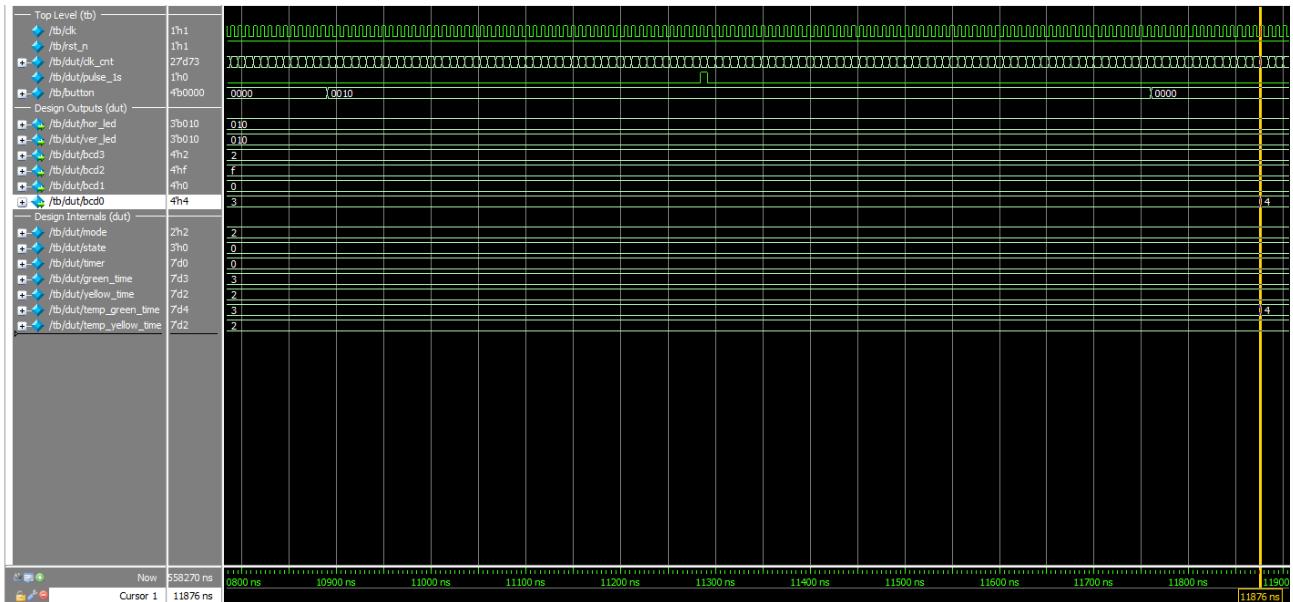


Figure 1.6

Figure 1.6 also shows that Button 1 is pressed, which functions as the increment control for the green LED duration. After the button is released and the debounce interval has passed, the `bcd0` and `temp_green_time` signals update to a value of 4. This confirms that the 7-segment LED display correctly reflects the button input.

Since Button 3 (the save function) has not yet been pressed, the `green_time` signal retains its previous value, meaning the updated duration for the green LEDs has not been stored.

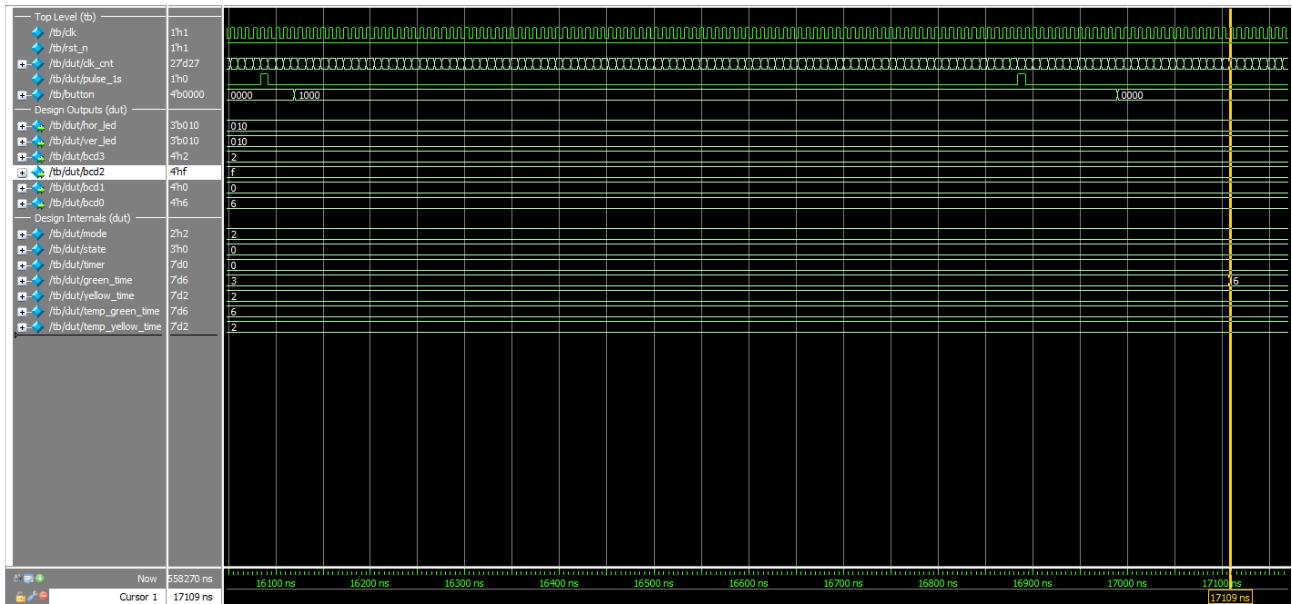


Figure 1.7

After pressing Button 1 three times, the green LED countdown reaches 6 seconds. To save this value, Button 3 is pressed.

As shown, once Button 3 is pressed and released - after the debounce interval - the `green_time` signal updates to 6, confirming that the green LEDs have been successfully reconfigured to count down for 6 seconds.

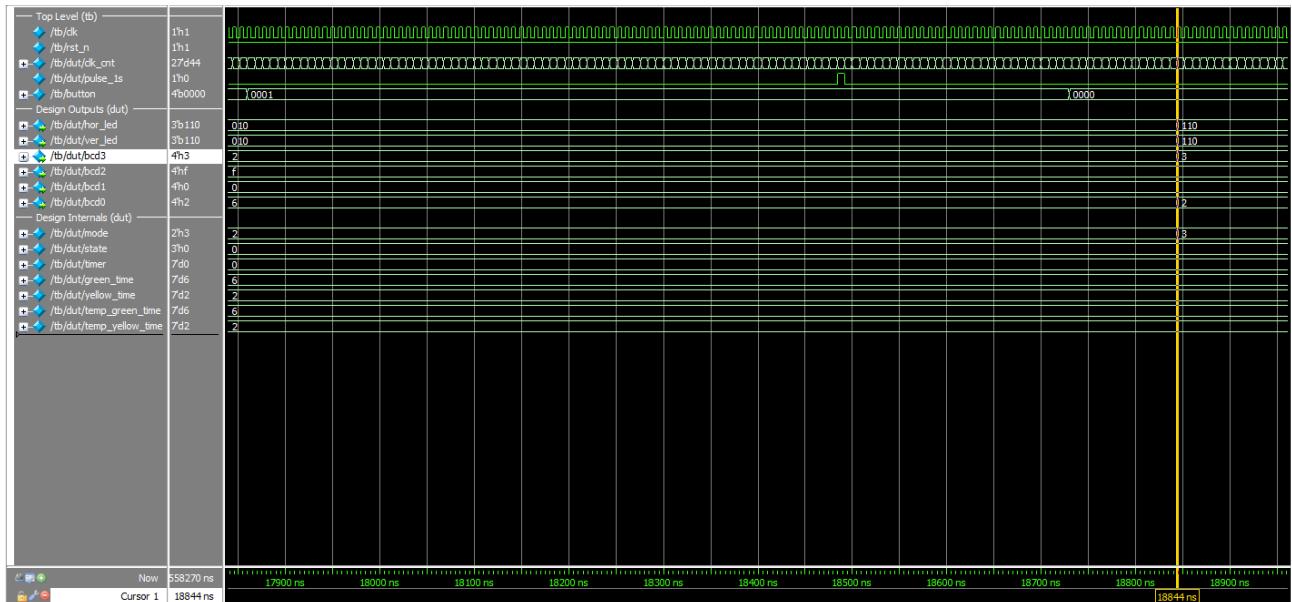


Figure 1.8

Figure 1.8 illustrates the action of pressing Button 0, which triggers the FSM to switch to Mode 3. In this mode, both the vertical and horizontal LEDs turn yellow, confirming that the system has successfully transitioned to Mode 3.

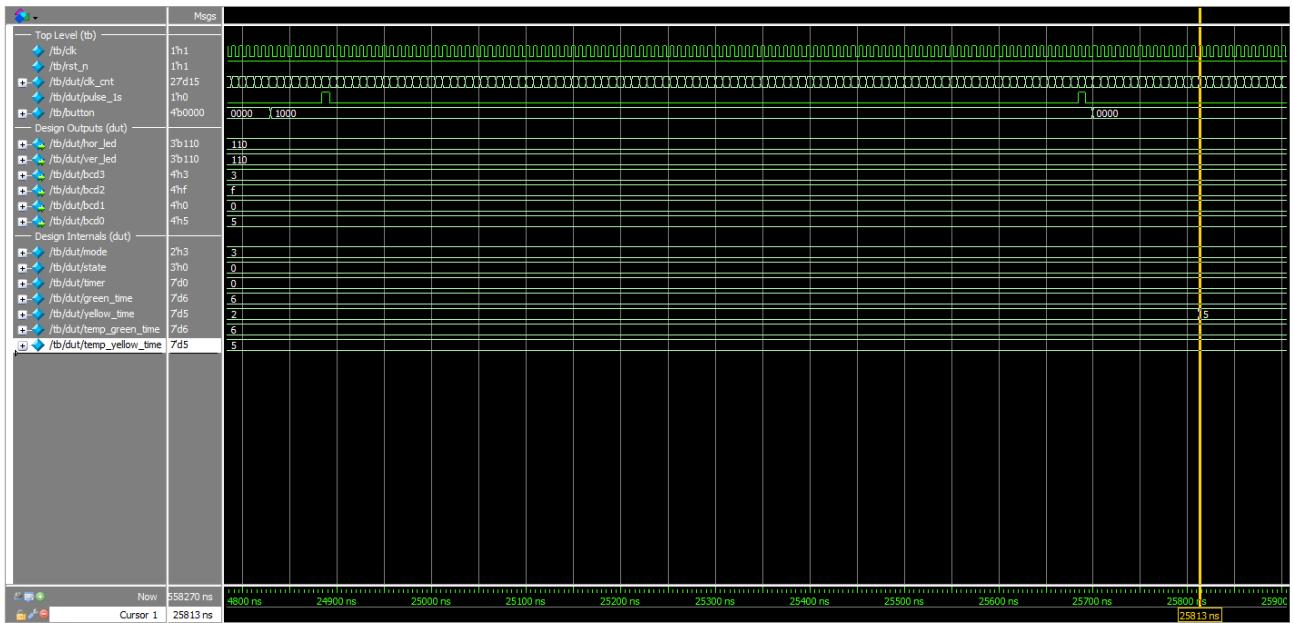


Figure 1.9

Figure 1.9 illustrates that the user has temporarily configured the yellow LED duration, increasing it from 2 seconds to 5 seconds through the `temp_yellow_time` signal. When Button 3 is pressed, the updated value is saved, and the `yellow_time` signal is set to 5, confirming that the yellow LEDs have been successfully reconfigured to a 5-second duration.

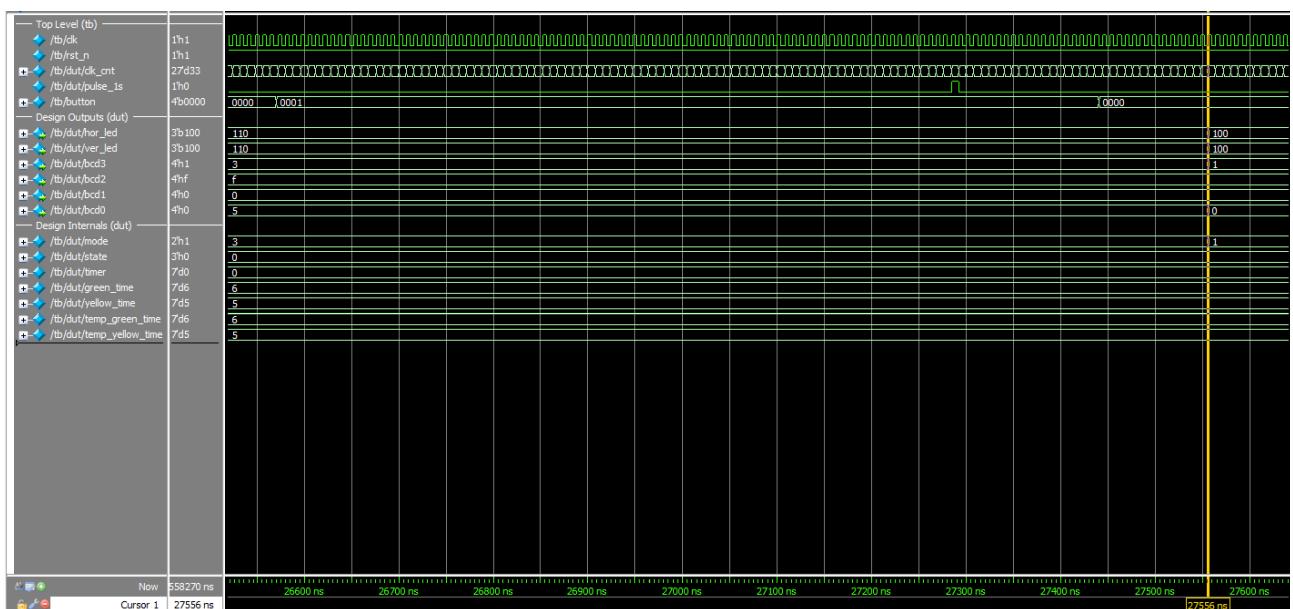


Figure 1.10

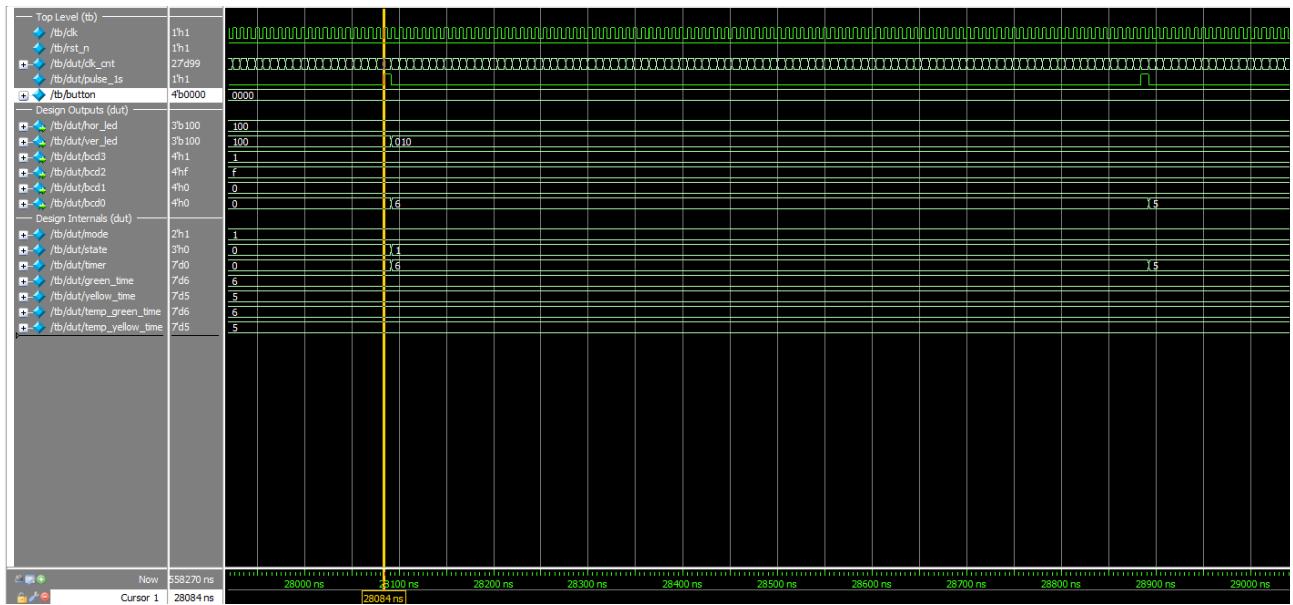


Figure 1.11

Figures 1.10 and 1.11 illustrate the system returning to running mode after Button 0 is pressed. At this point, the 7-segment display and LEDs reset to their initial state, with both directions showing red LEDs and the countdown timer set to 0.

When the next `pulse_1s` signal is asserted, the traffic lights resume normal operation using the newly configured values. The green light now runs with a 6-second duration, replacing the previous 3-second interval.

Upon the following `pulse_1s` assertion, the countdown successfully decreases to 5 seconds, confirming that the configuration has been saved and that the traffic lights operate correctly with the updated timing.

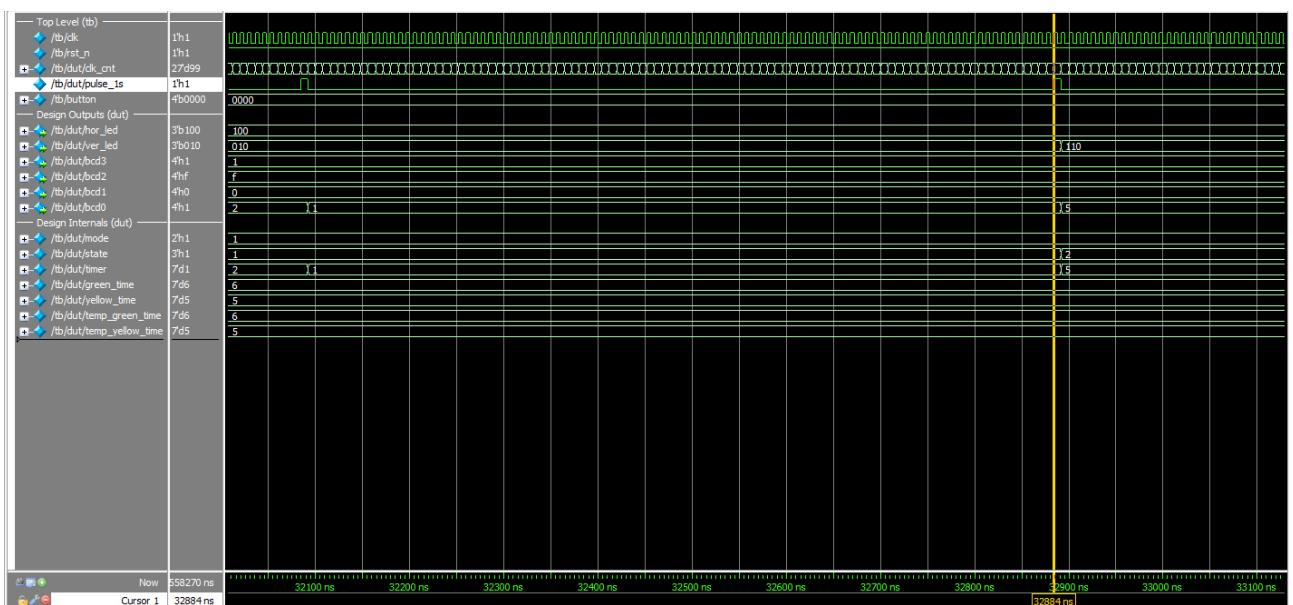


Figure 1.12

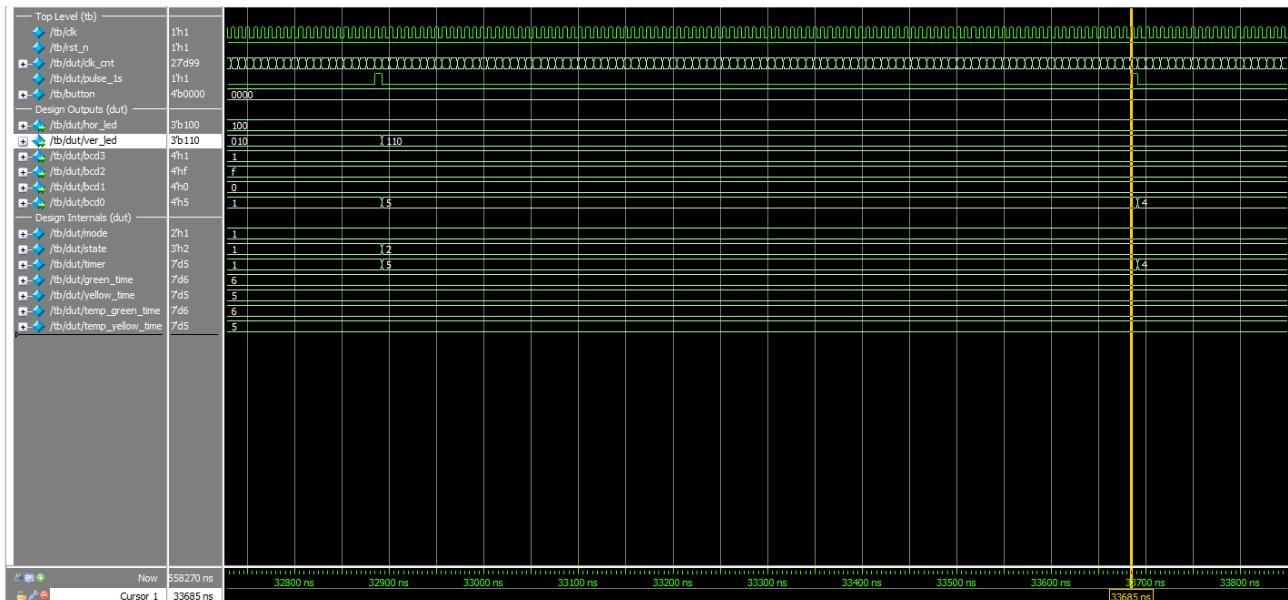


Figure 1.13

We now skip to the point where the vertical green LED finishes its countdown and transitions to the yellow LED, in order to verify whether the updated value has been applied.

Figure 1.12 shows that after the green LED counts down to 1 second, another `pulse_1s` is asserted, switching the vertical light to the yellow LED with a duration of 5 seconds, as indicated by the `timer` signal.

In Figure 1.13, when one second elapses (signaled by a high `pulse_1s`), the timer updates to 4 seconds. This confirms that both the green LED duration and the yellow LED duration have been successfully updated through button presses, and the traffic lights continue to operate correctly with the new values.

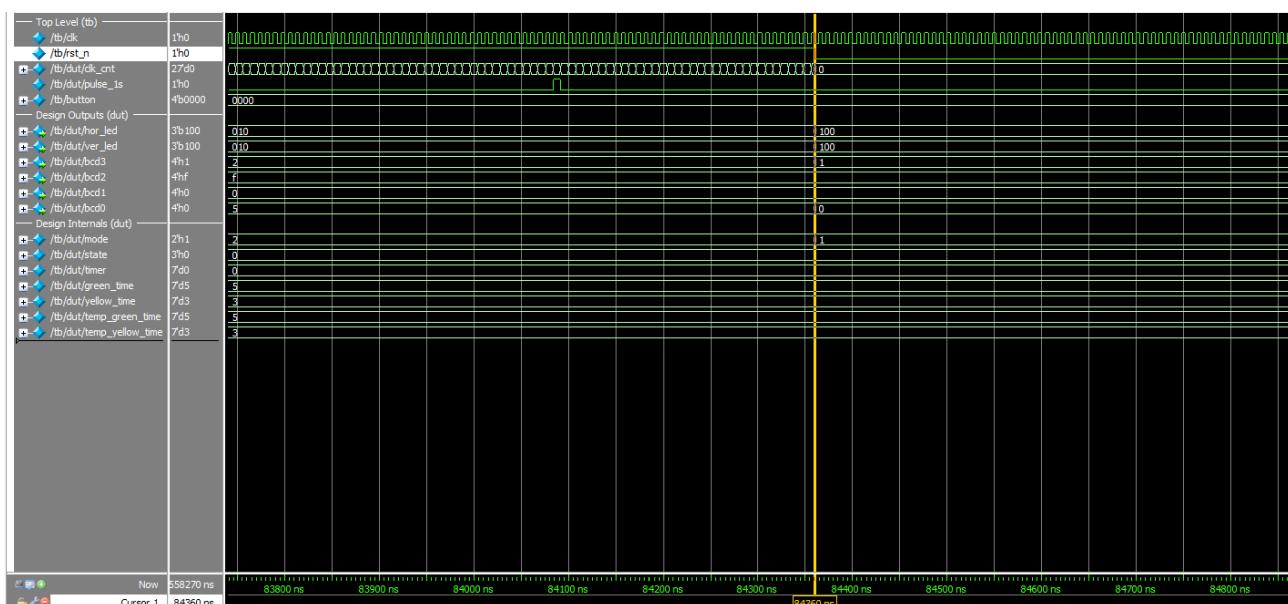


Figure 1.14

Since the design uses an asynchronous active-low reset, asserting the reset immediately forces both the vertical and horizontal LEDs to red. At the same time, the 7-segment display is updated to Mode 1, with the countdown value set to 0, as indicated by the signals `bcd3`, `bcd2`, `bcd1`, and `bcd0`.

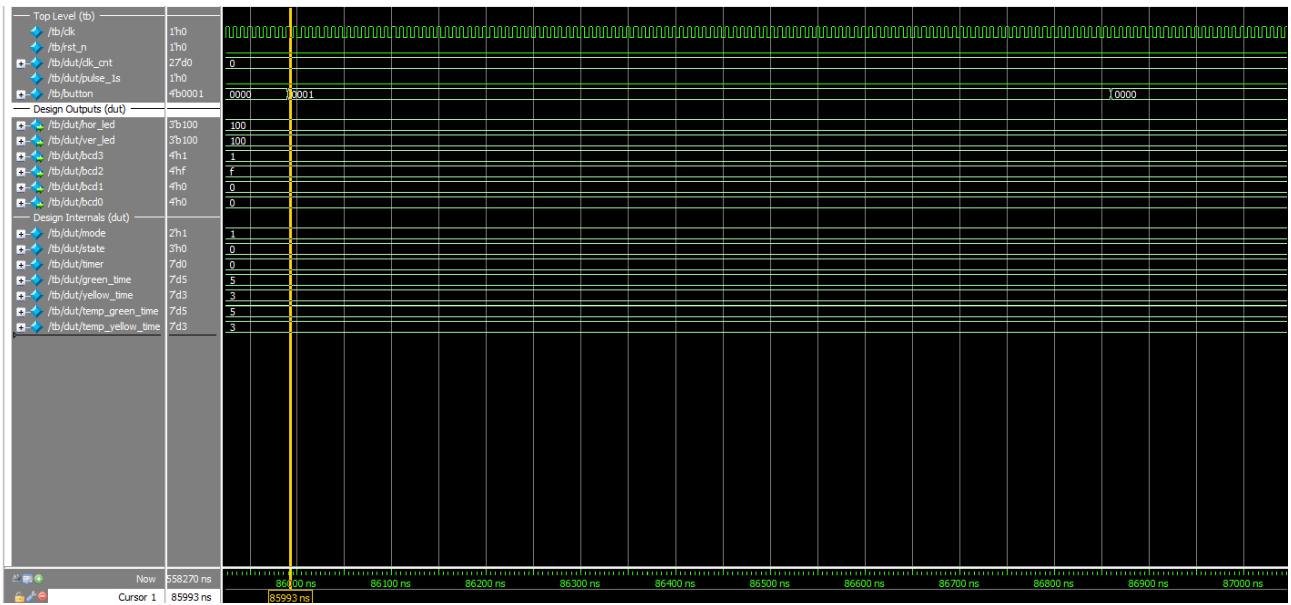


Figure 1.15

By observing Figure 1.15, we can see that pressing Button 1 has no effect while the reset signal is active. This confirms that the reset mechanism is functioning correctly.

The behavior is demonstrated more clearly in Test 3 of the test bench module, which specifically verifies the reset functionality.

2.5 FPGA results

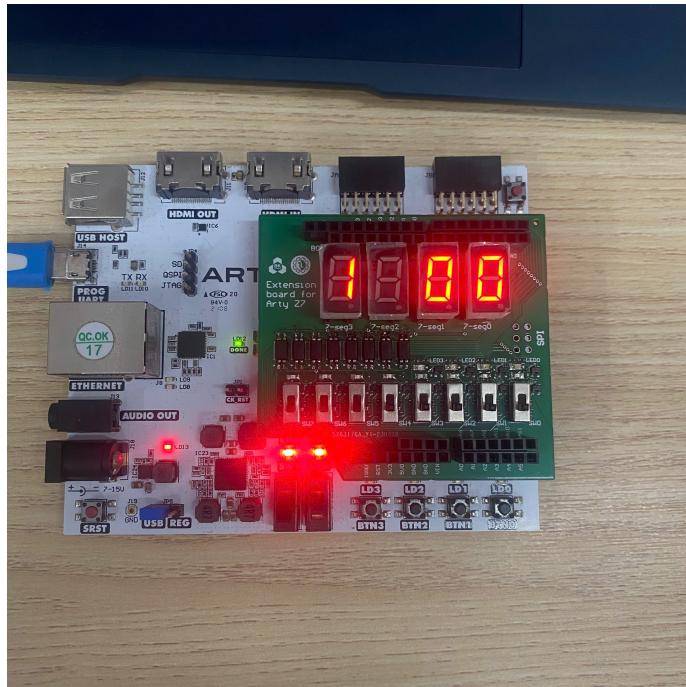


Figure 1.16

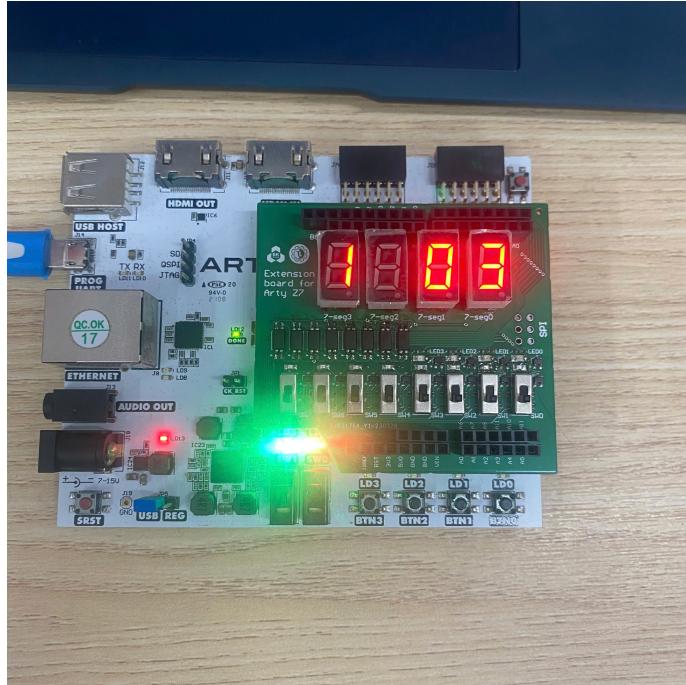


Figure 1.17

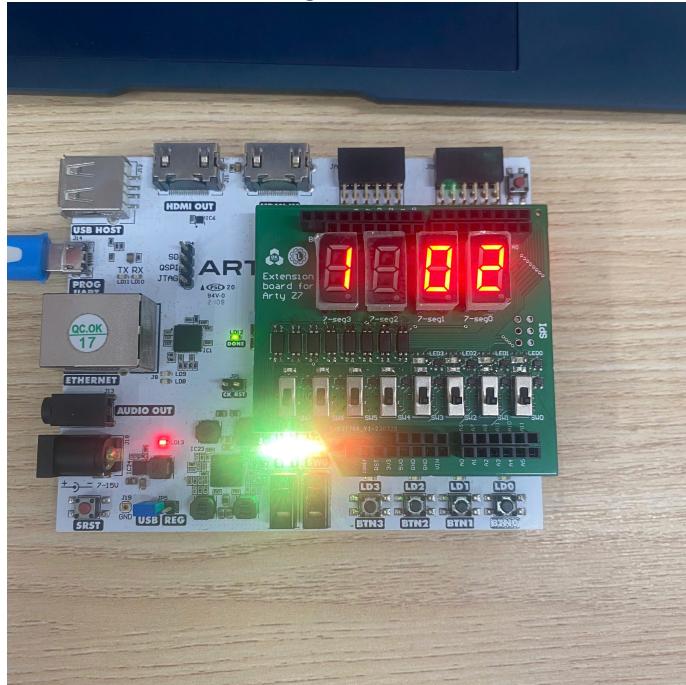


Figure 1.18

The three picture illustrates a part of the FPGA implementation results. Figure 1.16 shows the initial states when reset is on. Figure 1.17 shows the first run state where horizontal LED is red and vertical LED is green. The two leftmost 7-segment LEDs show number 1 meaning Mode 1 is on while the two rightmost 7-segment LEDs shows number 3 in Figure 1.17 meaning it start to count down at second 3 based on vertical green LED. Figure 1.18 shows what happen 1 seconds later, where the two rightmost 7-segment LEDs show number 2 meaning the FPGA has counted down successfully.

3 Exercise 2

3.1 RTL implementation

This module implements a digital display controller with LED indicators and 4-digit BCD outputs that scroll or bounce a numeric pattern across a physical 7-segment display. The system support two display effects:

- Effect 1: The 7-segment LEDs display the numeric “25” scrolling from left to right repeatedly. During this mode, a LED indicator will show red color to notify the user effect 1 is on.
- Effect 2: The 7-segment LEDs display the numeric “25”. When the test reach the right edge, it will shift left; on the other hand, when the test reaches the left edge, it will shift right. During this mode, a LED indicator will show green color to notify the user effect 2 is on.

A switch is used as a reset for the system. Once the switch is activated, the 7-segment LEDs display always present the text ”25” on the leftmost side. Another switch is used to set effect, when the switch is off, the system runs with effect 1, when the switch is on, it changes to effect 2. The switch manipulates the effect will not be affected by the reset switch. When user configures the system to run with effect 2 then turn on the reset switch, the LED indicator still shows green color, as for indicating when the reset is released the system will run with effect 2 from the start. When the text is displaying, switching effect will only affects how the text behaves, not reset the text to initial state then run in the activated effect.

```
1 module ex2 (
2     input wire clk,
3     input wire rst_n,
4     input wire sw,
5     output reg [2:0] led,
6     output reg [15:0] bcd
7 );
8
9 'ifdef SIMULATION
10    //for sim, a sec is 100 cycles
11    parameter CLK_FREQ = 27'd100;
12 'else
13    //for fpga, a sec is 125m cycles
14    parameter CLK_FREQ = 27'd125_000_000;
15 'endif
16
17 parameter SHIFT_FREQ = 2;
18 parameter DIV_COUNT = CLK_FREQ / SHIFT_FREQ;
19
20 parameter RED = 3'b100;
21 parameter GREEN = 3'b010;
22
23 parameter BCD_2 = 4'd2;
24 parameter BCD_5 = 4'd5;
25 parameter BCD_BLANK = 4'hF;
26 parameter ALL_BLANK = 16'hFFFF;
27
```

```

28 parameter S0 = {BCD_2, BCD_5, BCD_BLANK, BCD_BLANK}; // "25__"
29 parameter S1 = {BCD_BLANK, BCD_2, BCD_5, BCD_BLANK}; // "__25"
30 parameter S2 = {BCD_BLANK, BCD_BLANK, BCD_2, BCD_5}; // "__25"
31 parameter S3 = {BCD_5, BCD_BLANK, BCD_BLANK, BCD_2}; // "5__2"
32
33 reg [26:0] clk_cnt;
34 wire tick;
35 reg [1:0] state;
36 reg direction; //0: left to right, 1: right to left
37
38 assign tick = (clk_cnt == DIV_COUNT - 1);
39
40 always @(posedge clk or negedge rst_n) begin
41     if (!rst_n)
42         clk_cnt <= 27'd0;
43     else if (tick)
44         clk_cnt <= 27'd0;
45     else
46         clk_cnt <= clk_cnt + 1;
47 end
48
49 always @(posedge clk or negedge rst_n) begin
50     if (!rst_n) begin
51         state <= 0;
52         direction <= 0;
53     end else if (tick) begin
54         //scroll
55         if (sw == 0) begin
56             if (state == 2'd3)
57                 state <= 2'd0;
58             else
59                 state <= state + 1;
60         end else begin
61             //bounce
62             if (direction == 0) begin
63                 if (state == 2'd2) begin
64                     direction <= 1;
65                     state <= 2'd1;
66                 end else if (state == 2'd3) begin
67                     direction <= 1;
68                     state <= 2'd2;
69                 end else
70                     state <= state + 1;
71             end else begin
72                 if (state == 2'd0) begin
73                     direction <= 0;
74                     state <= 2'd1;
75                 end else
76                     state <= state - 1;
77             end
78         end
79     end else begin
80         state <= state;

```

```

81         direction <= direction;
82     end
83 end

84
85 always @(*) begin
86     case (state)
87         2'd0: bcd = S0;
88         2'd1: bcd = S1;
89         2'd2: bcd = S2;
90         2'd3: bcd = S3;
91         default: bcd = ALL_BLANK;
92     endcase
93
94     if (sw == 0)
95         led = RED;
96     else
97         led = GREEN;
98 end
99 endmodule

```

Program 4: RTL implementation of Exercise 2.

3.2 Testbench

The testbench used to verify the correct operation of the RTL design for Exercise 2. It tests the design across several operating scenarios to ensure correct state transitions, output functionality and response to user input.

- Test 1 (Initial values check): Verifies that, after reset, the output values display on the 7-segment LEDs and the indicator LED are set correctly to their initial, expected values.
- Test 2 (Effect 1 check): With the switch set to 0, the testbench checks that the display pattern scrolls through all states in the correct order, looping back to the start.
- Test 3 (Effect 2 check): With the switch set to 1, the testbenh verifies that the display pattern bounces back and forth between the ends, changing direction as expected.
- Test 4 and 5 (Mode switching): The test alternates between scroll and bounce modes, ensuring that the state machine handles mode changes correctly and outputs the proper LED color and display pattern immediately after each switch.
- Test 6 (Reset functionality check): The testbench asserts and de-asserts the reset signal during both scroll and bounce modes, checking whether the module correctly returns to its initial state after a reset.

```

1 module tb;
2 reg clk;
3 reg rst_n;
4 reg sw;
5 wire [2:0] led;
6 wire [15:0] bcd;
7
8 parameter CLK_PERIOD = 8; // 8ns => 125MHz
9 parameter TICK_WAIT = (CLK_PERIOD * 50);

```

```

10
11 parameter RED = 3'b100;
12 parameter GREEN = 3'b010;
13
14 parameter BCD_2 = 4'd2;
15 parameter BCD_5 = 4'd5;
16 parameter BCD_BLANK = 4'hF;
17 parameter ALL_BLANK = 16'hFFFF;
18
19 parameter S0 = {BCD_2, BCD_5, BCD_BLANK, BCD_BLANK}; // "25__"
20 parameter S1 = {BCD_BLANK, BCD_2, BCD_5, BCD_BLANK}; // "__25"
21 parameter S2 = {BCD_BLANK, BCD_BLANK, BCD_2, BCD_5}; // "__25"
22 parameter S3 = {BCD_5, BCD_BLANK, BCD_BLANK, BCD_2}; // "5__2"
23
24 integer pass, fail;
25
26 ex2 dut (
27     .clk (clk),
28     .rst_n (rst_n),
29     .sw (sw),
30     .led (led),
31     .bcd (bcd)
32 );
33
34 task divi;
35     $display ("-----");
36     -----");
37 endtask
38
39 task msg (input [700:0] txt);
40     begin
41         divi();
42         $display ("%0s", txt);
43         divi();
44     end
45 endtask
46
47 task check (input [15:0] exp_bcd, input [2:0] exp_led);
48     begin
49         $display ("[OUTPUT] Time = %0t | 7SEG = 16'h%4h, LED = 3'b%3b"
50             , $time, bcd, led);
51         $display ("[EXPECT] Time = %0t | 7SEG = 16'h%4h, LED = 3'b%3b"
52             , $time, exp_bcd, exp_led);
53
54         if ((bcd === exp_bcd) && (led === exp_led)) begin
55             $display ("===== > PASSED");
56             pass = pass + 1;
57         end else begin
58             $display ("===== > FAILED");
59             fail = fail + 1;
60         end
61     end
62 end

```

```

60    endtask
61
62    task mode (input tsw);
63        begin
64            divi();
65            $display ("[SWITCH] Time = %0t | Switching to effect %0d",
66                      $time, tsw + 1);
67            divi();
68            sw = tsw;
69        end
70    endtask
71
72    initial begin
73        clk = 0;
74        forever #(CLK_PERIOD/2) clk = ~clk;
75    end
76
77    initial begin
78        rst_n = 0;
79        sw = 0;
80        pass = 0;
81        fail = 0;
82        #100;
83        rst_n = 1;
84        #100;
85
86        msg ("TEST 1: INITIAL VALUES CHECK");
87        check (S0, RED);
88
89        msg ("TEST 2: SCROLL MODE CHECK");
90        #(TICK_WAIT);
91        check (S1, RED);
92
93        #(TICK_WAIT);
94        check (S2, RED);
95
96        #(TICK_WAIT);
97        check (S3, RED);
98
99        #(TICK_WAIT);
100       check (S0, RED);
101
102       #(TICK_WAIT);
103       check (S1, RED);
104
105       msg ("TEST 3: BOUNCE MODE CHECK");
106       mode (1);
107       #10;
108       check (S1, GREEN);
109
110       #(TICK_WAIT);
111       check (S2, GREEN);

```

```

112 #(TICK_WAIT);
113 check (S1, GREEN);
114
115 #(TICK_WAIT);
116 check (S0, GREEN);
117
118 #(TICK_WAIT);
119 check (S1, GREEN);
120
121 msg ("TEST 4: SWITCH BACK TO SCROLL MODE");
122 mode (0);
123 #10;
124 check (S1, RED);
125
126 #(TICK_WAIT);
127 check (S2, RED);
128
129 #(TICK_WAIT);
130 check (S3, RED);
131
132 msg ("TEST 5: SWITCH BACK TO BOUNCE MODE");
133 mode (1);
134 #10;
135 check (S3, GREEN);
136
137 #(TICK_WAIT);
138 check (S2, GREEN);
139
140 #(TICK_WAIT);
141 check (S1, GREEN);
142
143 #(TICK_WAIT);
144 check (S0, GREEN);
145
146 #(TICK_WAIT);
147 check (S1, GREEN);
148
149 msg ("TEST 6: RESET CHECK");
150 $display ("Resetting... ");
151 @(posedge clk);
152 rst_n = 0;
153 #10;
154 check (S0, GREEN);
155
156 #(TICK_WAIT);
157 check (S0, GREEN);
158
159 mode (0);
160 #10;
161 check (S0, RED);
162
163 mode (1);
164 $display ("Releasing reset... ");

```

```

165     #(TICK_WAIT);
166     rst_n = 1;
167     #10;
168
169     check (S0, GREEN);
170
171     #(TICK_WAIT);
172     check (S1, GREEN);
173
174     #(TICK_WAIT);
175     check (S2, GREEN);
176
177     #(TICK_WAIT);
178     check (S1, GREEN);
179
180     #(TICK_WAIT);
181     check (S0, GREEN);
182
183     #(TICK_WAIT);
184     check (S1, GREEN);
185
186     msg ("SUMMARY");
187     $display ("TOTAL TESTS : %0d", pass + fail);
188     $display ("Total PASSED: %0d", pass);
189     $display ("Total FAILED: %0d", fail);
190
191     if (fail == 0)
192         $display ("=====> ALL TESTS PASSED");
193     else if (pass == 0)
194         $display ("=====> ALL TESTS FAILED");
195     else
196         $display ("SOME TESTS FAILED");
197
198     #100;
199     $finish;
200 end
201 endmodule

```

Program 5: Testbench implementation of Exercise 2.

3.3 Testbench results

All test cases executed successfully, with each marked as PASSED. This outcome confirms that the test module behaves as intended and that the implemented RTL design meets the expected functionality.

```

1  # -----
2  # TEST 1: INITIAL VALUES CHECK
3  # -----
4  # [OUTPUT] Time = 200 | 7SEG = 16'h25ff, LED = 3'b100
5  # [EXPECT] Time = 200 | 7SEG = 16'h25ff, LED = 3'b100
6  # ======> PASSED
7  # -----

```

```

8 # TEST 2: SCROLL MODE CHECK
9 -----
10 # [OUTPUT] Time = 600 | 7SEG = 16'hf25f, LED = 3'b100
11 # [EXPECT] Time = 600 | 7SEG = 16'hf25f, LED = 3'b100
12 # =====> PASSED
13 # [OUTPUT] Time = 1000 | 7SEG = 16'hff25, LED = 3'b100
14 # [EXPECT] Time = 1000 | 7SEG = 16'hff25, LED = 3'b100
15 # =====> PASSED
16 # [OUTPUT] Time = 1400 | 7SEG = 16'h5ff2, LED = 3'b100
17 # [EXPECT] Time = 1400 | 7SEG = 16'h5ff2, LED = 3'b100
18 # =====> PASSED
19 # [OUTPUT] Time = 1800 | 7SEG = 16'h25ff, LED = 3'b100
20 # [EXPECT] Time = 1800 | 7SEG = 16'h25ff, LED = 3'b100
21 # =====> PASSED
22 # [OUTPUT] Time = 2200 | 7SEG = 16'hf25f, LED = 3'b100
23 # [EXPECT] Time = 2200 | 7SEG = 16'hf25f, LED = 3'b100
24 # =====> PASSED
25 #
26 # TEST 3: BOUNCE MODE CHECK
27 -----
28 #
29 # [SWITCH] Time = 2200 | Switching to effect 2
30 #
31 # [OUTPUT] Time = 2210 | 7SEG = 16'hf25f, LED = 3'b010
32 # [EXPECT] Time = 2210 | 7SEG = 16'hf25f, LED = 3'b010
33 # =====> PASSED
34 # [OUTPUT] Time = 2610 | 7SEG = 16'hff25, LED = 3'b010
35 # [EXPECT] Time = 2610 | 7SEG = 16'hff25, LED = 3'b010
36 # =====> PASSED
37 # [OUTPUT] Time = 3010 | 7SEG = 16'hf25f, LED = 3'b010
38 # [EXPECT] Time = 3010 | 7SEG = 16'hf25f, LED = 3'b010
39 # =====> PASSED
40 # [OUTPUT] Time = 3410 | 7SEG = 16'h25ff, LED = 3'b010
41 # [EXPECT] Time = 3410 | 7SEG = 16'h25ff, LED = 3'b010
42 # =====> PASSED
43 # [OUTPUT] Time = 3810 | 7SEG = 16'hf25f, LED = 3'b010
44 # [EXPECT] Time = 3810 | 7SEG = 16'hf25f, LED = 3'b010
45 # =====> PASSED
46 #
47 # TEST 4: SWITCH BACK TO SCROLL MODE
48 -----
49 #
50 # [SWITCH] Time = 3810 | Switching to effect 1
51 #
52 # [OUTPUT] Time = 3820 | 7SEG = 16'hf25f, LED = 3'b100
53 # [EXPECT] Time = 3820 | 7SEG = 16'hf25f, LED = 3'b100
54 # =====> PASSED
55 # [OUTPUT] Time = 4220 | 7SEG = 16'hff25, LED = 3'b100
56 # [EXPECT] Time = 4220 | 7SEG = 16'hff25, LED = 3'b100
57 # =====> PASSED
58 # [OUTPUT] Time = 4620 | 7SEG = 16'h5ff2, LED = 3'b100
59 # [EXPECT] Time = 4620 | 7SEG = 16'h5ff2, LED = 3'b100
60 # =====> PASSED

```

```

61 # -----
62 # TEST 5: SWITCH BACK TO BOUNCE MODE
63 #
64 #
65 # [SWITCH] Time = 4620 | Switching to effect 2
66 #
67 # [OUTPUT] Time = 4630 | 7SEG = 16'h5ff2, LED = 3'b010
68 # [EXPECT] Time = 4630 | 7SEG = 16'h5ff2, LED = 3'b010
69 # =====> PASSED
70 # [OUTPUT] Time = 5030 | 7SEG = 16'hff25, LED = 3'b010
71 # [EXPECT] Time = 5030 | 7SEG = 16'hff25, LED = 3'b010
72 # =====> PASSED
73 # [OUTPUT] Time = 5430 | 7SEG = 16'hf25f, LED = 3'b010
74 # [EXPECT] Time = 5430 | 7SEG = 16'hf25f, LED = 3'b010
75 # =====> PASSED
76 # [OUTPUT] Time = 5830 | 7SEG = 16'h25ff, LED = 3'b010
77 # [EXPECT] Time = 5830 | 7SEG = 16'h25ff, LED = 3'b010
78 # =====> PASSED
79 # [OUTPUT] Time = 6230 | 7SEG = 16'hf25f, LED = 3'b010
80 # [EXPECT] Time = 6230 | 7SEG = 16'hf25f, LED = 3'b010
81 # =====> PASSED
82 #
83 # TEST 6: RESET CHECK
84 #
85 # Resetting...
86 # [OUTPUT] Time = 6246 | 7SEG = 16'h25ff, LED = 3'b010
87 # [EXPECT] Time = 6246 | 7SEG = 16'h25ff, LED = 3'b010
88 # =====> PASSED
89 # [OUTPUT] Time = 6646 | 7SEG = 16'h25ff, LED = 3'b010
90 # [EXPECT] Time = 6646 | 7SEG = 16'h25ff, LED = 3'b010
91 # =====> PASSED
92 #
93 # [SWITCH] Time = 6646 | Switching to effect 1
94 #
95 # [OUTPUT] Time = 6656 | 7SEG = 16'h25ff, LED = 3'b100
96 # [EXPECT] Time = 6656 | 7SEG = 16'h25ff, LED = 3'b100
97 # =====> PASSED
98 #
99 # [SWITCH] Time = 6656 | Switching to effect 2
100 #
101 # Releasing reset...
102 # [OUTPUT] Time = 7066 | 7SEG = 16'h25ff, LED = 3'b010
103 # [EXPECT] Time = 7066 | 7SEG = 16'h25ff, LED = 3'b010
104 # =====> PASSED
105 # [OUTPUT] Time = 7466 | 7SEG = 16'hf25f, LED = 3'b010
106 # [EXPECT] Time = 7466 | 7SEG = 16'hf25f, LED = 3'b010
107 # =====> PASSED
108 # [OUTPUT] Time = 7866 | 7SEG = 16'hff25, LED = 3'b010
109 # [EXPECT] Time = 7866 | 7SEG = 16'hff25, LED = 3'b010
110 # =====> PASSED
111 # [OUTPUT] Time = 8266 | 7SEG = 16'hf25f, LED = 3'b010
112 # [EXPECT] Time = 8266 | 7SEG = 16'hf25f, LED = 3'b010
113 # =====> PASSED

```

```
114 # [OUTPUT] Time = 8666 | 7SEG = 16'h25ff , LED = 3'b010
115 # [EXPECT] Time = 8666 | 7SEG = 16'h25ff , LED = 3'b010
116 # =====> PASSED
117 # [OUTPUT] Time = 9066 | 7SEG = 16'hf25f , LED = 3'b010
118 # [EXPECT] Time = 9066 | 7SEG = 16'hf25f , LED = 3'b010
119 # =====> PASSED
120 #
121 # -----
122 # SUMMARY
123 #
124 # -----
125 # TOTAL TESTS : 28
126 # Total PASSED: 28
127 # Total FAILED: 0
128 # =====> ALL TESTS PASSED
129 # ** Note: $finish      : ..../tb/tb.v(198)
130 #           Time: 9166 ns Iteration: 0 Instance: /tb
```

Simulation 2: Testbench results of Exercise 2.

3.4 Simulation waveform

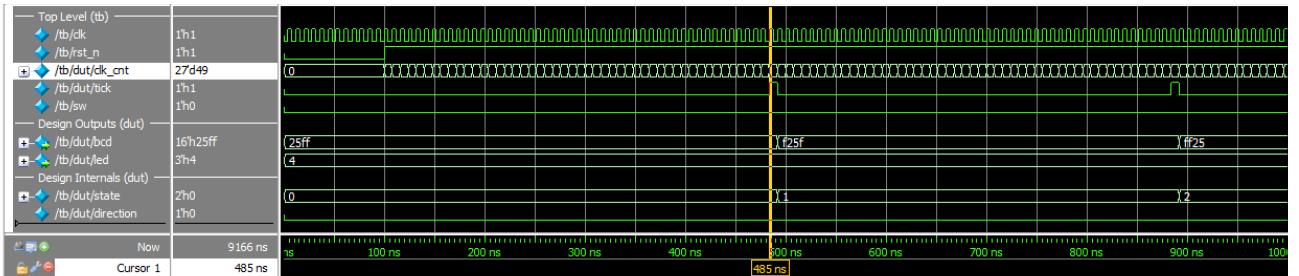


Figure 2.1

Figure 2.1 shows that after the reset is asserted and then deasserted, the module initializes to its initial state. In this state, the LED displays red, and the direction is set to 0, meaning the text string “25” moves from left to right.

In the simulation, one second corresponds to 100 clock cycles. The shifting effect occurs twice per second, so the string shifts every 50 clock cycles. When the `clk_cnt` signal counts from 0 to 49, the `tick` signal is raised high. On the following clock cycle, the string transitions to state 1, where “25” appears in the middle of the four 7-segment LED displays.

At the next tick, the string shifts again to state 2, positioning “25” on the two rightmost 7-segment LED displays.

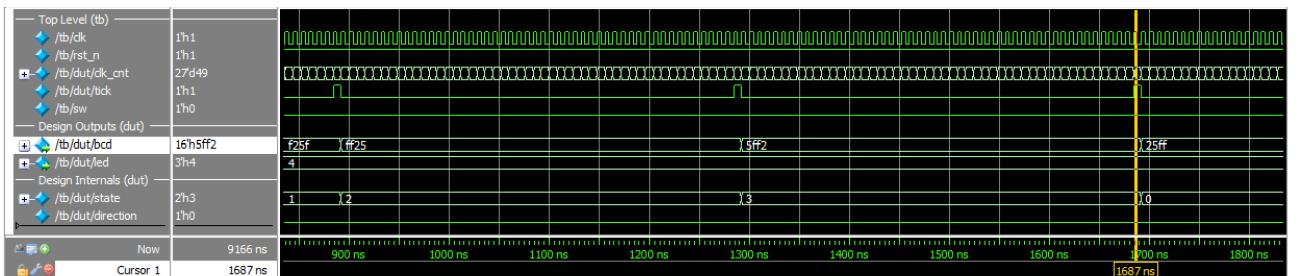


Figure 2.2

Since effect 1 scrolls from left to right, after reaching state 2 (“ff25”), the string shifts to state 3 (“5ff2”) one clock cycle after the next tick signal is asserted, producing a smooth scrolling transition.

At the following `tick`, one clock cycle later, the string returns to state 0 (“25ff”), thereby restarting the scrolling sequence from the beginning.

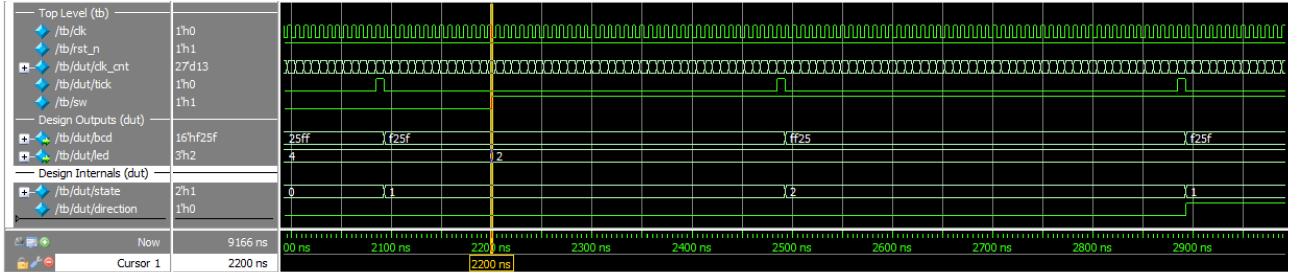


Figure 2.3

When the switch is turned on, indicated by the `sw` signal being asserted, the module activates effect 2, bouncing. In this mode, the LED changes to green, notifying the user that effect 2 is active.

Figure 2.3 shows that after the string reaches the right edge, the direction value changes to 1, meaning the string will now move from right to left. As a result, it bounces back to the middle of the four 7-segment LED displays.

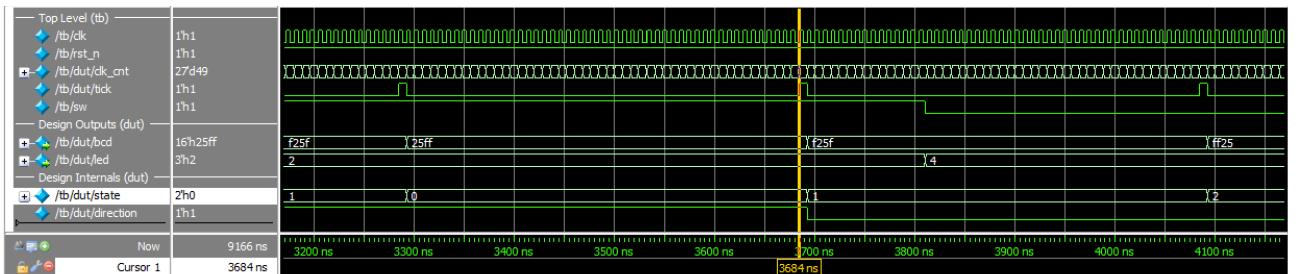


Figure 2.4

In Figure 2.4, the string shifts from right to left, and when it reaches the leftmost position, it bounces back to the right. At this point, the direction signal changes from 1 to 0 immediately after the `tick` signal is asserted at 3648 ns.

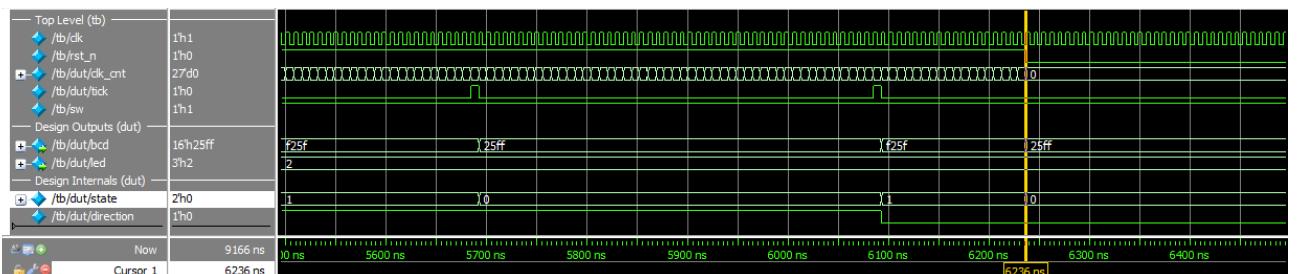


Figure 2.5

Skipping a few tests, Figure 2.5 demonstrates how the reset signal affects the module. When reset is asserted, the string immediately stops shifting and returns to the initial state (state 0). Importantly, the current effect remains active, and the user configuration is not reset.

Additional behavior can be observed more clearly through the test bench module, which provides easier tracking of the test results.

3.5 FPGA results

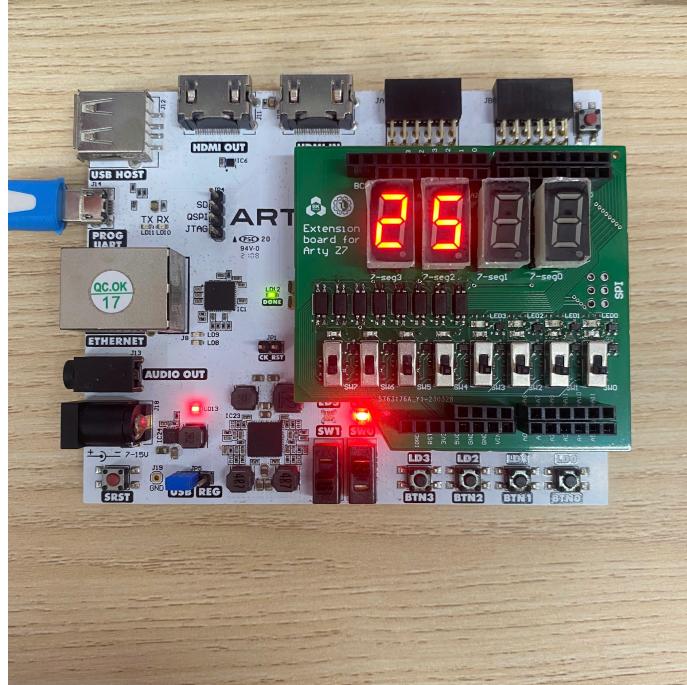


Figure 2.6

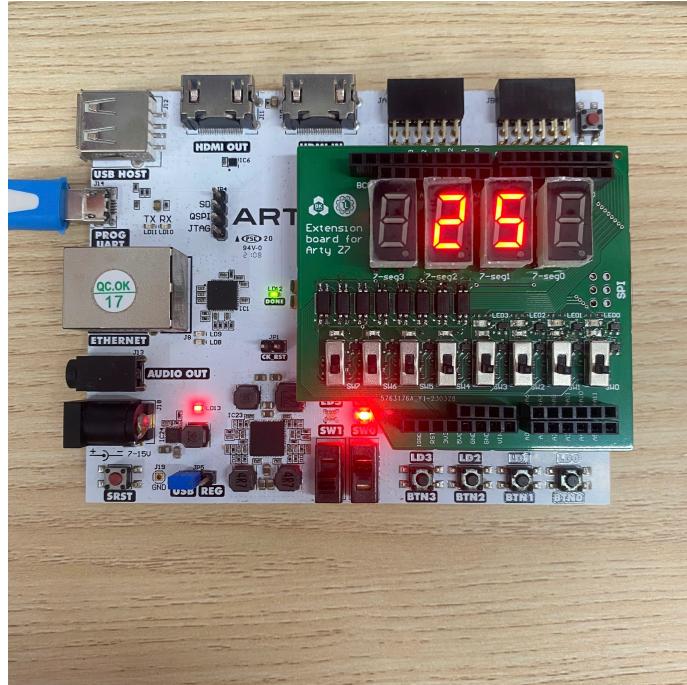


Figure 2.7

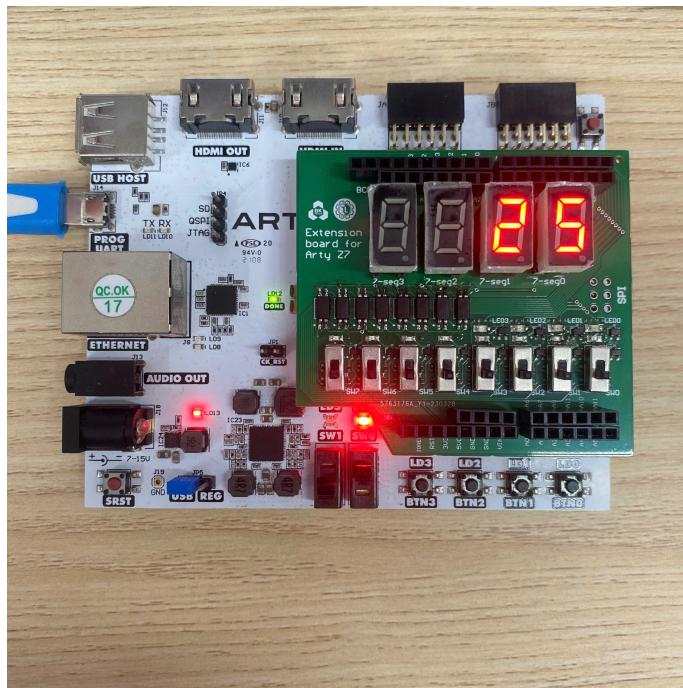


Figure 2.8

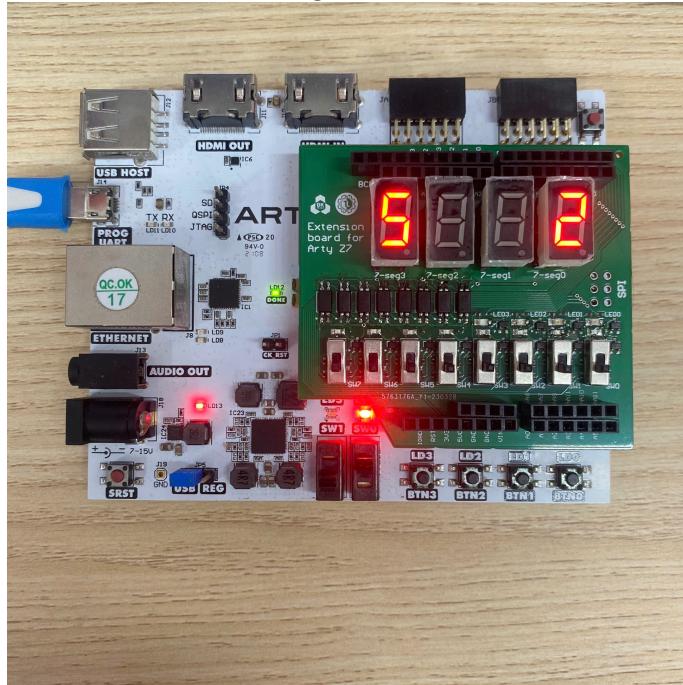


Figure 2.9

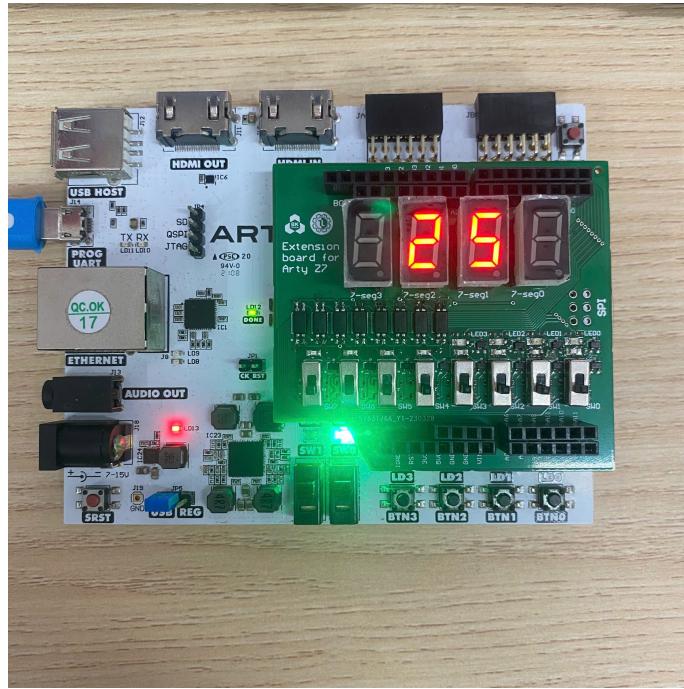


Figure 2.10

Figures 2.6 to 2.9 illustrate how the string “25” scrolls across the four 7-segment LED displays, moving from the leftmost to the rightmost position. During this process, the red LED remains on, indicating to the user that effect 1 is active.

Figure 2.10 shows the FPGA after the effect switch is turned on. At this point, the module transitions to effect 2, and the LED changes to green, signaling the mode switch.

4 Exercise 3

4.1 RTL implementation

This module used a FSM to handle a state machine that changes the display mode of a bit string. Initially, LEDs show the default 4-bit random string, which is performed by a reset signal, in this module we particularly set the default bit string to be 4'b0011. Buttons are used to change the display mode as follow:

- Button 0: Mode reset: Show the default 4-bit string on LEDs.
- Button 1: Mode circular shift left ring: Shift 4-bit string to left in a ring every 1 second.
- Button 2: Mode circular shift right ring: Shift 4-bit string to right in a ring every 1 second.
- Button 3: Pause: Pause the current shifting string.

```
1 module ex3 (
2     input wire clk,
3     input wire rst_n,
4     input wire [3:0] btn,
5     output reg [3:0] led
6 );
7
8 'ifdef SIMULATION
9     //for sim, a sec is 100 cycles
10    parameter CLK_FREQ = 27'd100;
11 'else
12     //for fpga, a sec is 125m cycles
13    parameter CLK_FREQ = 27'd125_000_000;
14 'endif
15
16 parameter PATTERN = 4'b0011;
17 parameter MODE0 = 2'd0;
18 parameter MODE1 = 2'd1;
19 parameter MODE2 = 2'd2;
20 parameter MODE3 = 2'd3;
21
22 reg [1:0] mode;
23 reg [26:0] clk_cnt;
24 wire tick_1s;
25 assign tick_1s = (clk_cnt == CLK_FREQ - 1);
26
27 always @(posedge clk or negedge rst_n) begin
28     if (!rst_n)
29         clk_cnt <= 27'd0;
30     else if (tick_1s)
31         clk_cnt <= 27'd0;
32     else
33         clk_cnt <= clk_cnt + 1;
34 end
35
36 always @(posedge clk or negedge rst_n) begin
```

```

37     if (!rst_n)
38         mode <= MODE0;
39     else if (btn[0])
40         mode <= MODE0;
41     else if (btn[1])
42         mode <= MODE1;
43     else if (btn[2])
44         mode <= MODE2;
45     else if (btn[3])
46         mode <= MODE3;
47     else
48         mode <= mode;
49 end
50
51 always @ (posedge clk or negedge rst_n) begin
52     if (!rst_n)
53         led <= PATTERN;
54     else if (tick_1s) begin
55         case (mode)
56             MODE1: led <= {led[2:0], led[3]}; //shift left
57             MODE2: led <= {led[0], led[3:1]}; //shift right
58             MODE3: led <= led;                //pause
59             default: led <= PATTERN;        //reset pattern
60         endcase
61     end else if (btn[0])
62         led <= PATTERN;
63     else
64         led <= led;
65 end
66 endmodule

```

Program 6: RTL implementation of Exercise 3.

4.2 Testbench

The testbench executes a sequence of functional tests for Exercise 3, including:

- Test 1 (Initial values check): After applying reset, the testbench verifies that the LED outputs initialized to the expected default pattern, which is 4'b0011.
- Test 2 (Shift left test): The test simulates pressing button 1 to shift left and confirms that subsequent clock ticks continuously shift the pattern left, with wrapping, across several cycles.
- Test 3 (Shift right test): By pressing button 2 to shift right, the testbench checks that the LED pattern shifts right as intended, with the correct bit wrapping behavior, for multiple cycles.
- Test 4 (Pause mode test): Pressing button 3 tests the pause functionality, confirming that the LED outputs remain unchanged even after additional clock ticks.
- Test 5 (Reset check through button 0): The testbench validates the effect of button 0 press, ensuring the LED outputs restore to the default pattern, mode and pattern updates are blocked during reset.

- Test 6 (Reset check through system reset): The same effect with button 0 press. However, during the global reset activation, no button press can be operated, the system remains with the default pattern bit string displayed on the LEDs. After the reset is released, the system must behave normally as expected.

```

1 module tb;
2 reg clk;
3 reg rst_n;
4 reg [3:0] btn;
5 wire [3:0] led;
6
7 parameter CLK_PERIOD = 8; // 8ns = 125MHz
8 parameter DEBOUNCE_WAIT = CLK_PERIOD * 5;
9 parameter TICK_WAIT = CLK_PERIOD * 100;
10 parameter PATTERN = 4'b0011;
11
12 integer pass, fail;
13
14 ex3 dut (
15     .clk      (clk),
16     .rst_n   (rst_n),
17     .btn      (btn),
18     .led      (led)
19 );
20
21 task divi;
22     $display ("-----");
23     -----");
24 endtask
25
26 task msg (input [700:0] txt);
27     begin
28         divi();
29         $display ("%0s", txt);
30         divi();
31     end
32 endtask
33
34 task check (input [3:0] exp_led);
35     begin
36         $display ("[OUTPUT] Time = %0t | LED = 4'b%4b", $time, led);
37         $display ("[EXPECT] Time = %0t | LED = 4'b%4b", $time, exp_led
38             );
39
40         if (led === exp_led) begin
41             $display ("===== > PASSED");
42             pass = pass + 1;
43         end else begin
44             $display ("===== > FAILED");
45             fail = fail + 1;
46         end
47     end
48 end

```

```

47 endtask

48

49 task press (input [3:0] btn_press);
50 begin
51     case (btn_press)
52         4'b0001: $display ("Button 0 is pressed");
53         4'b0010: $display ("Button 1 is pressed");
54         4'b0100: $display ("Button 2 is pressed");
55         4'b1000: $display ("Button 3 is pressed");
56         default: $display ("More than one button is pressed");
57     endcase
58
59     btn = btn_press;
60     #(DEBOUNCE_WAIT);
61     btn = 4'b0000;
62     #(DEBOUNCE_WAIT);
63 end
64 endtask

65

66 initial begin
67     clk = 0;
68     forever #(CLK_PERIOD/2) clk = ~clk;
69 end

70

71 initial begin
72     rst_n = 0;
73     btn = 4'b0000;
74     pass = 0;
75     fail = 0;
76     #100;
77     rst_n = 1;
78     #100;

79     msg ("TEST 1: INITIAL VALUE CHECK");
80     check (PATTERN);

81     msg ("TEST 2: BUTTON 1 PRESS (SHIFT LEFT) CHECK");
82     press (4'b0010);

83     #(TICK_WAIT);
84     check (4'b0110);

85     #(TICK_WAIT);
86     check (4'b1100);

87     #(TICK_WAIT);
88     check (4'b1001);

89     #(TICK_WAIT);
90     check (4'b0011);

91     msg ("TEST 3: BUTTON 2 PRESS (SHIFT RIGHT) CHECK");
92     press (4'b0100);

```

```

100
101 #(TICK_WAIT);
102 check (4'b1001);
103
104 #(TICK_WAIT);
105 check (4'b1100);
106
107 #(TICK_WAIT);
108 check (4'b0110);
109
110 #(TICK_WAIT);
111 check (4'b0011);
112 msg ("TEST 4: BUTTON 3 PRESS (PAUSE) CHECK");
113 #(TICK_WAIT);
114 check (4'b1001);
115
116 press (4'b1000);
117
118 #(TICK_WAIT);
119 check (4'b1001);
120
121 #(TICK_WAIT);
122 check (4'b1001);
123
124 msg ("TEST 5: BUTTON 0 PRESS (RESET) CHECK");
125 press (4'b0001);
126
127 #(TICK_WAIT);
128 check (PATTERN);
129
130 #(TICK_WAIT);
131 check (PATTERN);
132
133 #(TICK_WAIT);
134 check (PATTERN);
135
136 press (4'b0100);
137
138 #(TICK_WAIT);
139 check (4'b1001);
140
141 #(TICK_WAIT);
142 check (4'b1100);
143
144 msg ("TEST 6: RESET CHECK");
145 $display ("Reseting . . .");
146 rst_n = 0;
147
148 #(TICK_WAIT);
149 check (PATTERN);
150
151 press (4'b0010);
152 #(TICK_WAIT);

```

```

153     check (PATTERN);
154
155 #(TICK_WAIT);
156     check (PATTERN);
157
158     press (4'b0100);
159 #(TICK_WAIT);
160     check (PATTERN);
161
162 #(TICK_WAIT);
163     check (PATTERN);
164
165 #(CLK_PERIOD * 5);
166 $display ("Releasing reset...");
167 rst_n = 1;
168 #10;
169
170     check (PATTERN);
171
172     press (4'b0010);
173
174 #(TICK_WAIT);
175     check (4'b0110);
176
177 #(TICK_WAIT);
178     check (4'b1100);
179
180 msg ("SUMMARY");
181 $display ("TOTAL TESTS : %0d", pass + fail);
182 $display ("Total PASSED: %0d", pass);
183 $display ("Total FAILED: %0d", fail);
184
185 if (fail == 0)
186     $display ("===== > ALL TESTS PASSED");
187 else if (pass == 0)
188     $display ("===== > ALL TESTS FAILED");
189 else
190     $display ("SOME TESTS FAILED");
191
192 #100;
193 $finish;
194 end
195 endmodule

```

Program 7: Testbench implementation of Exercise 3.

4.3 Testbench results

All test cases executed successfully, with each marked as PASSED. This outcome confirms that the test module behaves as intended and that the implemented RTL design meets the expected functionality.

```
1 # -----
2 # TEST 1: INITIAL VALUE CHECK
3 #
4 # [OUTPUT] Time = 200 | LED = 4'b0011
5 # [EXPECT] Time = 200 | LED = 4'b0011
6 # =====> PASSED
7 #
8 # -----
9 # TEST 2: BUTTON 1 PRESS (SHIFT LEFT) CHECK
10 #
11 # Button 1 is pressed
12 # [OUTPUT] Time = 1080 | LED = 4'b0110
13 # [EXPECT] Time = 1080 | LED = 4'b0110
14 # =====> PASSED
15 # [OUTPUT] Time = 1880 | LED = 4'b1100
16 # [EXPECT] Time = 1880 | LED = 4'b1100
17 # =====> PASSED
18 # [OUTPUT] Time = 2680 | LED = 4'b1001
19 # [EXPECT] Time = 2680 | LED = 4'b1001
20 # =====> PASSED
21 # [OUTPUT] Time = 3480 | LED = 4'b0011
22 # [EXPECT] Time = 3480 | LED = 4'b0011
23 # =====> PASSED
24 #
25 # -----
26 # TEST 3: BUTTON 2 PRESS (SHIFT RIGHT) CHECK
27 #
28 # Button 2 is pressed
29 # [OUTPUT] Time = 4360 | LED = 4'b1001
30 # [EXPECT] Time = 4360 | LED = 4'b1001
31 # =====> PASSED
32 # [OUTPUT] Time = 5160 | LED = 4'b1100
33 # [EXPECT] Time = 5160 | LED = 4'b1100
34 # =====> PASSED
35 # [OUTPUT] Time = 5960 | LED = 4'b0110
36 # [EXPECT] Time = 5960 | LED = 4'b0110
37 # =====> PASSED
38 # [OUTPUT] Time = 6760 | LED = 4'b0011
39 # [EXPECT] Time = 6760 | LED = 4'b0011
40 # =====> PASSED
41 #
42 # -----
43 # TEST 4: BUTTON 3 PRESS (PAUSE) CHECK
44 #
45 # [OUTPUT] Time = 7560 | LED = 4'b1001
46 # [EXPECT] Time = 7560 | LED = 4'b1001
47 # =====> PASSED
48 # Button 3 is pressed
49 # [OUTPUT] Time = 8440 | LED = 4'b1001
50 # [EXPECT] Time = 8440 | LED = 4'b1001
51 # =====> PASSED
```

```

49 # [OUTPUT] Time = 9240 | LED = 4'b1001
50 # [EXPECT] Time = 9240 | LED = 4'b1001
51 # =====> PASSED
52 #
53 # TEST 5: BUTTON 0 PRESS (RESET) CHECK
54 #
55 # Button 0 is pressed
56 # [OUTPUT] Time = 10120 | LED = 4'b0011
57 # [EXPECT] Time = 10120 | LED = 4'b0011
58 # =====> PASSED
59 # [OUTPUT] Time = 10920 | LED = 4'b0011
60 # [EXPECT] Time = 10920 | LED = 4'b0011
61 # =====> PASSED
62 # [OUTPUT] Time = 11720 | LED = 4'b0011
63 # [EXPECT] Time = 11720 | LED = 4'b0011
64 # =====> PASSED
65 # Button 2 is pressed
66 # [OUTPUT] Time = 12600 | LED = 4'b1001
67 # [EXPECT] Time = 12600 | LED = 4'b1001
68 # =====> PASSED
69 # [OUTPUT] Time = 13400 | LED = 4'b1100
70 # [EXPECT] Time = 13400 | LED = 4'b1100
71 # =====> PASSED
72 #
73 # TEST 6: RESET CHECK
74 #
75 # Resetting...
76 # [OUTPUT] Time = 14200 | LED = 4'b0011
77 # [EXPECT] Time = 14200 | LED = 4'b0011
78 # =====> PASSED
79 # Button 1 is pressed
80 # [OUTPUT] Time = 15080 | LED = 4'b0011
81 # [EXPECT] Time = 15080 | LED = 4'b0011
82 # =====> PASSED
83 # [OUTPUT] Time = 15880 | LED = 4'b0011
84 # [EXPECT] Time = 15880 | LED = 4'b0011
85 # =====> PASSED
86 # Button 2 is pressed
87 # [OUTPUT] Time = 16760 | LED = 4'b0011
88 # [EXPECT] Time = 16760 | LED = 4'b0011
89 # =====> PASSED
90 # [OUTPUT] Time = 17560 | LED = 4'b0011
91 # [EXPECT] Time = 17560 | LED = 4'b0011
92 # =====> PASSED
93 # Releasing reset...
94 # [OUTPUT] Time = 17610 | LED = 4'b0011
95 # [EXPECT] Time = 17610 | LED = 4'b0011
96 # =====> PASSED
97 # Button 1 is pressed
98 # [OUTPUT] Time = 18490 | LED = 4'b0110
99 # [EXPECT] Time = 18490 | LED = 4'b0110
100 # =====> PASSED
101 # [OUTPUT] Time = 19290 | LED = 4'b1100

```

```

102 # [EXPECT] Time = 19290 | LED = 4'b1100
103 # =====> PASSED
104 #
105 # SUMMARY
106 #
107 # TOTAL TESTS : 25
108 # Total PASSED: 25
109 # Total FAILED: 0
110 #
111 # =====> ALL TESTS PASSED
112 # ** Note: $finish : ./tb/tb.v(192)
#     Time: 19390 ns Iteration: 0 Instance: /tb

```

Simulation 3: Testbench results of Exercise 3.

4.4 Simulation waveform

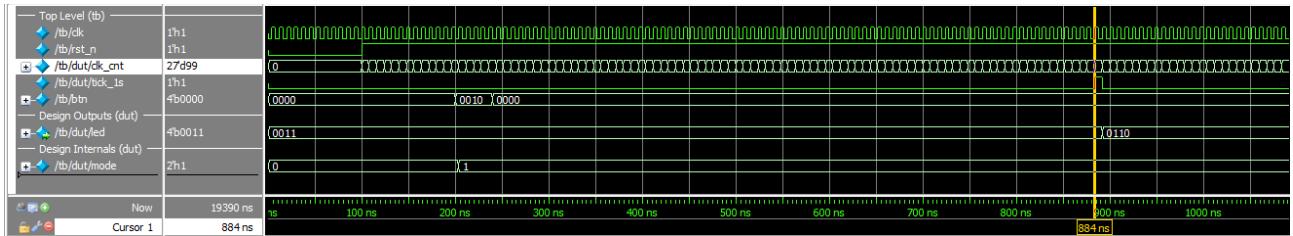


Figure 3.1

In this simulation, one second corresponds to 100 clock cycles.

Figure 3.1 shows that after the reset is asserted and then deasserted, the LEDs display the default string 4'b0011. When Button 1 (shift left) is pressed, the system waits 100 clock cycles until the `tick_1s` signal is asserted, indicating that one second has elapsed.

On the following clock cycle, the string shifts to the left, resulting in 4'b0110, as reflected by the `led` signal.

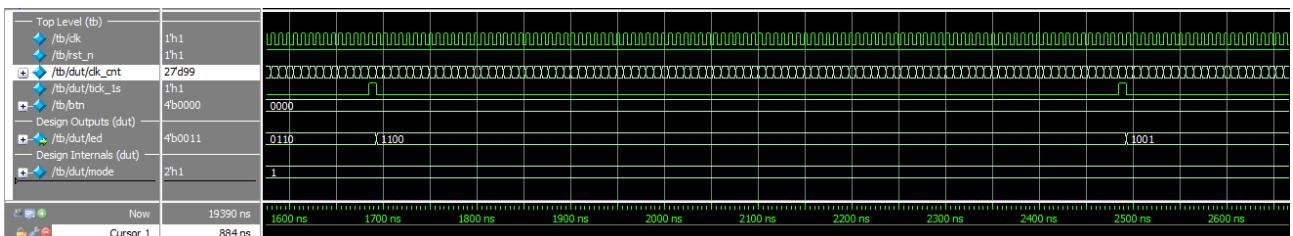


Figure 3.2

Figure 3.2 illustrates how the string continues to shift left at 1-second intervals, triggered by the assertion of the `tick_1s` signal.

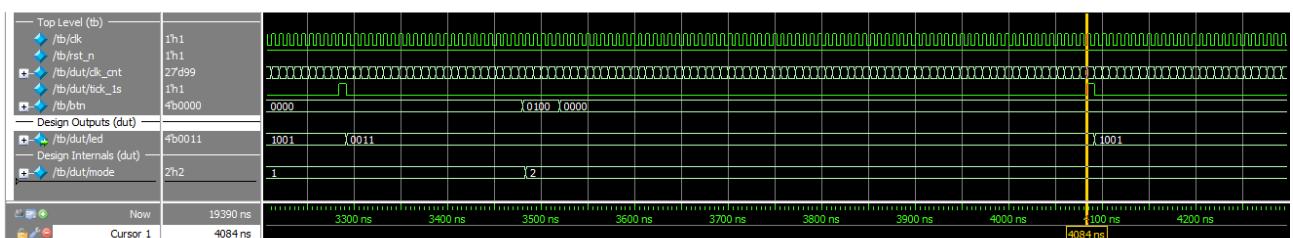


Figure 3.3

Figure 3.3 shows that the string initially holds the value 4'b0011. After pressing Button 2 (shift right), the string shifts to the right. One clock cycle after the `tick_1s` signal is asserted, the result becomes 4'b1001.

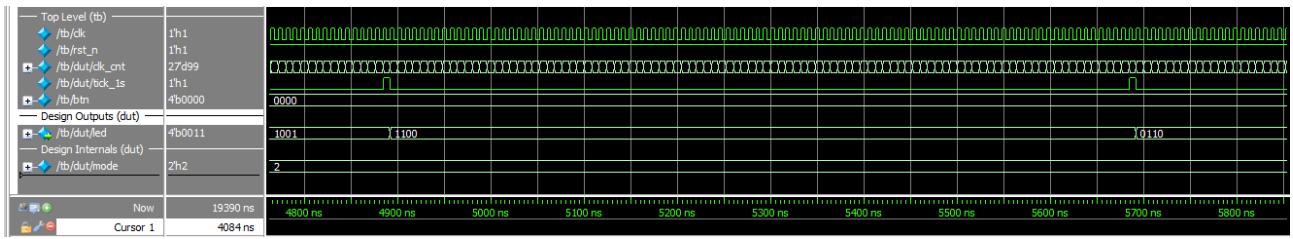


Figure 3.4

Figure 3.4 illustrates how the string continues to shift to the right at 1-second intervals, triggered by the assertion of the `tick_1s` signal.

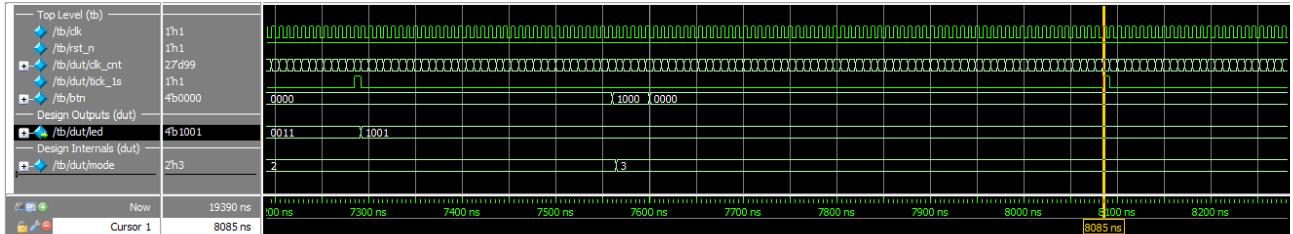


Figure 3.5

Figure 3.5 demonstrates that when Button 3 (pause) is pressed, the string remains unchanged. Even after the next second, indicated by the assertion of the `tick_1s` signal, the value stays at `4'b1001`. This confirms that the pause function operates correctly, preventing any further shifts while active.

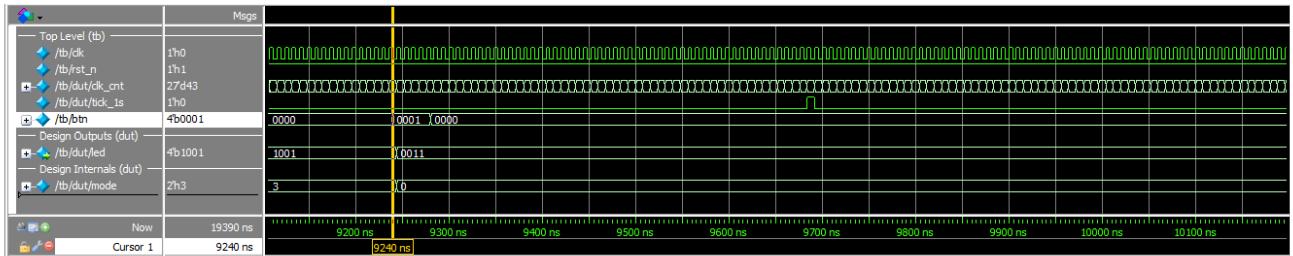


Figure 3.6

Button 0 is used to reset the string, and it is designed to take effect immediately upon being pressed. For example, when the string holds the value `4'b1001`, pressing Button 0 resets it instantly to the default value `4'b0011`.

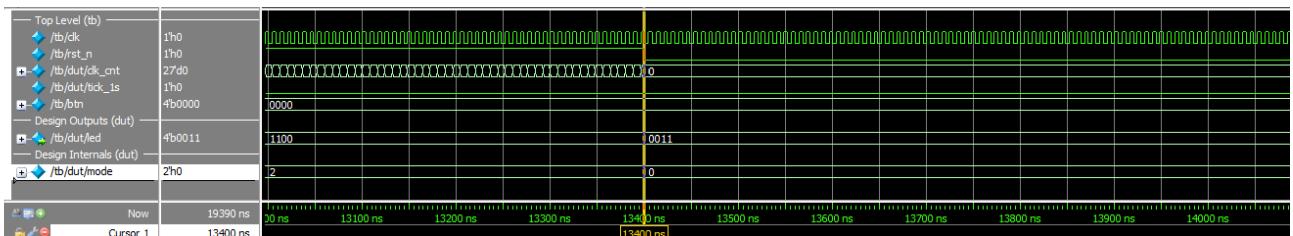


Figure 3.7

Figure 3.7 illustrates the behavior of the reset mechanism. Since the design uses an asynchronous active-low reset, asserting the reset immediately forces the string value `4'b1100` back to its default value `4'b0011` at 13400 ns.

4.5 FPGA results

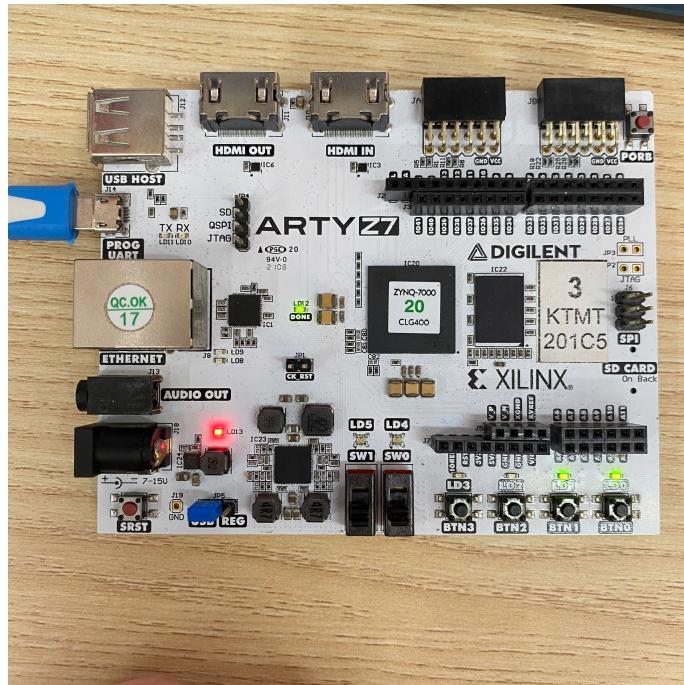


Figure 3.8

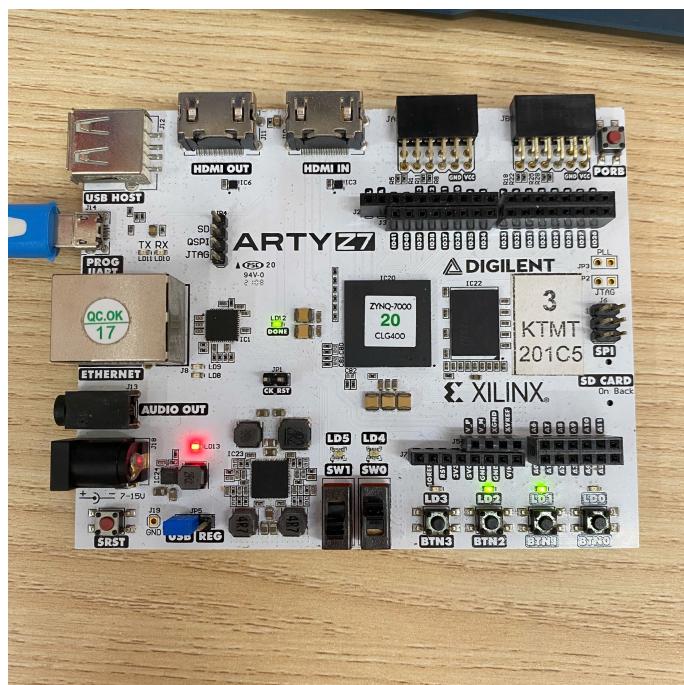


Figure 3.9

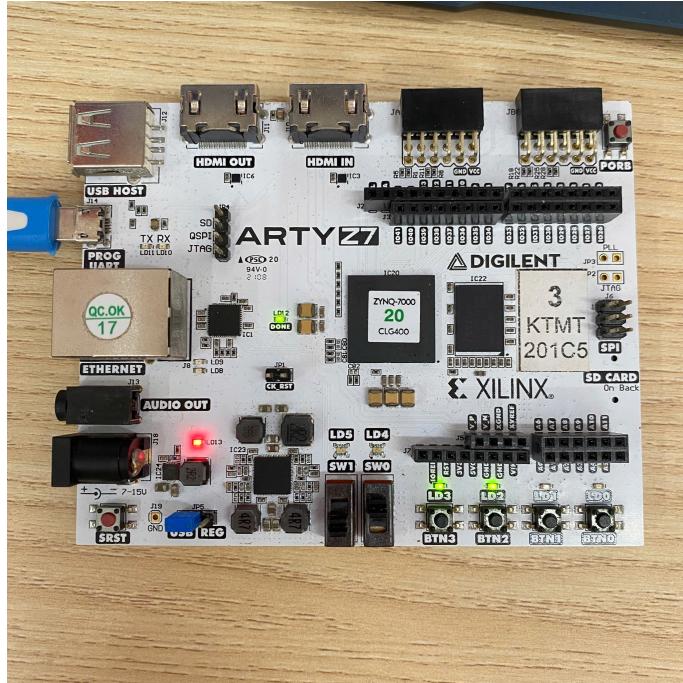


Figure 3.10

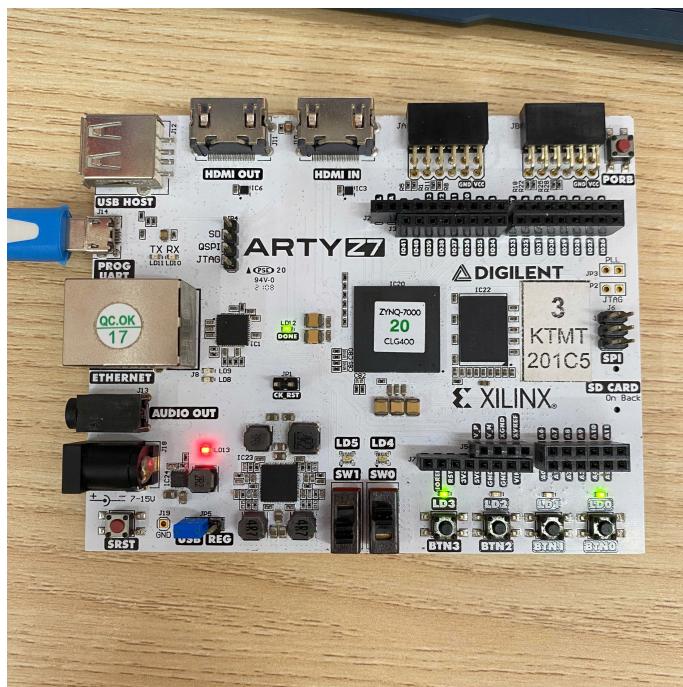


Figure 3.11

This section presents part of the FPGA demonstration. Figures 3.8 to 3.11 illustrate how the string shifts to the left when Button 1 is pressed. The sequence progresses from the initial value 4'b0011 to 4'b0110, then to 4'b1100, and finally to 4'b1001.



The screenshot shows a terminal window titled "Terminal 1" with the status "Serial: (COM6, 115200, 8, 1, None, None - CONNECTED) - Encoding: (ISO-8859-1)". The window displays a sequence of text output from the serial port. The output starts with a "RESET" command followed by an LED value of "0011". This is followed by a series of "SHIFT LEFT" commands, each resulting in a new LED value: "0110", "1100", "1001", "0011", and finally "1001" again. After this, there is a "SHIFT RIGHT" command followed by "1100", "0110", and "0110" again. The sequence ends with two "PAUSE" commands, each followed by an LED value of "0110".

```
RESET
LED = 0011
SHIFT LEFT
LED = 0110
SHIFT LEFT
LED = 1100
SHIFT LEFT
LED = 1001
SHIFT LEFT
LED = 0011
SHIFT RIGHT
LED = 1001
SHIFT RIGHT
LED = 1100
SHIFT RIGHT
LED = 0110
PAUSE
LED = 0110
PAUSE
LED = 0110
```

Figure 3.12

Figure 3.12 shows the transmission of the current LED string to the PC via UART. This functionality was successfully implemented and verified by observing the UART output in the terminal window. The terminal logs show a sequence of operations including reset, left shift, right shift, and pause, with each action followed by an updated LED value. For example, after issuing a SHIFT LEFT command, the LED string transitions from 0011 to 0110, then to 1100, and so on. Similarly, SHIFT RIGHT operations correctly reverse the pattern, and PAUSE maintains the current value across ticks. These outputs confirm that the system reliably communicates the LED state to the PC in real time using UART.

5 Divider

5.1 RTL implementation

These modules are built to perform unsigned division and remainder operations based on the provided algorithm in Lab 1 documentation. The two module implemented with combinational logic only and doesn't handle the case of a divisor of zero. In this implementation, no / or % in the Verilog code.

The `divu_1iter` module is intended to perform a single iteration of unsiged integer division, updating remainder, quotient and divided registers based on its inputs.

```
1 module divu_1iter (
2     input wire [31:0] dividend_in,
3     input wire [31:0] quotient_in,
4     input wire [31:0] remainder_in,
5     input wire [31:0] divisor,
6
7     output wire [31:0] dividend_out,
8     output wire [31:0] quotient_out,
9     output wire [31:0] remainder_out
10 );
11
12 wire [31:0] new_remainder, subtract;
13 wire can_subtract;
14 assign new_remainder = {remainder_in[30:0], dividend_in[31]};
15 assign subtract = new_remainder - divisor;
16 assign can_subtract = new_remainder >= divisor;
17
18 assign remainder_out = can_subtract ? subtract : new_remainder;
19 assign quotient_out = {quotient_in[30:0], can_subtract};
20 assign dividend_out = dividend_in << 1;
21 endmodule
```

Program 8: RTL implementation of the `divu_1liter` module.

The `divider_unsigned` module computes the quotient and remainder for unsigned integer division operations, a fundamental operation in many digital systems.

```
1 module divider_unsigned (
2     input wire [31:0] dividend,
3     input wire [31:0] divisor,
4     output wire [31:0] quotient,
5     output wire [31:0] remainder
6 );
7
8 wire [31:0] dividend_arr [0:32];
9 wire [31:0] quotient_arr [0:32];
10 wire [31:0] remainder_arr [0:32];
11
12 assign dividend_arr[0] = dividend;
13 assign quotient_arr[0] = 32'b0;
14 assign remainder_arr[0] = 32'b0;
15
16 genvar i;
```

```

17 generate
18   for (i = 0; i < 32; i = i + 1) begin : loop
19     divu_1iter div_iter (
20       .dividend_in  (dividend_arr[i]),
21       .quotient_in (quotient_arr[i]),
22       .remainder_in (remainder_arr[i]),
23       .divisor      (divisor),
24       .dividend_out (dividend_arr[i+1]),
25       .quotient_out (quotient_arr[i+1]),
26       .remainder_out (remainder_arr[i+1])
27     );
28   end
29 endgenerate
30
31 assign quotient = quotient_arr[32];
32 assign remainder = remainder_arr[32];
33 endmodule

```

Program 9: RTL implementation of the divider_unsigned module.

5.2 Testbench

This testbench is used to check the arithmetic and logical accuracy of the `divu_1iter` design over a diverse set of test cases, simulating a variety of operand values and initial conditions. It ensures that the module correctly implements the intended division iteration logic, including handling edge cases, large operands and multiple input combinations.

```

1 module tb_divu_1iter;
2 reg [31:0] remainder_in;
3 reg [31:0] quotient_in;
4 reg [31:0] dividend_in;
5 reg [31:0] divisor;
6
7 wire [31:0] remainder_out;
8 wire [31:0] quotient_out;
9 wire [31:0] dividend_out;
10
11 integer pass, fail;
12
13 divu_1iter u_dut (
14   .remainder_in (remainder_in),
15   .quotient_in (quotient_in),
16   .dividend_in (dividend_in),
17   .divisor      (divisor),
18
19   .remainder_out (remainder_out),
20   .quotient_out (quotient_out),
21   .dividend_out (dividend_out)
22 );
23
24 task divi;
25   $display ("-----")

```

```

26      -----");
27 endtask
28
29 task check (input [31:0] exp_rem, input [31:0] exp_quo, input [31:0]
30   exp_div);
31   begin
32     $display ("[OUTPUT] Time = %0t | remainder_out = %0d,
33               quotient_out = %0d, dividend_out = %h", $time,
34               remainder_out, quotient_out, dividend_out);
35     $display ("[EXPECT] Time = %0t | remainder_out = %0d,
36               quotient_out = %0d, dividend_out = %h", $time, exp_rem,
37               exp_quo, exp_div);
38
39     if ((remainder_out === exp_rem) && (quotient_out === exp_quo)
40       && (dividend_out === exp_div)) begin
41       $display ("=====> PASSED");
42       pass = pass + 1;
43     end else begin
44       $display ("=====> FAILED");
45       fail = fail + 1;
46     end
47   end
48 endtask
49
50 task test (input [31:0] div_in, input [31:0] dvsr, input [31:0] rem_in
51   , input [31:0] quo_in);
52   begin
53     divi();
54     $display ("[TEST]    Time = %0t | dividend_in = %0h, divisor =
55               %0d, remainder_in = %0d, quotient_in = %0d", $time, div_in,
56               dvsr, rem_in, quo_in);
57     divi();
58
59     dividend_in = div_in;
60     divisor = dvsr;
61     remainder_in = rem_in;
62     quotient_in = quo_in;
63     #10;
64   end
65 endtask
66
67 initial begin
68   pass = 0;
69   fail = 0;
70   #10;
71
72   test (32'h8000_0000, 32'd2, 32'd0, 32'd8);
73   check (32'd1, 32'd16, 32'd0);
74
75   test (32'h8000_0000, 32'd1, 32'd0, 32'd8);
76   check (32'd0, 32'd17, 32'd0);
77
78   test (32'h0000_0004, 32'd3, 32'd2, 32'd1);

```

```

70      check (32'd1, 32'd3, 32'd8);
71
72      test (32'h4000_0000, 32'd5, 32'd3, 32'd0);
73      check (32'd1, 32'd1, 32'h8000_0000);
74
75      test (32'h0000_0000, 32'd10, 32'd4, 32'd1);
76      check (32'd8, 32'd2, 32'h0000_0000);
77
78      test (32'ha000_0000, 32'd3, 32'd2, 32'd5);
79      check (32'd2, 32'd11, 32'h4000_0000);
80
81      test (32'h8000_0000, 32'd6, 32'd2, 32'd0);
82      check (32'd5, 32'd0, 32'h0000_0000);
83
84      test (32'h8000_0000, 32'd5, 32'd2, 32'd0);
85      check (32'd0, 32'd1, 32'h0000_0000);
86
87      test (32'hFFFF_FFFF, 32'hFFFF_FFFF, 32'hFFFF_FFFF, 32'hFFFF_FFFF);
88      check (32'd0, 32'hFFFF_FFFF, 32'hFFFF_FFFE);
89
90      test (32'h1234_5678, 32'd100, 32'd200, 32'd42);
91      check (32'd300, 32'd85, 32'h2468_ACF0);
92
93      test (32'h1234_5678, 32'd500, 32'd200, 32'd42);
94      check (32'd400, 32'd84, 32'h2468_ACF0);
95
96      test (32'h0000_0000, 32'd1, 32'd0, 32'd123);
97      check (32'd0, 32'd246, 32'h0000_0000);
98
99      test (32'h8000_0000, 32'hFFFF_FFFF, 32'd0, 32'd0);
100     check (32'd1, 32'd0, 32'h0000_0000);
101
102     divi();
103     $display ("SUMMARY");
104     divi();
105     $display ("TOTAL TESTS : %0d", pass + fail);
106     $display ("Total PASSED: %0d", pass);
107     $display ("Total FAILED: %0d", fail);
108
109     if (fail == 0)
110         $display ("===== > ALL TESTS PASSED");
111     else
112         $display ("===== > SOME TESTS FAILED");
113
114     #100;
115     $finish;
116 end
117 endmodule

```

Program 10: Testbench implementation of divu_liter module.

This testbench applies a wide range of input combinations to the divider_unsigned module and checks the resulting quotient and remainder against the mathematically expected results. It ensures that the divider correctly process both typical and edge-cases inputs, guaranteeing reliability for synthesis or further hardware integration.

```

1  module tb_divider_unsigned;
2  reg [31:0] dividend;
3  reg [31:0] divisor;
4  wire [31:0] quotient;
5  wire [31:0] remainder;
6
7  integer pass, fail;
8
9  divider_unsigned u_dut (
10    .dividend (dividend),
11    .divisor (divisor),
12    .quotient (quotient),
13    .remainder (remainder)
14 );
15
16 task divi;
17   $display ("-----");
18   -----");
19 endtask
20
21 task msg (input [700:0] txt);
22   begin
23     divi();
24     $display ("%0s", txt);
25     divi();
26   end
27 endtask
28
29 task check (input [31:0] exp_quo, input [31:0] exp_rem);
30   begin
31     $display ("[OUTPUT] Time = %0t | quotient = %0d, remainder = %0d",
32               $time, quotient, remainder);
33     $display ("[EXPECT] Time = %0t | quotient = %0d, remainder = %0d",
34               $time, exp_quo, exp_rem);
35
36     if ((quotient === exp_quo) && (remainder === exp_rem)) begin
37       $display ("===== > PASSED");
38       pass = pass + 1;
39     end else begin
40       $display ("===== > FAILED");
41       fail = fail + 1;
42     end
43   end
44 endtask
45
46 task test (input [31:0] div_in, input [31:0] dvsr);
47   begin
48     divi();
49
50
51
146

```

```

47      $display ("[TEST]    Time = %0t | dividend = %0d, divisor = %0d
48          ", $time, div_in, dvsr);
49      divi();
50
51      dividend = div_in;
52      divisor  = dvsr;
53      #10;
54  end
55 endtask
56
57 initial begin
58     pass = 0;
59     fail = 0;
60     #10;
61
62     test (32'd4, 32'd2);
63     check (32'd2, 32'd0);
64
65     test (32'd4, 32'd4);
66     check (32'd1, 32'd0);
67
68     test (32'd10, 32'd4);
69     check (32'd2, 32'd2);
70
71     test (32'd2, 32'd4);
72     check (32'd0, 32'd2);
73
74     test (32'd100, 32'd1);
75     check (32'd100, 32'd0);
76
77     test (32'd100, 32'd7);
78     check (32'd14, 32'd2);
79
80     test (32'd0, 32'd50);
81     check (32'd0, 32'd0);
82
83     test (32'hFFFF_FFFF, 32'd1);
84     check (32'hFFFF_FFFF, 32'd0);
85
86     test (32'hFFFF_FFFF, 32'hFFFF_FFFF);
87     check (32'd1, 32'd0);
88
89     test (32'hFFFF_FFFF, 32'd2);
90     check (32'd2147483647, 32'd1);
91
92     test (32'h8000_0000, 32'd2);
93     check (32'd1073741824, 32'd0);
94
95     test (32'd123456789, 32'd987);
96     check (32'd125082, 32'd855);
97
98     test (32'd400000, 32'd399999);
99     check (32'd1, 32'd1);

```

```

99
100    test (32'd1024, 32'd1025);
101    check (32'd0, 32'd1024);

102
103    msg ("SUMMARY");
104    $display ("TOTAL TESTS : %0d", pass + fail);
105    $display ("Total PASSED: %0d", pass);
106    $display ("Total FAILED: %0d", fail);

107    if (fail == 0)
108        $display ("=====> ALL TESTS PASSED");
109    else
110        $display ("=====> SOME TESTS FAILED");

111
112    #100;
113    $finish;
114
115 end
116 endmodule

```

Program 11: Testbench implementation of divider_unsigned module.

5.3 Testbench results

All test cases executed successfully for both modules, with each marked as PASSED. This outcome confirms that the test modules behave as intended and that the implemented RTL designs meets the expected functionality.

```

1  # -----
2  # [TEST]  Time = 10 | dividend_in = 80000000, divisor = 2,
3  #           remainder_in = 0, quotient_in = 8
4  #
5  # -----
6  # [OUTPUT] Time = 20 | remainder_out = 1, quotient_out = 16,
7  #           dividend_out = 00000000
8  # [EXPECT] Time = 20 | remainder_out = 1, quotient_out = 16,
9  #           dividend_out = 00000000
10 # ======> PASSED
11 #
12 # -----
13 # [TEST]  Time = 20 | dividend_in = 80000000, divisor = 1,
14 #           remainder_in = 0, quotient_in = 8
15 #
16 # -----
17 # [OUTPUT] Time = 30 | remainder_out = 0, quotient_out = 17,
18 #           dividend_out = 00000000
19 # [EXPECT] Time = 30 | remainder_out = 0, quotient_out = 17,
20 #           dividend_out = 00000000
21 # ======> PASSED
22 #
23 # -----
24 # [TEST]  Time = 30 | dividend_in = 4, divisor = 3, remainder_in = 2,
25 #           quotient_in = 1
26 #
27 # -----
28 # [OUTPUT] Time = 40 | remainder_out = 1, quotient_out = 3,
29 #           dividend_out = 00000008
30 # [EXPECT] Time = 40 | remainder_out = 1, quotient_out = 3,
31 #           dividend_out = 00000008

```

```

18 # =====> PASSED
19 #
20 # [TEST] Time = 40 | dividend_in = 40000000, divisor = 5,
21 # remainder_in = 3, quotient_in = 0
22 #
23 # [OUTPUT] Time = 50 | remainder_out = 1, quotient_out = 1,
24 # dividend_out = 80000000
25 # [EXPECT] Time = 50 | remainder_out = 1, quotient_out = 1,
26 # dividend_out = 80000000
27 # =====> PASSED
28 #
29 # [TEST] Time = 50 | dividend_in = 0, divisor = 10, remainder_in =
30 # 4, quotient_in = 1
31 #
32 # [OUTPUT] Time = 60 | remainder_out = 8, quotient_out = 2,
33 # dividend_out = 00000000
34 # [EXPECT] Time = 60 | remainder_out = 8, quotient_out = 2,
35 # dividend_out = 00000000
36 # =====> PASSED
37 #
38 # [TEST] Time = 60 | dividend_in = a0000000, divisor = 3,
39 # remainder_in = 2, quotient_in = 5
40 #
41 # [OUTPUT] Time = 70 | remainder_out = 2, quotient_out = 11,
42 # dividend_out = 40000000
43 # [EXPECT] Time = 70 | remainder_out = 2, quotient_out = 11,
44 # dividend_out = 40000000
45 # =====> PASSED
46 #
47 # [TEST] Time = 70 | dividend_in = 80000000, divisor = 6,
48 # remainder_in = 2, quotient_in = 0
49 #
50 # [OUTPUT] Time = 80 | remainder_out = 5, quotient_out = 0,
51 # dividend_out = 00000000
52 # [EXPECT] Time = 80 | remainder_out = 5, quotient_out = 0,
53 # dividend_out = 00000000
# =====> PASSED
#
# [TEST] Time = 80 | dividend_in = 80000000, divisor = 5,
# remainder_in = 2, quotient_in = 0
#
# [OUTPUT] Time = 90 | remainder_out = 0, quotient_out = 1,
# dividend_out = 00000000
# [EXPECT] Time = 90 | remainder_out = 0, quotient_out = 1,
# dividend_out = 00000000
# =====> PASSED
#
# [TEST] Time = 90 | dividend_in = ffffffff, divisor = 4294967295,
# remainder_in = 4294967295, quotient_in = 4294967295
#
# [OUTPUT] Time = 100 | remainder_out = 0, quotient_out = 4294967295,
# dividend_out = fffffffe
# [EXPECT] Time = 100 | remainder_out = 0, quotient_out = 4294967295,

```

```

      dividend_out = ffffffe
54 # =====> PASSED
55 #
56 # [TEST]    Time = 100 | dividend_in = 12345678, divisor = 100,
57 #           remainder_in = 200, quotient_in = 42
58 #
59 # [OUTPUT]   Time = 110 | remainder_out = 300, quotient_out = 85,
60 #           dividend_out = 2468acf0
61 # [EXPECT]   Time = 110 | remainder_out = 300, quotient_out = 85,
62 #           dividend_out = 2468acf0
63 # =====> PASSED
64 #
65 # [TEST]    Time = 110 | dividend_in = 12345678, divisor = 500,
66 #           remainder_in = 200, quotient_in = 42
67 #
68 # [OUTPUT]   Time = 120 | remainder_out = 400, quotient_out = 84,
69 #           dividend_out = 2468acf0
70 # [EXPECT]   Time = 120 | remainder_out = 400, quotient_out = 84,
71 #           dividend_out = 2468acf0
72 # =====> PASSED
73 #
74 # [TEST]    Time = 120 | dividend_in = 0, divisor = 1, remainder_in =
75 #           0, quotient_in = 123
76 #
77 # [OUTPUT]   Time = 130 | remainder_out = 0, quotient_out = 246,
78 #           dividend_out = 00000000
79 # [EXPECT]   Time = 130 | remainder_out = 0, quotient_out = 246,
80 #           dividend_out = 00000000
81 # =====> PASSED
82 #
83 # [TEST]    Time = 130 | dividend_in = 80000000, divisor = 4294967295,
84 #           remainder_in = 0, quotient_in = 0
85 #
86 # [OUTPUT]   Time = 140 | remainder_out = 1, quotient_out = 0,
87 #           dividend_out = 00000000
# [EXPECT]   Time = 140 | remainder_out = 1, quotient_out = 0,
#           dividend_out = 00000000
# =====> PASSED
# -----
# SUMMARY
# -----
# TOTAL TESTS : 13
# Total PASSED: 13
# Total FAILED: 0
# =====> ALL TESTS PASSED
# ** Note: $finish : ../../tb/tb_divu_1iter.v(114)
#     Time: 240 ns  Iteration: 0  Instance: /tb_divu_1iter

```

Simulation 4: Testbench results of the divu_1iter module.

```

1 # -----
2 # [TEST]    Time = 10 | dividend = 4, divisor = 2
3 #
4 # [OUTPUT]   Time = 20 | quotient = 2, remainder = 0

```

```

5 # [EXPECT] Time = 20 | quotient = 2, remainder = 0
6 # =====> PASSED
7 #
8 # [TEST] Time = 20 | dividend = 4, divisor = 4
9 #
10 # [OUTPUT] Time = 30 | quotient = 1, remainder = 0
11 # [EXPECT] Time = 30 | quotient = 1, remainder = 0
12 # =====> PASSED
13 #
14 # [TEST] Time = 30 | dividend = 10, divisor = 4
15 #
16 # [OUTPUT] Time = 40 | quotient = 2, remainder = 2
17 # [EXPECT] Time = 40 | quotient = 2, remainder = 2
18 # =====> PASSED
19 #
20 # [TEST] Time = 40 | dividend = 2, divisor = 4
21 #
22 # [OUTPUT] Time = 50 | quotient = 0, remainder = 2
23 # [EXPECT] Time = 50 | quotient = 0, remainder = 2
24 # =====> PASSED
25 #
26 # [TEST] Time = 50 | dividend = 100, divisor = 1
27 #
28 # [OUTPUT] Time = 60 | quotient = 100, remainder = 0
29 # [EXPECT] Time = 60 | quotient = 100, remainder = 0
30 # =====> PASSED
31 #
32 # [TEST] Time = 60 | dividend = 100, divisor = 7
33 #
34 # [OUTPUT] Time = 70 | quotient = 14, remainder = 2
35 # [EXPECT] Time = 70 | quotient = 14, remainder = 2
36 # =====> PASSED
37 #
38 # [TEST] Time = 70 | dividend = 0, divisor = 50
39 #
40 # [OUTPUT] Time = 80 | quotient = 0, remainder = 0
41 # [EXPECT] Time = 80 | quotient = 0, remainder = 0
42 # =====> PASSED
43 #
44 # [TEST] Time = 80 | dividend = 4294967295, divisor = 1
45 #
46 # [OUTPUT] Time = 90 | quotient = 4294967295, remainder = 0
47 # [EXPECT] Time = 90 | quotient = 4294967295, remainder = 0
48 # =====> PASSED
49 #
50 # [TEST] Time = 90 | dividend = 4294967295, divisor = 4294967295
51 #
52 # [OUTPUT] Time = 100 | quotient = 1, remainder = 0
53 # [EXPECT] Time = 100 | quotient = 1, remainder = 0
54 # =====> PASSED
55 #
56 # [TEST] Time = 100 | dividend = 4294967295, divisor = 2
57 #

```

```

58 # [OUTPUT] Time = 110 | quotient = 2147483647, remainder = 1
59 # [EXPECT] Time = 110 | quotient = 2147483647, remainder = 1
60 # =====> PASSED
61 #
62 # -----
63 # [TEST] Time = 110 | dividend = 2147483648, divisor = 2
64 # -----
65 # [OUTPUT] Time = 120 | quotient = 1073741824, remainder = 0
66 # [EXPECT] Time = 120 | quotient = 1073741824, remainder = 0
67 # =====> PASSED
68 #
69 # -----
70 # [TEST] Time = 120 | dividend = 123456789, divisor = 987
71 # -----
72 # [OUTPUT] Time = 130 | quotient = 125082, remainder = 855
73 # [EXPECT] Time = 130 | quotient = 125082, remainder = 855
74 # =====> PASSED
75 #
76 # -----
77 # [TEST] Time = 130 | dividend = 400000, divisor = 399999
78 # -----
79 # [OUTPUT] Time = 140 | quotient = 1, remainder = 1
80 # [EXPECT] Time = 140 | quotient = 1, remainder = 1
81 # =====> PASSED
82 #
83 # -----
84 # [TEST] Time = 140 | dividend = 1024, divisor = 1025
85 # -----
86 # [OUTPUT] Time = 150 | quotient = 0, remainder = 1024
87 # [EXPECT] Time = 150 | quotient = 0, remainder = 1024
88 # =====> PASSED
89 #
90 # -----
91 # SUMMARY
92 #
93 # TOTAL TESTS : 14
# Total PASSED: 14
# Total FAILED: 0
# =====> ALL TESTS PASSED
# ** Note: $finish : ../../tb/tb_divider_unsigned.v(113)
#     Time: 250 ns Iteration: 0 Instance: /tb_divider_unsigned

```

Simulation 5: Testbench results of the divider_unsigned module.