

VIETNAM NATIONAL UNIVERSITY - HO CHI MINH CITY
HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY
Faculty of Computer Science and Engineering



LAB 3
INTRODUCTION TO SYSTEM ON CHIP
LABORATORY REPORT
Instructor: Pham Kieu Nhat Anh

Class: CC01
Name: Hoang Thuy Tram
Student ID: 2353202

Ho Chi Minh city, December 2025

Contents

1	Github	1
2	Overview	1
3	RTL implementation	2
4	Testbench	14
4.1	RegFile testbench	14
4.2	Processor testbench	18
5	Testbench results	23
5.1	RegFile testbench results	23
5.2	Processor testbench results	33
6	Simulation waveform	35
6.1	RegFile simulation waveform	35
6.2	Processor simulation waveform	36
7	Timing closure and Resource utilization	38
7.1	Timing closure	38
7.2	Resource utilization	39

1 Github

The Lab 3 project files (RTL source code, testbenches, simulation scripts) are located in the Lab03 folder. They are available at the following repository: <https://github.com/trxmhoang/SoC.git>

2 Overview

The `DatpathSingleCycle.v` file details the design and implementation of a 32-bit single-cycle RISC-V processor using Verilog. The processor implements the RV32I base integer instruction set. The architecture is single-cycle, meaning every instruction completes its execution within one clock cycle, whether it is a simple addition or a complex memory access. The design consists of four main modules:

- **RegFile:** The register file contains 32 general-purpose registers.
 - The RISC-V architecture specifies 32 registers (x0 to x31), each 32 bits wide. **RegFile** module is used to implement this storage.
 - In RISC-V, register x0 is hardwired to zero. Therefore, the module also checks if the destination register is x0 to ensure that any instruction trying to write to x0 effectively does nothing.
 - Writing to registers happens on the **posedge clk**, ensuring state updates are synchronized.
 - Reading is combination, which happens immediately, allowing the datapath to use register values within the same clock cycle.
- **DatpathSingleCycle:** The core logic that handles instruction decoding, ALU operations and control flow. It is the “brain” of the processor.
 - The 32-bit instruction received from instruction memory is sliced into specific fields. This splitting allows the processor to immediately identify the source registers (rs1, rs2), the destination register (rd) and the operation codes (opcode, funct3, funct7).
 - RISC-V instructions pack immediate values (constants) differently depending on the instruction type (I, S, B, J). The code extracts these bits and performs sign extension, replicates the most significant bit (MSB) to fill the upper bits of the 32-bit word, allowing the processor to handle negative numbers correctly in arithmetic operations.
 - The core logic is implemented in a large combinatorial **always @(*)** block. This block acts as the control unit. Based on the **inst_opcode**, the processor determines ALU operations (add, subtract, XOR, etc), memory access (read/write to memory via **OpLoad**, **OpStore**) and branching (whether to change the Program Counter (**pcNext**) based on the comparisons).
- **MemorySingleCycle:** A unified memory module for both instructions and data.
 - The memory module simulates a Von Neumann architecture physically with one memory array, but behaves like a Harvard architecture with separate ports for instruction and data to support single-cycle execution.
 - While the memory array is 32-bits wide, RISC-V addresses memory by byte. The code handles this using **store_we_dmem**, a 4-bit write enable mask. This allows writing individual bytes (SB), half-word (SH) or full words (SW) without corrupting neighbors.

- Processor: The top-level module connecting the datapath and memory.

In this design, we use `cla` module from Lab 2 to implement the `addi`, `add`, and `sub` instructions for fast addition and subtraction. Other situations where we need to add things, such as incrementing the PC or computing branch targets, we will use the `+` operator. Module `divu_liter`, `divider_unsigned` from Lab 1 are also used to replace `/`, `%` operators that handle division and remainder operations.

The logic is designed so that `pcCurrent` updates exactly once per clock edge. In the time between clock edges, the signal propagates through:

- Instruction memory fetch
- Register read
- ALU execution
- Data memory access
- Register write back

This design is conceptually simple and easy to debug. The CPI (Cycles Per Instruction) is exactly 1. However, the clock frequency is limited by the longest possible path (usually a Load instruction), making it slower than pipelined architectures in terms of absolute time.

3 RTL implementation

The provided Verilog code successfully implements a functional subset of the RISC-V 32-bit instruction set. By modularizing the design into Datapath, Control (embedded in Datapath) and Memory, the system achieves a clear separation of concerns. The use of combinatorial logic for instruction decoding ensures that the processor can react to new instructions immediately within the single clock cycle, satisfying the requirements of the architecture.

```

1  `timescale 1ns / 1ns
2
3  // registers are 32 bits in RV32
4  `define REG_SIZE 31
5
6  // RV opcodes are 7 bits
7  `define OPCODE_SIZE 6
8
9  // Don't forget your previous ALUs
10 /* `include "divider_unsigned.v"
11 `include "cla.v" */
12
13 module RegFile (
14     input      [4:0] rd,
15     input      ['REG_SIZE:0] rd_data,
16     input      [4:0] rs1,
17     output reg ['REG_SIZE:0] rs1_data,
18     input      [4:0] rs2,
19     output reg ['REG_SIZE:0] rs2_data,
20     input      clk,

```

```

21     input                                we,
22     input                                rst
23 );
24     localparam NumRegs = 32;
25     reg ['REG_SIZE:0] regs[0:NumRegs-1];
26     integer i;
27
28     // TODO: your code here
29     always @(posedge clk or posedge rst) begin
30         if (rst) begin
31             for (i = 0; i < NumRegs; i = i + 1) begin
32                 regs[i] <= 0;
33             end
34         end else if (we && (rd != 0)) begin
35             regs[rd] <= rd_data;
36         end
37     end
38
39     always @(*) begin
40         rs1_data = (rs1 == 0) ? 32'd0 : regs[rs1];
41         rs2_data = (rs2 == 0) ? 32'd0 : regs[rs2];
42     end
43 endmodule
44
45 module DatapathSingleCycle (
46     input                                clk,
47     input                                rst,
48     output reg                            halt,
49     output ['REG_SIZE:0] pc_to_imem,
50     input ['REG_SIZE:0] inst_from_imem,
51     // addr_to_dmem is a read-write port
52     output reg ['REG_SIZE:0] addr_to_dmem,
53     input ['REG_SIZE:0] load_data_from_dmem,
54     output reg ['REG_SIZE:0] store_data_to_dmem,
55     output reg [3:0] store_we_to_dmem
56 );
57
58     // components of the instruction
59     wire [6:0] inst_func7;
60     wire [4:0] inst_rs2;
61     wire [4:0] inst_rs1;
62     wire [2:0] inst_func3;
63     wire [4:0] inst_rd;
64     wire ['OPCODE_SIZE:0] inst_opcode;
65
66     // split R-type instruction - see section 2.2 of RiscV spec
67     assign {inst_func7, inst_rs2, inst_rs1, inst_func3, inst_rd,
68             inst_opcode} = inst_from_imem;
69
70     // setup for I, S, B & J type instructions
71     // I - short immediates and loads
72     wire [11:0] imm_i;
73     assign imm_i = inst_from_imem[31:20];

```

```

73 wire [ 4:0] imm_shamt = inst_from_imem[24:20];
74
75 // S - stores
76 wire [11:0] imm_s;
77 assign imm_s = {inst_funct7, inst_rd};
78
79 // B - conditionals
80 wire [12:0] imm_b;
81 assign {imm_b[12], imm_b[10:1], imm_b[11], imm_b[0]} = {inst_funct7,
82     inst_rd, 1'b0};
83
84 // J - unconditional jumps
85 wire [20:0] imm_j;
86 assign {imm_j[20], imm_j[10:1], imm_j[11], imm_j[19:12], imm_j[0]} =
87     {inst_from_imem[31:12], 1'b0};
88
89 wire ['REG_SIZE:0] imm_i_sext = {{20{imm_i[11]}}, imm_i[11:0]};
90 wire ['REG_SIZE:0] imm_s_sext = {{20{imm_s[11]}}, imm_s[11:0]};
91 wire ['REG_SIZE:0] imm_b_sext = {{19{imm_b[12]}}, imm_b[12:0]};
92 wire ['REG_SIZE:0] imm_j_sext = {{11{imm_j[20]}}, imm_j[20:0]};
93
94 // opcodes - see section 19 of RiscV spec
95 localparam ['OPCODE_SIZE:0] OpLoad      = 7'b00_000_11;
96 localparam ['OPCODE_SIZE:0] OpStore     = 7'b01_000_11;
97 localparam ['OPCODE_SIZE:0] OpBranch    = 7'b11_000_11;
98 localparam ['OPCODE_SIZE:0] OpJalr      = 7'b11_001_11;
99 localparam ['OPCODE_SIZE:0] OpMiscMem   = 7'b00_011_11;
100 localparam ['OPCODE_SIZE:0] OpJal       = 7'b11_011_11;
101
102 localparam ['OPCODE_SIZE:0] OpRegImm     = 7'b00_100_11;
103 localparam ['OPCODE_SIZE:0] OpRegReg     = 7'b01_100_11;
104 localparam ['OPCODE_SIZE:0] OpEnviron    = 7'b11_100_11;
105
106 localparam ['OPCODE_SIZE:0] OpAuipc      = 7'b00_101_11;
107 localparam ['OPCODE_SIZE:0] OpLui        = 7'b01_101_11;
108
109 wire inst_lui      = (inst_opcode == OpLui      );
110 wire inst_auipc     = (inst_opcode == OpAuipc     );
111 wire inst_jal       = (inst_opcode == OpJal       );
112 wire inst_jalr      = (inst_opcode == OpJalr      );
113
114 wire inst_beq       = (inst_opcode == OpBranch ) & (inst_from_imem
115     [14:12] == 3'b000);
116 wire inst_bne       = (inst_opcode == OpBranch ) & (inst_from_imem
117     [14:12] == 3'b001);
118 wire inst_blt       = (inst_opcode == OpBranch ) & (inst_from_imem
119     [14:12] == 3'b100);
120 wire inst_bge       = (inst_opcode == OpBranch ) & (inst_from_imem
121     [14:12] == 3'b101);
122 wire inst_bltu      = (inst_opcode == OpBranch ) & (inst_from_imem
123     [14:12] == 3'b110);
124 wire inst_bgeu      = (inst_opcode == OpBranch ) & (inst_from_imem
125     [14:12] == 3'b111);

```

```

118
119 wire inst_lb      = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b000);
120 wire inst_lh      = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b001);
121 wire inst_lw      = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b010);
122 wire inst_lbu     = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b100);
123 wire inst_lhu     = (inst_opcode == OpLoad   ) & (inst_from_imem
    [14:12] == 3'b101);
124
125 wire inst_sb      = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b000);
126 wire inst_sh      = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b001);
127 wire inst_sw      = (inst_opcode == OpStore  ) & (inst_from_imem
    [14:12] == 3'b010);
128
129 wire inst_addi     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b000);
130 wire inst_slti     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b010);
131 wire inst_sltiu    = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b011);
132 wire inst_xori     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b100);
133 wire inst_ori      = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b110);
134 wire inst_andi     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b111);
135
136 wire inst_slli     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b001) & (inst_from_imem[31:25] == 7'd0      );
137 wire inst_srli     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'd0      );
138 wire inst_srai     = (inst_opcode == OpRegImm ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'b0100000);
139
140 wire inst_add      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b000) & (inst_from_imem[31:25] == 7'd0      );
141 wire inst_sub      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b000) & (inst_from_imem[31:25] == 7'b0100000);
142 wire inst_sll      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b001) & (inst_from_imem[31:25] == 7'd0      );
143 wire inst_slt      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b010) & (inst_from_imem[31:25] == 7'd0      );
144 wire inst_sltu     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b011) & (inst_from_imem[31:25] == 7'd0      );
145 wire inst_xor      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b100) & (inst_from_imem[31:25] == 7'd0      );
146 wire inst_srl      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'd0      );

```

```

147 wire inst_sra      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b101) & (inst_from_imem[31:25] == 7'b0100000);
148 wire inst_or       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b110) & (inst_from_imem[31:25] == 7'd0      );
149 wire inst_and      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [14:12] == 3'b111) & (inst_from_imem[31:25] == 7'd0      );
150
151 wire inst_mul       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b000      );
152 wire inst_mulh      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b001      );
153 wire inst_mulhsu    = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b010      );
154 wire inst_mulhu     = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b011      );
155 wire inst_div       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b100      );
156 wire inst_divu      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b101      );
157 wire inst_rem       = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b110      );
158 wire inst_remu      = (inst_opcode == OpRegReg ) & (inst_from_imem
    [31:25] == 7'd1  ) & (inst_from_imem[14:12] == 3'b111      );
159
160 wire inst_ecall     = (inst_opcode == OpEnviron) & (inst_from_imem
    [31:7]  == 25'd0  );
161 wire inst_fence     = (inst_opcode == OpMiscMem);
162
163 // program counter
164 reg ['REG_SIZE:0] pcNext, pcCurrent;
165 always @(posedge clk) begin
166     if (rst) begin
167         pcCurrent <= 32'd0;
168     end else begin
169         pcCurrent <= pcNext;
170     end
171 end
172 assign pc_to_imem = pcCurrent;
173
174 // cycle/inst._from_imem counters
175 reg ['REG_SIZE:0] cycles_current, num_inst_current;
176 always @(posedge clk) begin
177     if (rst) begin
178         cycles_current <= 0;
179         num_inst_current <= 0;
180     end else begin
181         cycles_current <= cycles_current + 1;
182         if (!rst) begin
183             num_inst_current <= num_inst_current + 1;
184         end
185     end
186 end
187

```



```

188 // NOTE: don't rename your RegFile instance as the tests expect it
    to be 'rf'
189 // TODO: you will need to edit the port connections, however.
190 wire ['REG_SIZE:0] rs1_data;
191 wire ['REG_SIZE:0] rs2_data;
192 reg ['REG_SIZE:0] rd_data;
193 reg rf_we;
194
195 RegFile rf (
196     .clk      (clk),
197     .rst      (rst),
198     .we       (rf_we),
199     .rd       (inst_rd),
200     .rd_data  (rd_data),
201     .rs1      (inst_rs1),
202     .rs2      (inst_rs2),
203     .rs1_data (rs1_data),
204     .rs2_data (rs2_data)
205 );
206
207 wire [31:0] cla_res, cla_op_b, cla_op_b_raw;
208 wire cla_cin;
209
210 assign cla_op_b_raw = (inst_opcode == OpRegImm) ? imm_i_sext :
    rs2_data;
211 assign cla_op_b = inst_sub ? ~cla_op_b_raw : cla_op_b_raw;
212 assign cla_cin = inst_sub ? 1'b1 : 1'b0;
213
214 cla u_cla (
215     .a  (rs1_data),
216     .b  (cla_op_b),
217     .cin (cla_cin),
218     .sum (cla_res)
219 );
220
221 wire [31:0] div_op_a, div_op_b;
222 wire is_signed_div;
223 assign is_signed_div = inst_div | inst_rem;
224 assign div_op_a = (is_signed_div & rs1_data[31]) ? (~rs1_data + 1) :
    rs1_data;
225 assign div_op_b = (is_signed_div & rs2_data[31]) ? (~rs2_data + 1) :
    rs2_data;
226
227 wire [31:0] div_quot_raw, div_rem_raw;
228 divider_unsigned u_div (
229     .dividend  (div_op_a),
230     .divisor    (div_op_b),
231     .quotient   (div_quot_raw),
232     .remainder  (div_rem_raw)
233 );
234
235 reg [31:0] div_res;
236 always @(*) begin

```

```

237     if (inst_div || inst_divu) begin
238         if (rs2_data == 0) begin
239             div_res = 32'hFFFF_FFFF;
240         end else if (inst_div && (rs1_data == 32'h8000_0000) && (
241             rs2_data == 32'hFFFF_FFFF)) begin
242             div_res = 32'h8000_0000;
243         end else if (is_signed_div && (rs1_data[31] ^ rs2_data[31]))
244             begin
245                 div_res = ~div_quot_raw + 32'd1;
246             end else begin
247                 div_res = div_quot_raw;
248             end
249         end else begin // rem or remu
250             if (rs2_data == 0) begin
251                 div_res = rs1_data;
252             end else if (inst_rem && (rs1_data == 32'h8000_0000) && (
253                 rs2_data == 32'hFFFF_FFFF)) begin
254                 div_res = 32'd0;
255             end else if (is_signed_div && (rs1_data[31])) begin
256                 div_res = ~div_rem_raw + 32'd1;
257             end else begin
258                 div_res = div_rem_raw;
259             end
260         end
261     end
262
263     wire [63:0] mul_u, mul_s, mul_su;
264     assign mul_u = {32'b0, rs1_data} * {32'b0, rs2_data};
265     assign mul_s = $signed(rs1_data) * $signed(rs2_data);
266     assign mul_su = $signed(rs1_data) * $signed({1'b0, rs2_data});
267
268     reg take_branch;
269     always @(*) begin
270         case (inst_funct3)
271             3'b000: take_branch = (rs1_data == rs2_data);
272                     // beq
273             3'b001: take_branch = (rs1_data != rs2_data);
274                     // bne
275             3'b100: take_branch = ($signed(rs1_data) < $signed(rs2_data));
276                     // blt
277             3'b101: take_branch = ($signed(rs1_data) >= $signed(rs2_data));
278                     // bge
279             3'b110: take_branch = (rs1_data < rs2_data);
280                     // bltu
281             3'b111: take_branch = (rs1_data >= rs2_data);
282                     // bgeu
283             default: take_branch = 1'b0;
284         endcase
285     end
286
287     reg [31:0] load_data;
288     always @(*) begin
289         case (addr_to_dmem[1:0])

```

```

281     2'b00: load_data = load_data_from_dmem;
282     2'b01: load_data = load_data_from_dmem >> 8;
283     2'b10: load_data = load_data_from_dmem >> 16;
284     2'b11: load_data = load_data_from_dmem >> 24;
285     endcase
286 end
287
288 reg illegal_inst;
289
290 always @(*) begin
291     illegal_inst = 1'b0;
292     pcNext = pcCurrent + 4;
293     rf_we = 0;
294     rd_data = 0;
295     halt = 0;
296     addr_to_dmem = 0;
297     store_data_to_dmem = 0;
298     store_we_to_dmem = 0;
299
300     case (inst_opcode)
301         OpLui: begin
302             // TODO: start here by implementing lui
303             rf_we = 1;
304             rd_data = {inst_from_imem[31:12], 12'b0};
305         end
306
307         OpAuipc: begin
308             rf_we = 1;
309             rd_data = pcCurrent + {inst_from_imem[31:12], 12'b0};
310         end
311
312         OpJal: begin
313             rf_we = 1;
314             rd_data = pcCurrent + 4;
315             pcNext = pcCurrent + imm_j_sext;
316         end
317
318         OpJalr: begin
319             rf_we = 1;
320             rd_data = pcCurrent + 4;
321             pcNext = (rs1_data + imm_i_sext) & ~32'd1;
322         end
323
324         OpBranch: begin
325             if (take_branch) begin
326                 pcNext = pcCurrent + imm_b_sext;
327             end
328         end
329
330         OpLoad: begin
331             rf_we = 1;
332             addr_to_dmem = rs1_data + imm_i_sext;
333

```

```

334     case (inst_funct3)
335         3'b000: rd_data = {{24{load_data[7]}}}, load_data[7:0]]; //
                 lb
336         3'b001: rd_data = {{16{load_data[15]}}}, load_data[15:0]]; //
                 lh
337         3'b010: rd_data = load_data; //
                 lw
338         3'b100: rd_data = {24'b0, load_data[7:0]]; //
                 lbu
339         3'b101: rd_data = {16'b0, load_data[15:0]]; //
                 lhu
340     endcase
341 end
342
343 OpStore: begin
344     addr_to_dmem = rs1_data + imm_s_sext;
345     store_data_to_dmem = rs2_data << (addr_to_dmem[1:0] * 8);
346
347     case (inst_funct3)
348         3'b000: store_we_to_dmem = 4'b0001 << addr_to_dmem[1:0]; //
                 sb
349         3'b001: store_we_to_dmem = 4'b0011 << addr_to_dmem[1:0]; //
                 sh
350         3'b010: store_we_to_dmem = 4'b1111; //
                 sw
351     endcase
352 end
353
354 OpRegImm: begin
355     rf_we = 1;
356     case (inst_funct3)
357         3'b000: rd_data = cla_res; // addi
358         3'b010: rd_data = ($signed(rs1_data) < $signed(imm_i_sext))
                 ? 32'd1 : 32'd0; // slti
359         3'b011: rd_data = (rs1_data < imm_i_sext) ? 32'd1 : 32'd0;
                 // sltiu
360         3'b100: rd_data = rs1_data ^ imm_i_sext;
                 // xori
361         3'b110: rd_data = rs1_data | imm_i_sext;
                 // ori
362         3'b111: rd_data = rs1_data & imm_i_sext;
                 // andi
363         3'b001: rd_data = rs1_data << imm_shamt;
                 // slli
364         3'b101: begin
365             if (inst_funct7 == 7'd0) begin
366                 rd_data = rs1_data >> imm_shamt; // srli
367             end else begin
368                 rd_data = $signed(rs1_data) >>> imm_shamt; // srai
369             end
370         end
371     endcase
372 end

```

```

373
374 OpRegReg: begin
375     rf_we = 1;
376     if (inst_funct7 == 7'd1) begin
377         case (inst_funct3)
378             3'b000: rd_data = rs1_data * rs2_data;           // mul
379             3'b001: rd_data = mul_s[63:32];                 // mulh
380             3'b010: rd_data = mul_su[63:32];                 //
381                     mulhsu
382             3'b011: rd_data = mul_u[63:32];                 //
383                     mulhu
384             3'b100, 3'b101, 3'b110, 3'b111: rd_data = div_res; // div,
385                     divu, rem, remu
386         endcase
387     end else begin
388         case (inst_funct3)
389             3'b000: rd_data = cla_res;
390                     // add,
391                     sub
392             3'b001: rd_data = rs1_data << rs2_data[4:0];
393                     // sll
394             3'b010: rd_data = ($signed(rs1_data) < $signed(rs2_data))
395                     ? 32'd1 : 32'd0; // slt
396             3'b011: rd_data = (rs1_data < rs2_data) ? 32'd1 : 32'd0;
397                     // sltu
398             3'b100: rd_data = rs1_data ^ rs2_data;
399                     // xor
400             3'b101: begin
401                 if (inst_funct7[5]) rd_data = $signed(rs1_data) >>>
402                     rs2_data[4:0]; // sra
403                 else rd_data = rs1_data >> rs2_data[4:0];
404                     // srl
405             end
406             3'b110: rd_data = rs1_data | rs2_data;
407                     // or
408             3'b111: rd_data = rs1_data & rs2_data;
409                     // and
410         endcase
411     end
412 end
413
414 OpEnviron: begin
415     if (inst_from_imem[31:7] == 25'd0) halt = 1'b1; // ecall
416 end
417
418 default: begin
419     illegal_inst = 1'b1;
420 end
421 endcase
422 end
423 endmodule
424
425 /* A memory module that supports 1-cycle reads and writes, with one

```

```

    read-only port
413 * and one read+write port.
414 */
415 module MemorySingleCycle #(
416     parameter NUM_WORDS = 512
417 ) (
418     input                rst,                // rst for both imem
         and dmem
419     input                clock_mem,          // clock for both imem
         and dmem
420     input                ['REG_SIZE:0] pc_to_imem, // must always be
         aligned to a 4B boundary
421     output reg ['REG_SIZE:0] inst_from_imem, // the value at memory
         location pc_to_imem
422     input                ['REG_SIZE:0] addr_to_dmem, // must always be
         aligned to a 4B boundary
423     output reg ['REG_SIZE:0] load_data_from_dmem, // the value at memory
         location addr_to_dmem
424     input                ['REG_SIZE:0] store_data_to_dmem, // the value to be
         written to addr_to_dmem, controlled by store_we_to_dmem
425     // Each bit determines whether to write the corresponding byte of
         store_data_to_dmem to memory location addr_to_dmem.
426     // E.g., 4'b1111 will write 4 bytes. 4'b0001 will write only the
         least-significant byte.
427     input                [        3:0] store_we_to_dmem
428 );
429
430 // memory is arranged as an array of 4B words
431 reg ['REG_SIZE:0] mem_array[0:NUM_WORDS-1];
432
433 // preload instructions to mem_array
434 always @(posedge rst) begin
435     $readmemh("mem_initial_contents.hex", mem_array);
436 end
437
438 localparam AddrMsb = $clog2(NUM_WORDS) + 1;
439 localparam AddrLsb = 2;
440
441 always @(posedge clock_mem) begin
442     inst_from_imem <= mem_array[{pc_to_imem[AddrMsb:AddrLsb]}];
443 end
444
445 always @(negedge clock_mem) begin
446     if (store_we_to_dmem[0]) begin
447         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][7:0] <=
            store_data_to_dmem[7:0];
448     end
449     if (store_we_to_dmem[1]) begin
450         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][15:8] <=
            store_data_to_dmem[15:8];
451     end
452     if (store_we_to_dmem[2]) begin
453         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][23:16] <=

```

```

        store_data_to_dmem[23:16];
454     end
455     if (store_we_to_dmem[3]) begin
456         mem_array[addr_to_dmem[AddrMsb:AddrLsb]][31:24] <=
            store_data_to_dmem[31:24];
457     end
458     // dmem is "read-first": read returns value before the write
459     load_data_from_dmem <= mem_array[{addr_to_dmem[AddrMsb:AddrLsb]}];
460     end
461 endmodule

462
463 /*
464 This shows the relationship between clock_proc and clock_mem. The
    clock_mem is
465 phase-shifted 90    from clock_proc. You could think of one proc cycle
    being
466 broken down into 3 parts. During part 1 (which starts @posedge
    clock_proc)
467 the current PC is sent to the imem. In part 2 (starting @posedge
    clock_mem) we
468 read from imem. In part 3 (starting @negedge clock_mem) we read/write
    memory and
469 prepare register/PC updates, which occur at @posedge clock_proc.
470
471     ----
472 proc: |   | |____
473
474     ----
475 mem:  ___|   |___
476 */
477 module Processor (
478     input  clock_proc,
479     input  clock_mem,
480     input  rst,
481     output halt
482 );
483
484 wire ['REG_SIZE:0] pc_to_imem, inst_from_imem, mem_data_addr,
    mem_data_loaded_value, mem_data_to_write;
485 wire [          3:0] mem_data_we;
486
487 // This wire is set by cocotb to the name of the currently-running
    test, to make it easier
488 // to see what is going on in the waveforms.
489 wire [(8*32)-1:0] test_case;
490
491 MemorySingleCycle #(
    .NUM_WORDS(8192)
492 ) memory (
493     .rst                (rst),
494     .clock_mem          (clock_mem),
495     // imem is read-only
496     .pc_to_imem         (pc_to_imem),
497     .inst_from_imem     (inst_from_imem),

```

```

498 // dmem is read-write
499 .addr_to_dmem      (mem_data_addr),
500 .load_data_from_dmem (mem_data_loaded_value),
501 .store_data_to_dmem  (mem_data_to_write),
502 .store_we_to_dmem    (mem_data_we)
503 );
504
505 DatapathSingleCycle datapath (
506     .clk              (clock_proc),
507     .rst              (rst),
508     .pc_to_imem       (pc_to_imem),
509     .inst_from_imem    (inst_from_imem),
510     .addr_to_dmem      (mem_data_addr),
511     .store_data_to_dmem (mem_data_to_write),
512     .store_we_to_dmem   (mem_data_we),
513     .load_data_from_dmem (mem_data_loaded_value),
514     .halt              (halt)
515 );
516 endmodule

```

Program 1: RTL implementation of the DatapathSingleCycle module.

4 Testbench

4.1 RegFile testbench

This test bench is used to verify the correctness of Register File. It uses two main tasks:

- Task **wr** for simulates a synchronous write operation by driving **we**, **rd** and **rd_data** aligned with the positive clock edge.
- Task **check** to sample the read ports (**rs1_data**, **rs2_data**) on the negative clock edge. This ensures the data from the DUT is stable before comparison.

The test bench provides four distinct tests to validate the correctness of the module:

- Test 1 (x0 verification): To confirm that register x0 is read-only and hardwired to zero.
- Test 2 (Basic read/write sanity check): To confirm basic storage capability.
- Test 3 (Iterative register access): To verify address decoding and reset behavior for all registers. The test generates a random 32-bit integer, which is then written to the register and immediately verified.
- Test 4 (Write all and read back): To ensure that writing to one register does not corrupt data in others. The test filling all registers then use a loop to read them back sequentially.

```

1  `timescale 1ns / 1ps
2  module tb_reg;
3  reg clk, rst, we;
4  reg [4:0] rs1, rs2, rd;
5  reg [31:0] rd_data;
6  wire [31:0] rs1_data, rs2_data;

```



```

7
8 integer i, pass, fail;
9 reg [31:0] wr_val [0:31];
10 reg [31:0] exp_val;
11
12 RegFile dut (
13     .clk (clk),
14     .rst (rst),
15     .we (we),
16     .rs1 (rs1),
17     .rs2 (rs2),
18     .rd (rd),
19     .rd_data (rd_data),
20     .rs1_data (rs1_data),
21     .rs2_data (rs2_data)
22 );
23
24 task divi;
25     $display ("%0s", {80{"-"}});
26 endtask
27
28 task br;
29     $display ("%0s", {80{"="}});
30 endtask
31
32 task msg (input [700:0] txt);
33     begin
34         br();
35         $display ("%0s", txt);
36         br();
37     end
38 endtask
39
40 initial begin
41     clk = 0;
42     forever #5 clk = ~clk;
43 end
44
45 task setup;
46     begin
47         rst = 1;
48         repeat (2) @(posedge clk);
49         #1;
50         rst = 0;
51         we = 0;
52         @(posedge clk);
53     end
54 endtask
55
56 task wr (input [4:0] reg_num, input [31:0] val);
57     begin
58         divi();
59         $display ("[WRITE] Time = %0t | rd = 0x%2h, Data = 0x%2h",

```

```

        $time, reg_num, val);
60     divi();
61
62     @(posedge clk);
63     #1;
64     we = 1;
65     rd = reg_num;
66     rd_data = val;
67
68     @(posedge clk);
69     #1;
70     we = 0;
71
72     end
73 endtask
74
75 task check (input [4:0] reg_num, input [31:0] exp);
76     begin
77         rs1 = reg_num;
78         @(negedge clk);
79         #1;
80         if (rs1_data == exp) begin
81             $display ("[PASS] Time = %0t | rs1 = 0x%2h, Expected = 0x
82             %8h, Output = 0x%8h", $time, reg_num, exp, rs1_data);
83             pass = pass + 1;
84         end else begin
85             $display ("[FAIL] Time = %0t | rs1 = 0x%2h, Expected = 0x
86             %8h, Output = 0x%8h", $time, reg_num, exp, rs1_data);
87             fail = fail + 1;
88         end
89     end
90 endtask
91
92 task check_all (input [4:0] reg1, input [31:0] exp1, input [4:0] reg2,
93     input [31:0] exp2);
94     begin
95         rs1 = reg1;
96         rs2 = reg2;
97         @(negedge clk);
98         #1;
99
100         if (rs1_data == exp1) begin
101             $display ("[PASS] Time = %0t | rs1 = 0x%2h, Expected = 0x
102             %8h, Output = 0x%8h", $time, reg1, exp1, rs1_data);
103             pass = pass + 1;
104         end else begin
105             $display ("[FAIL] Time = %0t | rs1 = 0x%2h, Expected = 0x
106             %8h, Output = 0x%8h", $time, reg1, exp1, rs1_data);
107             fail = fail + 1;
108         end
109
110         if (rs2_data == exp2) begin
111             $display ("[PASS] Time = %0t | rs2 = 0x%2h, Expected = 0x
112             %8h, Output = 0x%8h", $time, reg2, exp2, rs2_data);

```

```

106         pass = pass + 1;
107     end else begin
108         $display ("[FAIL] Time = %0t | rs2 = 0x%2h, Expected = 0x
109             %8h, Output = 0x%8h", $time, reg2, exp2, rs2_data);
110         fail = fail + 1;
111     end
112 endtask
113
114 task init (input [4:0] reg1, input [4:0] reg2, input [31:0] exp);
115     begin
116         @(negedge clk);
117         #1;
118         if (rs1_data != 0 || rs2_data != 0) begin
119             $display ("[FAIL] Time = %0t | rs1 = 0x%2h and rs2 = 0x%2
120                 h should be initialized to 0", $time, reg1, reg2);
121             fail = fail + 1;
122         end else begin
123             $display ("[PASS] Time = %0t | rs1 = 0x%2h and rs2 = 0x%2
124                 h initialized to 0", $time, reg1, reg2);
125             pass = pass + 1;
126         end
127     end
128 endtask
129
130 initial begin
131     pass = 0;
132     fail = 0;
133
134     msg ("TEST 1: WRITE AND READ x0");
135     setup();
136     check (5'd0, 32'd0);
137
138     wr (5'd0, 32'hFFFF_FFFF);
139     check (5'd0, 32'd0);
140
141     wr (5'd0, 32'h1234_5678);
142     check (5'd0, 32'd0);
143
144     msg ("TEST 2: WRITE AND READ x1");
145     setup();
146     wr (5'd1, 32'h1234_5678);
147     check (5'd1, 32'h1234_5678);
148
149     msg ("TEST 3: CHECK ALL REGISTERS");
150     setup();
151     for (i = 1; i < 32; i = i + 1) begin
152         rs1 = i[4:0];
153         rs2 = i[4:0];
154         init (rs1, rs2, 32'd0);
155
156         exp_val = $urandom();

```

```

156         wr (i[4:0], exp_val);
157         check_all (i[4:0], exp_val, i[4:0], exp_val);
158     end
159
160     msg ("TEST 4: WRITE ALL AND READ BACK");
161     setup();
162     wr_val[0] = 32'd0; // x0
163
164     for (i = 1; i < 32; i = i + 1) begin
165         wr_val[i] = $urandom();
166         wr (i[4:0], wr_val[i]);
167     end
168
169     for (i = 1; i < 31; i = i + 1) begin
170         check_all (i[4:0], wr_val[i], i + 1, wr_val[i + 1]);
171     end
172
173     msg ("SUMMARY");
174     $display ("TOTAL TESTS : %0d", pass + fail);
175     $display ("TOTAL PASSED: %0d", pass);
176     $display ("TOTAL FAILED: %0d", fail);
177
178     if (fail == 0)
179         $display ("=====> ALL TESTS PASSED");
180     else if (pass == 0)
181         $display ("=====> ALL TESTS FAILED");
182     else
183         $display ("=====> SOME TESTS FAILED");
184
185     #100;
186     $finish;
187 end
188 endmodule

```

Program 2: Test bench implementation for the RegFile module.

4.2 Processor testbench

The `tb_single` module serves as the top level integration test, validating the interaction between the Datapath, Control unit and Memory. It executes actual RISC-V machine code to ensure the processor complies with the ISA specification.

The testbench generates two clock signals to simulate the timing constraints of a single-cycle architecture:

- `clock_proc`: The main system clock. Register writes and PC updates occur on the rising edge.
- `clock_mem`: A phase-shifted 90 degrees from `clock_proc` clock.

The testbench uses the `load_inst` task to write 32-bit machine code directly into the `mem_array` of the instantiated Memory module. The task `check` uses hierarchical referencing to peek directly into the internal register file in order to validating a CPU requires checking the state of internal general-purpose registers (x1-x31). Since the registers are limited by 32 with one is hardwired to zero values, there is only 31 registers that can store data. Therefore, the

testbench breaks into two tests, Test 1 focuses on ALU operations such as ADD, XOR, SRAI; multiplication and division; use LW and SW to verify the load/store path and executes a JAL to skip instructions, verifying the PC updates non-sequentially. Meanwhile, Test 2 focuses on implement signed and unsigned operations like MULH, MULHU; sub-word access that stores data using SB and reads back using LB and LBU to verifying that the memory masking logic correctly handles sign-extension for 8 and 16-bit values; and a JALR instruction is used to jump to an address calculated at runtime, verifying the register-based jump logic.

```

1  `timescale 1ns / 1ps
2  module tb_single;
3  reg clock_proc, clock_mem, rst;
4  wire halt;
5  integer i, test, timeout, pass, fail;
6
7  Processor dut (
8      .clock_proc (clock_proc),
9      .clock_mem  (clock_mem),
10     .rst         (rst),
11     .halt        (halt)
12 );
13
14 task br;
15     $display ("%0s", {80{"="}});
16 endtask
17
18 task msg (input [700:0] txt);
19     begin
20         br();
21         $display ("%0s", txt);
22         br();
23     end
24 endtask
25
26 task load_inst (input [31:0] addr, input [31:0] inst);
27     begin
28         dut.memory.mem_array[addr >> 2] = inst;
29     end
30 endtask
31
32 task check (input [200:0] txt, input [4:0] reg_num, input [31:0] exp);
33     begin
34         if (dut.datapath.rf.reg[reg_num] === exp) begin
35             $display ("[PASS] Time = %0t | %s | Output x%0d = 0x%8h",
36                 $time, txt, reg_num, dut.datapath.rf.reg[reg_num]);
37             pass = pass + 1;
38         end else begin
39             $display ("[FAIL] Time = %0t | %s | Expect x%0d = 0x%8h |
40                 Output x%0d = 0x%8h", $time, txt, reg_num, exp, reg_num,
41                 dut.datapath.rf.reg[reg_num]);
42             fail = fail + 1;
43         end
44     end
45 endtask

```

```

43
44 initial begin
45     clock_proc = 0;
46     forever #5 clock_proc = ~clock_proc;
47 end
48
49 initial begin
50     #2.5 clock_mem = 0;
51     forever #5 clock_mem = ~clock_mem;
52 end
53
54 initial begin
55     msg ("TEST BEGIN");
56     rst = 1;
57     timeout = 0;
58     pass = 0;
59     fail = 0;
60     test = 0;
61     #20;
62
63     msg ("TEST 1");
64     load_inst (32'h00, 32'h00a00093); // ADDI x1, x0, 10
65     load_inst (32'h04, 32'hffb00113); // ADDI x2, x0, -5
66     load_inst (32'h08, 32'h002081b3); // ADD x3, x1, x2 (5)
67     load_inst (32'h0C, 32'h40208233); // SUB x4, x1, x2 (15)
68     load_inst (32'h10, 32'h0020f2b3); // AND x5, x1, x2 (10)
69     load_inst (32'h14, 32'h0020e333); // OR x6, x1, x2 (-5)
70     load_inst (32'h18, 32'h0020c3b3); // XOR x7, x1, x2 (-15)
71     load_inst (32'h1C, 32'h00209413); // SLLI x8, x1, 2 (40)
72     load_inst (32'h20, 32'h40115493); // SRAI x9, x2, 1 (-3)
73     load_inst (32'h24, 32'h00115513); // SRLI x10, x2, 1
74     load_inst (32'h28, 32'h001125b3); // SLT x11, x2, x1 (1)
75     load_inst (32'h2C, 32'h00113633); // SLTU x12, x2, x1 (0)
76     load_inst (32'h30, 32'h021086b3); // MUL x13, x1, x1 (100)
77     load_inst (32'h34, 32'h0220c733); // DIV x14, x1, x2 (-2)
78     load_inst (32'h38, 32'h0220e7b3); // REM x15, x1, x2 (0)
79     load_inst (32'h3C, 32'h02115833); // DIVU x16, x2, x1
80     load_inst (32'h40, 32'h06302223); // SW x3, 100(x0)
81     load_inst (32'h44, 32'h06402903); // LW x18, 100(x0)
82     load_inst (32'h48, 32'h00108463); // BEQ x1, x1, 8
83     load_inst (32'h4C, 32'h06300993); // (Skipped)
84     load_inst (32'h50, 32'h00100993); // ADDI x19, x0, 1
85     load_inst (32'h54, 32'h00800a6f); // JAL x20, 8
86     load_inst (32'h58, 32'h06300a93); // (Skipped)
87     load_inst (32'h5C, 32'h00200a93); // ADDI x21, x0, 2
88     load_inst (32'h60, 32'h12345b37); // LUI x22, 0x12345
89     load_inst (32'h68, 32'h0050cb93); // XORI x23, x1, 5
90     load_inst (32'h6C, 32'h00f0fc13); // ANDI x24, x1, 0xF
91     load_inst (32'h70, 32'hf006ec93); // ORI x25, x13, 0xFF00
92     load_inst (32'h74, 32'h0283ad13); // SLTI x26, x7, 0x28
93     load_inst (32'h78, 32'hff143d93); // SLTIU x27, x8, 0xffffffff1
94     load_inst (32'h7C, 32'h01309e33); // SLL x28, x1, x19
95     load_inst (32'h80, 32'h01335eb3); // SRL x29, x6, x19

```

```

96 load_inst (32'h84, 32'h41335f33); // SRA x30, x6, x19
97 load_inst (32'h8C, 32'h02337fb3); // REMU x31, x6, x3
98 load_inst(32'h90, 32'h00000073); // HALT
99
100 #10 rst = 0;
101 #1;
102
103 while (!halt && timeout < 1000) begin
104     #10 timeout = timeout + 10;
105 end
106
107 if (test == 0) begin
108     check ("ADDI x1, x0, 10", 1, 10);
109     check ("ADDI x2, x0, -5", 2, -5);
110     check ("ADD x3, x1, x2", 3, 5);
111     check ("SUB x4, x1, x2", 4, 15);
112     check ("AND x5, x1, x2", 5, 10);
113     check ("OR x6, x1, x2", 6, -5);
114     check ("XOR x7, x1, x2", 7, -15);
115     check ("SLLI x8, x1, 2", 8, 40);
116     check ("SRAI x9, x2, 1", 9, -3);
117     check ("SRLI x10, x2, 1", 10, 32'h7fff_fffd);
118     check ("SLT x11, x2, x1", 11, 1);
119     check ("SLTU x12, x2, x1", 12, 0);
120     check ("MUL x13, x1, x1", 13, 100);
121     check ("DIV x14, x1, x2", 14, -2);
122     check ("REM x15, x1, x2", 15, 0);
123     check ("DIVU x16, x2, x1", 16, 32'h1999_9999);
124     check ("LW x18, 100(x0)", 18, 5);
125     check ("ADDI x19, x0, 1", 19, 1);
126     check ("JAL x20, 8", 20, 32'h58); // PC of next instruction
127     check ("ADDI x21, x0, 2", 21, 2);
128     check ("LUI x22, 0x12345", 22, 32'h1234_5000);
129     check ("XORI x23, x1, 5", 23, 32'hf);
130     check ("ANDI x24, x1, 0xF", 24, 32'ha);
131     check ("ORI x25, x13, 0xFF00", 25, 32'hffff_ff64);
132     check ("SLTI x26, x7, 0x28", 26, 1);
133     check ("SLTIU x27, x8, 0xFFFF_FFF1", 27, 1);
134     check ("SLL x28, x1, x19", 28, 20);
135     check ("SRL x29, x6, x19", 29, 32'h7FFF_FFFD);
136     check ("SRA x30, x6, x19", 30, 32'hFFFF_FFFD);
137     check ("REMU x31, x6, x3", 31, 1);
138
139     if (halt) begin
140         $display ("[PASS] HALT asserted.");
141         pass = pass + 1;
142     end else begin
143         $display ("[FAIL] HALT is missing.");
144         fail = fail + 1;
145     end
146 end
147
148 msg ("TEST 2 (REUSED REGISTERS)");

```

```

149  @(negedge clock_proc);
150  rst = 1;
151  test = 1;
152  timeout = 0;
153  #20;
154
155  load_inst (32'h0, 32'hffb00093); // ADDI x1, x0, 0xFFFF_FFFB
156  load_inst (32'h4, 32'h00300113); // ADDI x2, x0, 3
157  load_inst (32'h8, 32'h022091b3); // MULH x3, x1, x2
158  load_inst (32'hC, 32'h0220a233); // MULHSU x4, x1, x2
159  load_inst (32'h10, 32'h0220b2b3); // MULHU x5, x1, x2
160  load_inst (32'h14, 32'he9800313); // ADDI x6, x0, 0xABCD_FE98
161  load_inst (32'h18, 32'h06600223); // SB x6, 100(x0)
162  load_inst (32'h1C, 32'h06601423); // SH x6, 104(x0)
163  load_inst (32'h20, 32'h06400383); // LB x7, 100(x0)
164  load_inst (32'h24, 32'h06801403); // LH x8, 104(x0)
165  load_inst (32'h28, 32'h00831463); // BNE x6, x8, 8
166  load_inst (32'h2C, 32'h06904483); // LBU x9, 105(x0)
167  load_inst (32'h30, 32'h06805503); // LHU x10, 104(x0)
168  load_inst (32'h34, 32'h00a4c463); // BLT x9, x10, 12
169  load_inst (32'h38, 32'h00a4c5b3); // XOR x11, x9, x10 //skipped
170  load_inst (32'h3C, 32'h00a4e5b3); // OR x11, x9, x10 // skipped
171  load_inst (32'h40, 32'h00a485b3); // ADD x11, x9, x10
172  load_inst (32'h44, 32'h00535463); // BGE x6, x5, 8
173  load_inst (32'h48, 32'h0062e663); // BLTU x5, x6, 12
174  load_inst (32'h4C, 32'h00a4e633); // OR x12, x9, x10 // skip then
      turned back by bgeu
175  load_inst (32'h50, 32'h08200767); // JALR x14, 130(x0)
176  load_inst (32'h54, 32'h0004e633); // OR x12, x9, x0
177  load_inst (32'h58, 32'h06c02c23); // SW x12, 120(x0)
178  load_inst (32'h5C, 32'h07802683); // LW x13, 120(x0)
179  load_inst (32'h60, 32'hfe9576e3); // BGEU x10, x9, -20
180  load_inst (32'h82, 32'h00000073); // HALT
181
182  #10 rst = 0;
183  #1;
184  while (!halt && timeout < 1000) begin
185      #10 timeout = timeout + 10;
186  end
187
188  if (test) begin
189      check ("ADDI x1, x0, 0xFFFF_FFFB", 1, 32'hFFFF_FFFB);
190      check ("ADDI x2, x0, 3", 2, 32'h3);
191      check ("MULH x3, x1, x2", 3, 32'hFFFF_FFFF);
192      check ("MULHSU x4, x1, x2", 4, 32'hFFFF_FFFF);
193      check ("MULHU x5, x1, x2", 5, 32'h2);
194      check ("ADDI x6, x0, 0xABCD_FE98", 6, 32'hFFFF_FE98);
195      check ("LB x7, 100(x0)", 7, 32'hFFFF_FF98);
196      check ("LH x8, 104(x0)", 8, 32'hFFFF_FE98);
197      check ("LBU x9, 105(x0)", 9, 32'h0000_00FE);
198      check ("LHU x10, 104(x0)", 10, 32'h0000_FE98);
199      check ("ADD x11, x9, x10", 11, 32'h0000_FF96);
200      check ("OR x12, x9, x10", 12, 32'h0000_FEFE);

```



```

201     check ("LW x13, 120(x0)", 13, 32'h0000_00FE);
202     check ("JALR x14, 130(x0)", 14, 32'h54);
203
204     if (halt) begin
205         $display ("[PASS] HALT asserted.");
206         pass = pass + 1;
207     end else begin
208         $display ("[FAIL] HALT is missing.");
209         fail = fail + 1;
210     end
211 end
212
213 msg ("SUMMARY");
214 $display ("TOTAL TESTS : %0d", pass + fail);
215 $display ("TOTAL PASSED: %0d", pass);
216 $display ("TOTAL FAILED: %0d", fail);
217
218 if (fail == 0)
219     $display ("=====> ALL TESTS PASSED");
220 else if (pass == 0)
221     $display ("=====> ALL TESTS FAILED");
222 else
223     $display ("=====> SOME TESTS FAILED");
224
225 msg ("TEST END");
226
227 #100;
228 $finish;
229 end
230 endmodule

```

Program 3: Test bench implementation for the Processor module.

5 Testbench results

All test cases executed successfully for all tested modules, with each marked as **PASSED**. This outcome confirms that the test modules behave as intended and that the implemented RTL designs meet the expected functionality.

5.1 RegFile testbench results

```

1  # =====
2  # TEST 1: WRITE AND READ x0
3  # =====
4  # [PASS] Time = 31000 | rs1 = 0x00, Expected = 0x00000000, Output = 0
   # x00000000
5  # -----
6  # [WRITE] Time = 31000 | rd = 0x00, Data = 0xffffffff
7  # -----
8  # [PASS] Time = 51000 | rs1 = 0x00, Expected = 0x00000000, Output = 0
   # x00000000
9  # -----

```

```

10 # [WRITE] Time = 51000 | rd = 0x00, Data = 0x12345678
11 # -----
12 # [PASS] Time = 71000 | rs1 = 0x00, Expected = 0x00000000, Output = 0
    x00000000
13 # =====
14 # TEST 2: WRITE AND READ x1
15 # =====
16 # -----
17 # [WRITE] Time = 95000 | rd = 0x01, Data = 0x12345678
18 # -----
19 # [PASS] Time = 121000 | rs1 = 0x01, Expected = 0x12345678, Output =
    0x12345678
20 # =====
21 # TEST 3: CHECK ALL REGISTERS
22 # =====
23 # [PASS] Time = 151000 | rs1 = 0x01 and rs2 = 0x01 initialized to 0
24 # -----
25 # [WRITE] Time = 151000 | rd = 0x01, Data = 0x369d4b49
26 # -----
27 # [PASS] Time = 171000 | rs1 = 0x01, Expected = 0x369d4b49, Output =
    0x369d4b49
28 # [PASS] Time = 171000 | rs2 = 0x01, Expected = 0x369d4b49, Output =
    0x369d4b49
29 # [PASS] Time = 181000 | rs1 = 0x02 and rs2 = 0x02 initialized to 0
30 # -----
31 # [WRITE] Time = 181000 | rd = 0x02, Data = 0x2e53207a
32 # -----
33 # [PASS] Time = 201000 | rs1 = 0x02, Expected = 0x2e53207a, Output =
    0x2e53207a
34 # [PASS] Time = 201000 | rs2 = 0x02, Expected = 0x2e53207a, Output =
    0x2e53207a
35 # [PASS] Time = 211000 | rs1 = 0x03 and rs2 = 0x03 initialized to 0
36 # -----
37 # [WRITE] Time = 211000 | rd = 0x03, Data = 0x7cb0da7e
38 # -----
39 # [PASS] Time = 231000 | rs1 = 0x03, Expected = 0x7cb0da7e, Output =
    0x7cb0da7e
40 # [PASS] Time = 231000 | rs2 = 0x03, Expected = 0x7cb0da7e, Output =
    0x7cb0da7e
41 # [PASS] Time = 241000 | rs1 = 0x04 and rs2 = 0x04 initialized to 0
42 # -----
43 # [WRITE] Time = 241000 | rd = 0x04, Data = 0x6a8defda
44 # -----
45 # [PASS] Time = 261000 | rs1 = 0x04, Expected = 0x6a8defda, Output =
    0x6a8defda
46 # [PASS] Time = 261000 | rs2 = 0x04, Expected = 0x6a8defda, Output =
    0x6a8defda
47 # [PASS] Time = 271000 | rs1 = 0x05 and rs2 = 0x05 initialized to 0
48 # -----
49 # [WRITE] Time = 271000 | rd = 0x05, Data = 0xc7119e4e
50 # -----
51 # [PASS] Time = 291000 | rs1 = 0x05, Expected = 0xc7119e4e, Output =
    0xc7119e4e

```

```

52 # [PASS] Time = 291000 | rs2 = 0x05, Expected = 0xc7119e4e, Output =
    0xc7119e4e
53 # [PASS] Time = 301000 | rs1 = 0x06 and rs2 = 0x06 initialized to 0
54 # -----
55 # [WRITE] Time = 301000 | rd = 0x06, Data = 0xf0b39a02
56 # -----
57 # [PASS] Time = 321000 | rs1 = 0x06, Expected = 0xf0b39a02, Output =
    0xf0b39a02
58 # [PASS] Time = 321000 | rs2 = 0x06, Expected = 0xf0b39a02, Output =
    0xf0b39a02
59 # [PASS] Time = 331000 | rs1 = 0x07 and rs2 = 0x07 initialized to 0
60 # -----
61 # [WRITE] Time = 331000 | rd = 0x07, Data = 0xb81d179b
62 # -----
63 # [PASS] Time = 351000 | rs1 = 0x07, Expected = 0xb81d179b, Output =
    0xb81d179b
64 # [PASS] Time = 351000 | rs2 = 0x07, Expected = 0xb81d179b, Output =
    0xb81d179b
65 # [PASS] Time = 361000 | rs1 = 0x08 and rs2 = 0x08 initialized to 0
66 # -----
67 # [WRITE] Time = 361000 | rd = 0x08, Data = 0xcaf481d9
68 # -----
69 # [PASS] Time = 381000 | rs1 = 0x08, Expected = 0xcaf481d9, Output =
    0xcaf481d9
70 # [PASS] Time = 381000 | rs2 = 0x08, Expected = 0xcaf481d9, Output =
    0xcaf481d9
71 # [PASS] Time = 391000 | rs1 = 0x09 and rs2 = 0x09 initialized to 0
72 # -----
73 # [WRITE] Time = 391000 | rd = 0x09, Data = 0x4aae874c
74 # -----
75 # [PASS] Time = 411000 | rs1 = 0x09, Expected = 0x4aae874c, Output =
    0x4aae874c
76 # [PASS] Time = 411000 | rs2 = 0x09, Expected = 0x4aae874c, Output =
    0x4aae874c
77 # [PASS] Time = 421000 | rs1 = 0x0a and rs2 = 0x0a initialized to 0
78 # -----
79 # [WRITE] Time = 421000 | rd = 0x0a, Data = 0xd0bc7957
80 # -----
81 # [PASS] Time = 441000 | rs1 = 0x0a, Expected = 0xd0bc7957, Output =
    0xd0bc7957
82 # [PASS] Time = 441000 | rs2 = 0x0a, Expected = 0xd0bc7957, Output =
    0xd0bc7957
83 # [PASS] Time = 451000 | rs1 = 0x0b and rs2 = 0x0b initialized to 0
84 # -----
85 # [WRITE] Time = 451000 | rd = 0x0b, Data = 0x6aa8df9b
86 # -----
87 # [PASS] Time = 471000 | rs1 = 0x0b, Expected = 0x6aa8df9b, Output =
    0x6aa8df9b
88 # [PASS] Time = 471000 | rs2 = 0x0b, Expected = 0x6aa8df9b, Output =
    0x6aa8df9b
89 # [PASS] Time = 481000 | rs1 = 0x0c and rs2 = 0x0c initialized to 0
90 # -----
91 # [WRITE] Time = 481000 | rd = 0x0c, Data = 0xfd6562cf

```

```

92 # -----
93 # [PASS] Time = 501000 | rs1 = 0x0c, Expected = 0xfd6562cf, Output =
    0xfd6562cf
94 # [PASS] Time = 501000 | rs2 = 0x0c, Expected = 0xfd6562cf, Output =
    0xfd6562cf
95 # [PASS] Time = 511000 | rs1 = 0x0d and rs2 = 0x0d initialized to 0
96 # -----
97 # [WRITE] Time = 511000 | rd = 0x0d, Data = 0x25568ff3
98 # -----
99 # [PASS] Time = 531000 | rs1 = 0x0d, Expected = 0x25568ff3, Output =
    0x25568ff3
100 # [PASS] Time = 531000 | rs2 = 0x0d, Expected = 0x25568ff3, Output =
    0x25568ff3
101 # [PASS] Time = 541000 | rs1 = 0x0e and rs2 = 0x0e initialized to 0
102 # -----
103 # [WRITE] Time = 541000 | rd = 0x0e, Data = 0x66fa2046
104 # -----
105 # [PASS] Time = 561000 | rs1 = 0x0e, Expected = 0x66fa2046, Output =
    0x66fa2046
106 # [PASS] Time = 561000 | rs2 = 0x0e, Expected = 0x66fa2046, Output =
    0x66fa2046
107 # [PASS] Time = 571000 | rs1 = 0x0f and rs2 = 0x0f initialized to 0
108 # -----
109 # [WRITE] Time = 571000 | rd = 0x0f, Data = 0x41766910
110 # -----
111 # [PASS] Time = 591000 | rs1 = 0x0f, Expected = 0x41766910, Output =
    0x41766910
112 # [PASS] Time = 591000 | rs2 = 0x0f, Expected = 0x41766910, Output =
    0x41766910
113 # [PASS] Time = 601000 | rs1 = 0x10 and rs2 = 0x10 initialized to 0
114 # -----
115 # [WRITE] Time = 601000 | rd = 0x10, Data = 0x81103480
116 # -----
117 # [PASS] Time = 621000 | rs1 = 0x10, Expected = 0x81103480, Output =
    0x81103480
118 # [PASS] Time = 621000 | rs2 = 0x10, Expected = 0x81103480, Output =
    0x81103480
119 # [PASS] Time = 631000 | rs1 = 0x11 and rs2 = 0x11 initialized to 0
120 # -----
121 # [WRITE] Time = 631000 | rd = 0x11, Data = 0x2942e4d8
122 # -----
123 # [PASS] Time = 651000 | rs1 = 0x11, Expected = 0x2942e4d8, Output =
    0x2942e4d8
124 # [PASS] Time = 651000 | rs2 = 0x11, Expected = 0x2942e4d8, Output =
    0x2942e4d8
125 # [PASS] Time = 661000 | rs1 = 0x12 and rs2 = 0x12 initialized to 0
126 # -----
127 # [WRITE] Time = 661000 | rd = 0x12, Data = 0x546a052c
128 # -----
129 # [PASS] Time = 681000 | rs1 = 0x12, Expected = 0x546a052c, Output =
    0x546a052c
130 # [PASS] Time = 681000 | rs2 = 0x12, Expected = 0x546a052c, Output =
    0x546a052c

```

```

131 # [PASS] Time = 691000 | rs1 = 0x13 and rs2 = 0x13 initialized to 0
132 # -----
133 # [WRITE] Time = 691000 | rd = 0x13, Data = 0xe34c5b88
134 # -----
135 # [PASS] Time = 711000 | rs1 = 0x13, Expected = 0xe34c5b88, Output =
    0xe34c5b88
136 # [PASS] Time = 711000 | rs2 = 0x13, Expected = 0xe34c5b88, Output =
    0xe34c5b88
137 # [PASS] Time = 721000 | rs1 = 0x14 and rs2 = 0x14 initialized to 0
138 # -----
139 # [WRITE] Time = 721000 | rd = 0x14, Data = 0x3635d07
140 # -----
141 # [PASS] Time = 741000 | rs1 = 0x14, Expected = 0x03635d07, Output =
    0x03635d07
142 # [PASS] Time = 741000 | rs2 = 0x14, Expected = 0x03635d07, Output =
    0x03635d07
143 # [PASS] Time = 751000 | rs1 = 0x15 and rs2 = 0x15 initialized to 0
144 # -----
145 # [WRITE] Time = 751000 | rd = 0x15, Data = 0xc691eee3
146 # -----
147 # [PASS] Time = 771000 | rs1 = 0x15, Expected = 0xc691eee3, Output =
    0xc691eee3
148 # [PASS] Time = 771000 | rs2 = 0x15, Expected = 0xc691eee3, Output =
    0xc691eee3
149 # [PASS] Time = 781000 | rs1 = 0x16 and rs2 = 0x16 initialized to 0
150 # -----
151 # [WRITE] Time = 781000 | rd = 0x16, Data = 0x6e6773f3
152 # -----
153 # [PASS] Time = 801000 | rs1 = 0x16, Expected = 0x6e6773f3, Output =
    0x6e6773f3
154 # [PASS] Time = 801000 | rs2 = 0x16, Expected = 0x6e6773f3, Output =
    0x6e6773f3
155 # [PASS] Time = 811000 | rs1 = 0x17 and rs2 = 0x17 initialized to 0
156 # -----
157 # [WRITE] Time = 811000 | rd = 0x17, Data = 0xd0cd0050
158 # -----
159 # [PASS] Time = 831000 | rs1 = 0x17, Expected = 0xd0cd0050, Output =
    0xd0cd0050
160 # [PASS] Time = 831000 | rs2 = 0x17, Expected = 0xd0cd0050, Output =
    0xd0cd0050
161 # [PASS] Time = 841000 | rs1 = 0x18 and rs2 = 0x18 initialized to 0
162 # -----
163 # [WRITE] Time = 841000 | rd = 0x18, Data = 0x43c3b3e2
164 # -----
165 # [PASS] Time = 861000 | rs1 = 0x18, Expected = 0x43c3b3e2, Output =
    0x43c3b3e2
166 # [PASS] Time = 861000 | rs2 = 0x18, Expected = 0x43c3b3e2, Output =
    0x43c3b3e2
167 # [PASS] Time = 871000 | rs1 = 0x19 and rs2 = 0x19 initialized to 0
168 # -----
169 # [WRITE] Time = 871000 | rd = 0x19, Data = 0x77622873
170 # -----

```

```

171 # [PASS] Time = 891000 | rs1 = 0x19, Expected = 0x77622873, Output =
    0x77622873
172 # [PASS] Time = 891000 | rs2 = 0x19, Expected = 0x77622873, Output =
    0x77622873
173 # [PASS] Time = 901000 | rs1 = 0x1a and rs2 = 0x1a initialized to 0
174 # -----
175 # [WRITE] Time = 901000 | rd = 0x1a, Data = 0x9ef912bb
176 # -----
177 # [PASS] Time = 921000 | rs1 = 0x1a, Expected = 0x9ef912bb, Output =
    0x9ef912bb
178 # [PASS] Time = 921000 | rs2 = 0x1a, Expected = 0x9ef912bb, Output =
    0x9ef912bb
179 # [PASS] Time = 931000 | rs1 = 0x1b and rs2 = 0x1b initialized to 0
180 # -----
181 # [WRITE] Time = 931000 | rd = 0x1b, Data = 0x34c281fc
182 # -----
183 # [PASS] Time = 951000 | rs1 = 0x1b, Expected = 0x34c281fc, Output =
    0x34c281fc
184 # [PASS] Time = 951000 | rs2 = 0x1b, Expected = 0x34c281fc, Output =
    0x34c281fc
185 # [PASS] Time = 961000 | rs1 = 0x1c and rs2 = 0x1c initialized to 0
186 # -----
187 # [WRITE] Time = 961000 | rd = 0x1c, Data = 0xe659f7ae
188 # -----
189 # [PASS] Time = 981000 | rs1 = 0x1c, Expected = 0xe659f7ae, Output =
    0xe659f7ae
190 # [PASS] Time = 981000 | rs2 = 0x1c, Expected = 0xe659f7ae, Output =
    0xe659f7ae
191 # [PASS] Time = 991000 | rs1 = 0x1d and rs2 = 0x1d initialized to 0
192 # -----
193 # [WRITE] Time = 991000 | rd = 0x1d, Data = 0x713c11cf
194 # -----
195 # [PASS] Time = 1011000 | rs1 = 0x1d, Expected = 0x713c11cf, Output =
    0x713c11cf
196 # [PASS] Time = 1011000 | rs2 = 0x1d, Expected = 0x713c11cf, Output =
    0x713c11cf
197 # [PASS] Time = 1021000 | rs1 = 0x1e and rs2 = 0x1e initialized to 0
198 # -----
199 # [WRITE] Time = 1021000 | rd = 0x1e, Data = 0x87401cb6
200 # -----
201 # [PASS] Time = 1041000 | rs1 = 0x1e, Expected = 0x87401cb6, Output =
    0x87401cb6
202 # [PASS] Time = 1041000 | rs2 = 0x1e, Expected = 0x87401cb6, Output =
    0x87401cb6
203 # [PASS] Time = 1051000 | rs1 = 0x1f and rs2 = 0x1f initialized to 0
204 # -----
205 # [WRITE] Time = 1051000 | rd = 0x1f, Data = 0xa24d13c7
206 # -----
207 # [PASS] Time = 1071000 | rs1 = 0x1f, Expected = 0xa24d13c7, Output =
    0xa24d13c7
208 # [PASS] Time = 1071000 | rs2 = 0x1f, Expected = 0xa24d13c7, Output =
    0xa24d13c7
209 # =====

```

```

210 # TEST 4: WRITE ALL AND READ BACK
211 # =====
212 # -----
213 # [WRITE] Time = 1095000 | rd = 0x01, Data = 0x4c8e7537
214 # -----
215 # -----
216 # [WRITE] Time = 1116000 | rd = 0x02, Data = 0xc969e31a
217 # -----
218 # -----
219 # [WRITE] Time = 1136000 | rd = 0x03, Data = 0xd837cd88
220 # -----
221 # -----
222 # [WRITE] Time = 1156000 | rd = 0x04, Data = 0x9f28cd7b
223 # -----
224 # -----
225 # [WRITE] Time = 1176000 | rd = 0x05, Data = 0x87f27d84
226 # -----
227 # -----
228 # [WRITE] Time = 1196000 | rd = 0x06, Data = 0x9162bd0c
229 # -----
230 # -----
231 # [WRITE] Time = 1216000 | rd = 0x07, Data = 0x613fb4ba
232 # -----
233 # -----
234 # [WRITE] Time = 1236000 | rd = 0x08, Data = 0xa75a26b9
235 # -----
236 # -----
237 # [WRITE] Time = 1256000 | rd = 0x09, Data = 0x97befd48
238 # -----
239 # -----
240 # [WRITE] Time = 1276000 | rd = 0x0a, Data = 0x74871bf9
241 # -----
242 # -----
243 # [WRITE] Time = 1296000 | rd = 0x0b, Data = 0x9b731590
244 # -----
245 # -----
246 # [WRITE] Time = 1316000 | rd = 0x0c, Data = 0x22e8e590
247 # -----
248 # -----
249 # [WRITE] Time = 1336000 | rd = 0x0d, Data = 0xd66099fd
250 # -----
251 # -----
252 # [WRITE] Time = 1356000 | rd = 0x0e, Data = 0xba542fdb
253 # -----
254 # -----
255 # [WRITE] Time = 1376000 | rd = 0x0f, Data = 0x8bb8376e
256 # -----
257 # -----
258 # [WRITE] Time = 1396000 | rd = 0x10, Data = 0x1603d7b9
259 # -----
260 # -----
261 # [WRITE] Time = 1416000 | rd = 0x11, Data = 0x781c5ba3
262 # -----

```

```

263 # -----
264 # [WRITE] Time = 1436000 | rd = 0x12, Data = 0x2381cb4e
265 # -----
266 # -----
267 # [WRITE] Time = 1456000 | rd = 0x13, Data = 0x671e6b6f
268 # -----
269 # -----
270 # [WRITE] Time = 1476000 | rd = 0x14, Data = 0x2ebaab9a
271 # -----
272 # -----
273 # [WRITE] Time = 1496000 | rd = 0x15, Data = 0xc3391889
274 # -----
275 # -----
276 # [WRITE] Time = 1516000 | rd = 0x16, Data = 0xcfe6f7b5
277 # -----
278 # -----
279 # [WRITE] Time = 1536000 | rd = 0x17, Data = 0x6be10d7b
280 # -----
281 # -----
282 # [WRITE] Time = 1556000 | rd = 0x18, Data = 0x720de158
283 # -----
284 # -----
285 # [WRITE] Time = 1576000 | rd = 0x19, Data = 0xdcdd928e
286 # -----
287 # -----
288 # [WRITE] Time = 1596000 | rd = 0x1a, Data = 0x327638a8
289 # -----
290 # -----
291 # [WRITE] Time = 1616000 | rd = 0x1b, Data = 0xdb062489
292 # -----
293 # -----
294 # [WRITE] Time = 1636000 | rd = 0x1c, Data = 0x879f10ac
295 # -----
296 # -----
297 # [WRITE] Time = 1656000 | rd = 0x1d, Data = 0x38674ea5
298 # -----
299 # -----
300 # [WRITE] Time = 1676000 | rd = 0x1e, Data = 0x5a2a5c21
301 # -----
302 # -----
303 # [WRITE] Time = 1696000 | rd = 0x1f, Data = 0xd5f6a9d
304 # -----
305 # [PASS] Time = 1721000 | rs1 = 0x01, Expected = 0x4c8e7537, Output =
    0x4c8e7537
306 # [PASS] Time = 1721000 | rs2 = 0x02, Expected = 0xc969e31a, Output =
    0xc969e31a
307 # [PASS] Time = 1731000 | rs1 = 0x02, Expected = 0xc969e31a, Output =
    0xc969e31a
308 # [PASS] Time = 1731000 | rs2 = 0x03, Expected = 0xd837cd88, Output =
    0xd837cd88
309 # [PASS] Time = 1741000 | rs1 = 0x03, Expected = 0xd837cd88, Output =
    0xd837cd88

```



```

310 # [PASS] Time = 1741000 | rs2 = 0x04, Expected = 0x9f28cd7b, Output =
    0x9f28cd7b
311 # [PASS] Time = 1751000 | rs1 = 0x04, Expected = 0x9f28cd7b, Output =
    0x9f28cd7b
312 # [PASS] Time = 1751000 | rs2 = 0x05, Expected = 0x87f27d84, Output =
    0x87f27d84
313 # [PASS] Time = 1761000 | rs1 = 0x05, Expected = 0x87f27d84, Output =
    0x87f27d84
314 # [PASS] Time = 1761000 | rs2 = 0x06, Expected = 0x9162bd0c, Output =
    0x9162bd0c
315 # [PASS] Time = 1771000 | rs1 = 0x06, Expected = 0x9162bd0c, Output =
    0x9162bd0c
316 # [PASS] Time = 1771000 | rs2 = 0x07, Expected = 0x613fb4ba, Output =
    0x613fb4ba
317 # [PASS] Time = 1781000 | rs1 = 0x07, Expected = 0x613fb4ba, Output =
    0x613fb4ba
318 # [PASS] Time = 1781000 | rs2 = 0x08, Expected = 0xa75a26b9, Output =
    0xa75a26b9
319 # [PASS] Time = 1791000 | rs1 = 0x08, Expected = 0xa75a26b9, Output =
    0xa75a26b9
320 # [PASS] Time = 1791000 | rs2 = 0x09, Expected = 0x97befd48, Output =
    0x97befd48
321 # [PASS] Time = 1801000 | rs1 = 0x09, Expected = 0x97befd48, Output =
    0x97befd48
322 # [PASS] Time = 1801000 | rs2 = 0x0a, Expected = 0x74871bf9, Output =
    0x74871bf9
323 # [PASS] Time = 1811000 | rs1 = 0x0a, Expected = 0x74871bf9, Output =
    0x74871bf9
324 # [PASS] Time = 1811000 | rs2 = 0x0b, Expected = 0x9b731590, Output =
    0x9b731590
325 # [PASS] Time = 1821000 | rs1 = 0x0b, Expected = 0x9b731590, Output =
    0x9b731590
326 # [PASS] Time = 1821000 | rs2 = 0x0c, Expected = 0x22e8e590, Output =
    0x22e8e590
327 # [PASS] Time = 1831000 | rs1 = 0x0c, Expected = 0x22e8e590, Output =
    0x22e8e590
328 # [PASS] Time = 1831000 | rs2 = 0x0d, Expected = 0xd66099fd, Output =
    0xd66099fd
329 # [PASS] Time = 1841000 | rs1 = 0x0d, Expected = 0xd66099fd, Output =
    0xd66099fd
330 # [PASS] Time = 1841000 | rs2 = 0x0e, Expected = 0xba542fdb, Output =
    0xba542fdb
331 # [PASS] Time = 1851000 | rs1 = 0x0e, Expected = 0xba542fdb, Output =
    0xba542fdb
332 # [PASS] Time = 1851000 | rs2 = 0x0f, Expected = 0x8bb8376e, Output =
    0x8bb8376e
333 # [PASS] Time = 1861000 | rs1 = 0x0f, Expected = 0x8bb8376e, Output =
    0x8bb8376e
334 # [PASS] Time = 1861000 | rs2 = 0x10, Expected = 0x1603d7b9, Output =
    0x1603d7b9
335 # [PASS] Time = 1871000 | rs1 = 0x10, Expected = 0x1603d7b9, Output =
    0x1603d7b9

```

```

336 # [PASS] Time = 1871000 | rs2 = 0x11, Expected = 0x781c5ba3, Output =
    0x781c5ba3
337 # [PASS] Time = 1881000 | rs1 = 0x11, Expected = 0x781c5ba3, Output =
    0x781c5ba3
338 # [PASS] Time = 1881000 | rs2 = 0x12, Expected = 0x2381cb4e, Output =
    0x2381cb4e
339 # [PASS] Time = 1891000 | rs1 = 0x12, Expected = 0x2381cb4e, Output =
    0x2381cb4e
340 # [PASS] Time = 1891000 | rs2 = 0x13, Expected = 0x671e6b6f, Output =
    0x671e6b6f
341 # [PASS] Time = 1901000 | rs1 = 0x13, Expected = 0x671e6b6f, Output =
    0x671e6b6f
342 # [PASS] Time = 1901000 | rs2 = 0x14, Expected = 0x2ebaab9a, Output =
    0x2ebaab9a
343 # [PASS] Time = 1911000 | rs1 = 0x14, Expected = 0x2ebaab9a, Output =
    0x2ebaab9a
344 # [PASS] Time = 1911000 | rs2 = 0x15, Expected = 0xc3391889, Output =
    0xc3391889
345 # [PASS] Time = 1921000 | rs1 = 0x15, Expected = 0xc3391889, Output =
    0xc3391889
346 # [PASS] Time = 1921000 | rs2 = 0x16, Expected = 0xcfe6f7b5, Output =
    0xcfe6f7b5
347 # [PASS] Time = 1931000 | rs1 = 0x16, Expected = 0xcfe6f7b5, Output =
    0xcfe6f7b5
348 # [PASS] Time = 1931000 | rs2 = 0x17, Expected = 0x6be10d7b, Output =
    0x6be10d7b
349 # [PASS] Time = 1941000 | rs1 = 0x17, Expected = 0x6be10d7b, Output =
    0x6be10d7b
350 # [PASS] Time = 1941000 | rs2 = 0x18, Expected = 0x720de158, Output =
    0x720de158
351 # [PASS] Time = 1951000 | rs1 = 0x18, Expected = 0x720de158, Output =
    0x720de158
352 # [PASS] Time = 1951000 | rs2 = 0x19, Expected = 0xdcdd928e, Output =
    0xdcdd928e
353 # [PASS] Time = 1961000 | rs1 = 0x19, Expected = 0xdcdd928e, Output =
    0xdcdd928e
354 # [PASS] Time = 1961000 | rs2 = 0x1a, Expected = 0x327638a8, Output =
    0x327638a8
355 # [PASS] Time = 1971000 | rs1 = 0x1a, Expected = 0x327638a8, Output =
    0x327638a8
356 # [PASS] Time = 1971000 | rs2 = 0x1b, Expected = 0xdb062489, Output =
    0xdb062489
357 # [PASS] Time = 1981000 | rs1 = 0x1b, Expected = 0xdb062489, Output =
    0xdb062489
358 # [PASS] Time = 1981000 | rs2 = 0x1c, Expected = 0x879f10ac, Output =
    0x879f10ac
359 # [PASS] Time = 1991000 | rs1 = 0x1c, Expected = 0x879f10ac, Output =
    0x879f10ac
360 # [PASS] Time = 1991000 | rs2 = 0x1d, Expected = 0x38674ea5, Output =
    0x38674ea5
361 # [PASS] Time = 2001000 | rs1 = 0x1d, Expected = 0x38674ea5, Output =
    0x38674ea5

```

```

362 # [PASS] Time = 2001000 | rs2 = 0x1e, Expected = 0x5a2a5c21, Output =
    0x5a2a5c21
363 # [PASS] Time = 2011000 | rs1 = 0x1e, Expected = 0x5a2a5c21, Output =
    0x5a2a5c21
364 # [PASS] Time = 2011000 | rs2 = 0x1f, Expected = 0x0d5f6a9d, Output =
    0x0d5f6a9d
365 # =====
366 # SUMMARY
367 # =====
368 # TOTAL TESTS : 157
369 # TOTAL PASSED: 157
370 # TOTAL FAILED: 0
371 # =====> ALL TESTS PASSED
372 # ** Note: $finish : ../../tb/tb_reg.v(186)
373 # Time: 2111 ns Iteration: 0 Instance: /tb_reg

```

Simulation 1: Simulation results of the RegFile module.

5.2 Processor testbench results

```

1 # =====
2 # =====
3 # TEST BEGIN
4 # =====
5 # =====
6 # TEST 1
7 # =====
8 # [PASS] Time = 371 | ADDI x1, x0, 10 | Output x1 = 0
    x0000000a
9 # [PASS] Time = 371 | ADDI x2, x0, -5 | Output x2 = 0
    xfffffffb
10 # [PASS] Time = 371 | ADD x3, x1, x2 | Output x3 = 0
    x00000005
11 # [PASS] Time = 371 | SUB x4, x1, x2 | Output x4 = 0
    x0000000f
12 # [PASS] Time = 371 | AND x5, x1, x2 | Output x5 = 0
    x0000000a
13 # [PASS] Time = 371 | OR x6, x1, x2 | Output x6 = 0
    xfffffffb
14 # [PASS] Time = 371 | XOR x7, x1, x2 | Output x7 = 0
    xffffff1
15 # [PASS] Time = 371 | SLLI x8, x1, 2 | Output x8 = 0
    x00000028
16 # [PASS] Time = 371 | SRAI x9, x2, 1 | Output x9 = 0
    xfffffffd
17 # [PASS] Time = 371 | SRLI x10, x2, 1 | Output x10 = 0
    x7ffffffd
18 # [PASS] Time = 371 | SLT x11, x2, x1 | Output x11 = 0
    x00000001
19 # [PASS] Time = 371 | SLTU x12, x2, x1 | Output x12 = 0
    x00000000
20 # [PASS] Time = 371 | MUL x13, x1, x1 | Output x13 = 0
    x00000064

```

```

21 # [PASS] Time = 371 | DIV x14, x1, x2 | Output x14 = 0
    xfffffffef
22 # [PASS] Time = 371 | REM x15, x1, x2 | Output x15 = 0
    x00000000
23 # [PASS] Time = 371 | DIVU x16, x2, x1 | Output x16 = 0
    x19999999
24 # [PASS] Time = 371 | LW x18, 100(x0) | Output x18 = 0
    x00000005
25 # [PASS] Time = 371 | ADDI x19, x0, 1 | Output x19 = 0
    x00000001
26 # [PASS] Time = 371 | JAL x20, 8 | Output x20 = 0
    x00000058
27 # [PASS] Time = 371 | ADDI x21, x0, 2 | Output x21 = 0
    x00000002
28 # [PASS] Time = 371 | LUI x22, 0x12345 | Output x22 = 0
    x12345000
29 # [PASS] Time = 371 | XORI x23, x1, 5 | Output x23 = 0
    x0000000f
30 # [PASS] Time = 371 | ANDI x24, x1, 0xF | Output x24 = 0
    x0000000a
31 # [PASS] Time = 371 | ORI x25, x13, 0xFF00 | Output x25 = 0
    xffffff64
32 # [PASS] Time = 371 | SLTI x26, x7, 0x28 | Output x26 = 0
    x00000001
33 # [PASS] Time = 371 | LTIU x27, x8, 0xFFFF_FFF1 | Output x27 = 0
    x00000001
34 # [PASS] Time = 371 | SLL x28, x1, x19 | Output x28 = 0
    x00000014
35 # [PASS] Time = 371 | SRL x29, x6, x19 | Output x29 = 0
    x7ffffffd
36 # [PASS] Time = 371 | SRA x30, x6, x19 | Output x30 = 0
    xfffffffd
37 # [PASS] Time = 371 | REMU x31, x6, x3 | Output x31 = 0
    x00000001
38 # [PASS] HALT asserted.
39 # =====
40 # TEST 2 (REUSED REGISTERS)
41 # =====
42 # [PASS] Time = 651 | ADDI x1, x0, 0xFFFF_FFFB | Output x1 = 0
    xfffffffb
43 # [PASS] Time = 651 | ADDI x2, x0, 3 | Output x2 = 0
    x00000003
44 # [PASS] Time = 651 | MULH x3, x1, x2 | Output x3 = 0
    xfffffffb
45 # [PASS] Time = 651 | MULHSU x4, x1, x2 | Output x4 = 0
    xfffffffb
46 # [PASS] Time = 651 | MULHU x5, x1, x2 | Output x5 = 0
    x00000002
47 # [PASS] Time = 651 | ADDI x6, x0, 0xABCD_FE98 | Output x6 = 0
    xfffffe98
48 # [PASS] Time = 651 | LB x7, 100(x0) | Output x7 = 0
    xffffff98

```

```

49 # [PASS] Time = 651 |          LH x8, 104(x0) | Output x8 = 0
    xfffffe98
50 # [PASS] Time = 651 |          LBU x9, 105(x0) | Output x9 = 0
    x000000fe
51 # [PASS] Time = 651 |          LHU x10, 104(x0) | Output x10 = 0
    x0000fe98
52 # [PASS] Time = 651 |          ADD x11, x9, x10 | Output x11 = 0
    x0000ff96
53 # [PASS] Time = 651 |          OR x12, x9, x10 | Output x12 = 0
    x0000fefe
54 # [PASS] Time = 651 |          LW x13, 120(x0) | Output x13 = 0
    x000000fe
55 # [PASS] Time = 651 |          JALR x14, 130(x0) | Output x14 = 0
    x00000054
56 # [PASS] HALT asserted.
57 # =====
58 # SUMMARY
59 # =====
60 # TOTAL TESTS : 46
61 # TOTAL PASSED: 46
62 # TOTAL FAILED: 0
63 # =====> ALL TESTS PASSED
64 # =====
65 # TEST END
66 # =====
67 # ** Note: $finish      : ../../tb/tb_single.v(230)
68 #      Time: 751 ns   Iteration: 0   Instance: /tb_single

```

Simulate 2: Testbench results of the Processor module.

6 Simulation waveform

6.1 RegFile simulation waveform

The screenshot in Figure 1 presents a portion of the waveform from Test 3. In this test, a random value is written to the destination register. The waveform confirms that the same value can be correctly read from both source registers, rs1 and rs2.

 


Figure 1

Figure 1 shows that at the positive clock edge occurring at 185141 ps, the write enable (**we**) signal is asserted. At this moment, the destination register **rd** is set to 0x2, and the written data **rd_data** is 32'h2e53207a. Because the storage is updated synchronously with the positive clock edge, while **rs1** and **rs2** can be read immediately after the new value is written, both **rs1_data**, **rs2_data** are updated to 32'h2e53207a on the next clock edge. This behavior confirms the correct store and read operations of the Register File module.

6.2 Processor simulation waveform

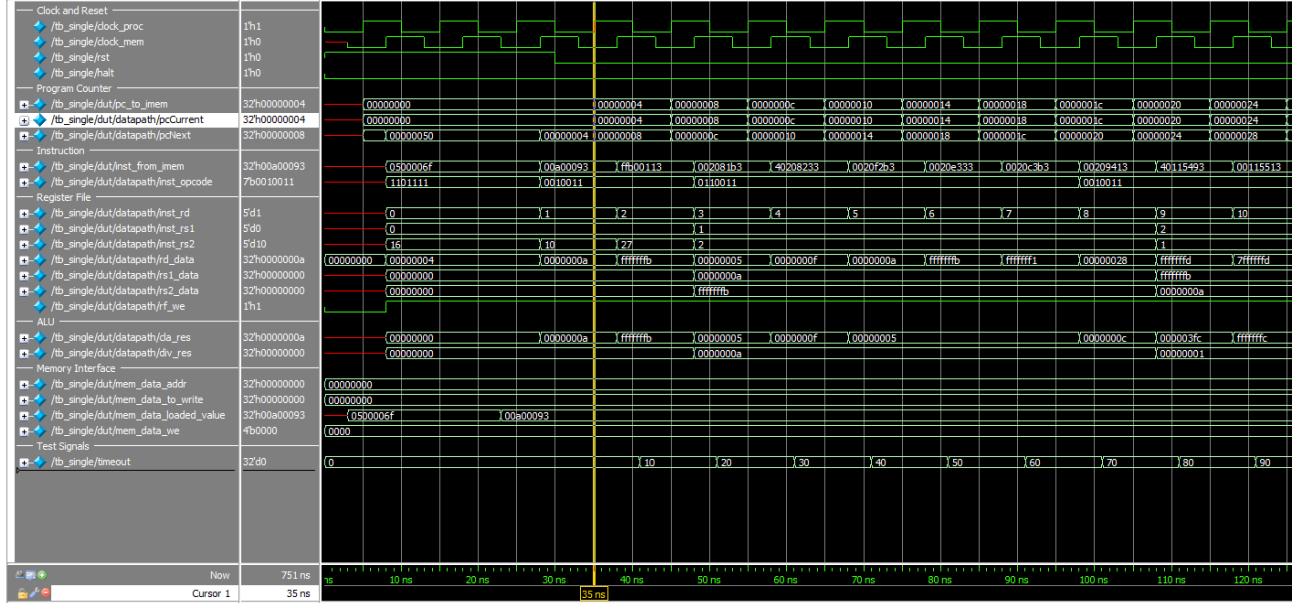


Figure 2

Looking at Figure 2, we can see that the first 30 ns is used to load instructions into the memory array while reset is asserted. Once reset is released at $t = 30\text{ns}$, instruction execution begins starting from $\text{PC} = 0\text{x}00$.

The first instruction is $0\text{x}00\text{a}00093$ (ADDI $x1, x0, 10$). The instruction fetch occurs on the positive edge of `clock_mem`, where the instruction is read from instruction memory into the `inst_from_imem` signal. The processor then decodes this instruction combinationally: `inst_rd` becomes 1 ($x1$), `inst_rs1` becomes 0 ($x0$), and the immediate value is extracted as 10. Since ADDI is an I-type instruction, `inst_rs2` is not used by the operation, but the decoder still extracts bits [24:20] from the instruction encoding. The register file performs a combinational read, so `rs1_data` immediately reflects the value of $x0$ (which is 0). On the next positive edge of `clock_proc`, the result ($0 + 10 = 10$) is written to register $x1$, and the PC increments to $0\text{x}04$.

Looking at a later instruction $0\text{x}002081\text{b}3$ at $\text{PC} = 0\text{x}08$ (ADD $x3, x1, x2$), we observe more complex datapath behavior. The decoder extracts: `inst_rd` = 3 ($x3$), `inst_rs1` = 1 ($x1$), `inst_rs2` = 2 ($x2$). The register file performs combinational reads, outputting `rs1_data` = $0\text{x}A$ (10 decimal) and `rs2_data` = $0\text{x}FFFFFFFB$ (-5 in two's complement). These values are fed into the CLA (Carry Lookahead Adder) module, which computes $10 + (-5) = 5$. The `cla_res` signal shows $0\text{x}00000005$, and this value propagates to `rd_data`. On the next positive edge of `clock_proc`, the value 5 is written to register $x3$.

The key timing relationship is: instruction fetch happens on the positive edge of `clock_mem`, combinational decoding and ALU computation occur immediately, and register writeback happens on the next positive edge of `clock_proc`. Memory operations (loads/stores) use the negative edge of `clock_mem` for data access to avoid conflicts with instruction fetch.

 


Figure 3

Looking at the instruction 0x02115833 (DIVU x16, x2, x1) executing around 180 ns in Figure 3, we observe the unsigned division operation. The `rs2_data` signal shows 0x0000000A (10 decimal), which is the value from register x1, while `rs1_data` shows 0xFFFFFFFFB (4,294,967,291 unsigned), which is the value from register x2. Note that DIVU follows the format DIVU rd, rs1, rs2, which computes $rd = rs1 / rs2$. Therefore, this instruction calculates $x2 / x1 = 4,294,967,291 / 10 = 429,496,729 = 0x19999999$. This unsigned division is executed by the `divider_unsigned` module, and the result appears on the `div_res` signal as 0x19999999. The `rd_data` signal also reflects this value, confirming that 0x19999999 will be written to register x16 on the next positive edge of `clock_proc`.

At approximately 188 ns, a store instruction 0x06302223 (SW x3, 100(x0)) executes. The `rf_we` (register file write enable) signal is deasserted because store instructions do not write to any register, unlike arithmetic or load instructions which require register writeback. For the SW instruction format (S-type), `rs1` provides the base address, `rs2` provides the source data, and the immediate provides the offset. In this case, `inst_rs2` = 3 (x3) with `rs2_data` = 0x00000005, `inst_rs1` = 0 (x0) with `rs1_data` = 0x00000000, and the offset is 100. The effective address is calculated as $0 + 100 = 100$ (decimal) = 0x00000064 (hex), which appears on `mem_data_addr`. The value 0x00000005 from x3 appears on `mem_data_to_write`, and this data is written to memory address 100 on the negative edge of `clock_mem`.

Subsequently, when instruction 0x06402903 (LW x18, 100(x0)) executes, the processor reads from the same memory location. The effective address calculation uses `rs1_data` = 0x00000000 (from x0) plus offset 100, resulting in address 0x00000064 on `mem_data_addr`. The `mem_data_loaded_value` signal shows 0x00000005, which is the data previously stored. The `inst_rd` field specifies x18 as the destination register, so this loaded value will be written to register x18 on the next `clock_proc` positive edge.

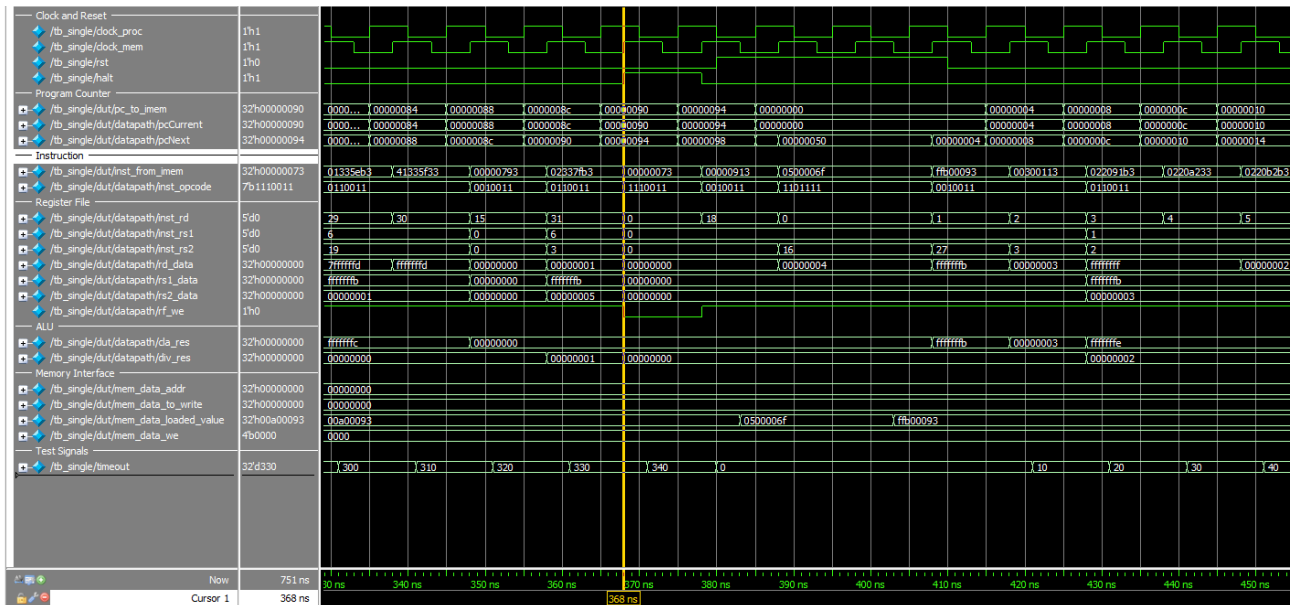


Figure 4

In Figure 4, at approximately 368 ns, the HALT instruction (0x00000073) is executed at PC = 0x90. This causes the halt signal to assert high, indicating successful completion of Test 1. The processor stops fetching and executing further instructions when halt is asserted. At 380 ns, the testbench reasserts the rst (reset) signal to reinitialize the processor state for Test 2. During this reset phase, the program counter returns to 0x0, and all 32 registers in the register file are cleared to 0x0. The testbench then loads a new sequence of instructions into instruction memory before releasing reset to begin Test 2 execution.

7 Timing closure and Resource utilization

7.1 Timing closure

Design Timing Summary		
Setup	Hold	Pulse Width
Worst Negative Slack (WNS): -106,309 ns	Worst Hold Slack (WHS): -0,239 ns	Worst Pulse Width Slack (WPWS): 3,500 ns
Total Negative Slack (TNS): -104255,298 ns	Total Hold Slack (THS): -54,937 ns	Total Pulse Width Negative Slack (TPWS): 0,000 ns
Number of Failing Endpoints: 1023	Number of Failing Endpoints: 1023	Number of Failing Endpoints: 0
Total Number of Endpoints: 2046	Total Number of Endpoints: 2046	Total Number of Endpoints: 1024
Timing constraints are not met.		

Figure 5: Timing summary.

Based on the implementation results from Vivado, the timing summary is as follows:

- Clock (clock_proc) constraint: 125 MHz (Period: 8.000 ns)
- Worst negative slack (WNS): -106.309 ns
- Conclusion: The design has not achieved Timing closure (Timing constraints are not met).

The negative WNS indicates that the signal propagation delay exceeds the clock period constraint. This is expected for a single-cycle processor architecture. In a single-cycle design, the critical path is significantly long as it must traverse multiple stages within one clock cycle, including instruction memory fetch, register file read, ALU/divider execution, data memory

access and write-back.

Based on the WNS, the minimum clock period required for the design to function correctly is:

$$T_{min} = T_{constraint} - WNS = 8.000 - (-106.309) \approx 114.31ns$$

The estimated maximum operating frequency (Fmax) is:

$$F_{max} = \frac{1}{T_{min}} \approx 8.75MHz$$

7.2 Resource utilization

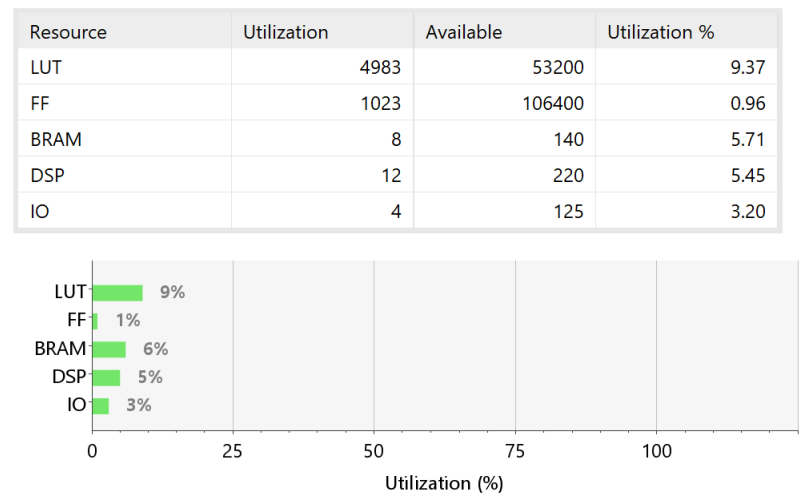


Figure 6: Utilization summary.

The design fits comfortably within the available resources of the Arty Z7-20 board. The utilization is dominated by Slice LUTs (Look-up Tables) rather than Flip-Flops. This is consistent with a single-cycle architecture, which relies heavily on large combinational logic blocks (such as the ALU, multiplier, and especially the divider) to complete instructions in a single cycle, rather than pipelining registers.